
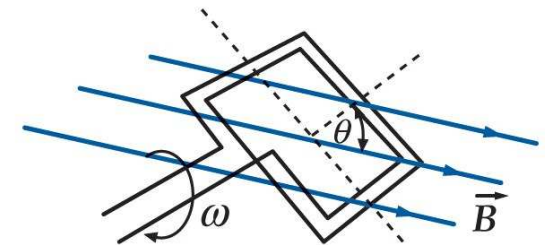


# Alternating Current Generator

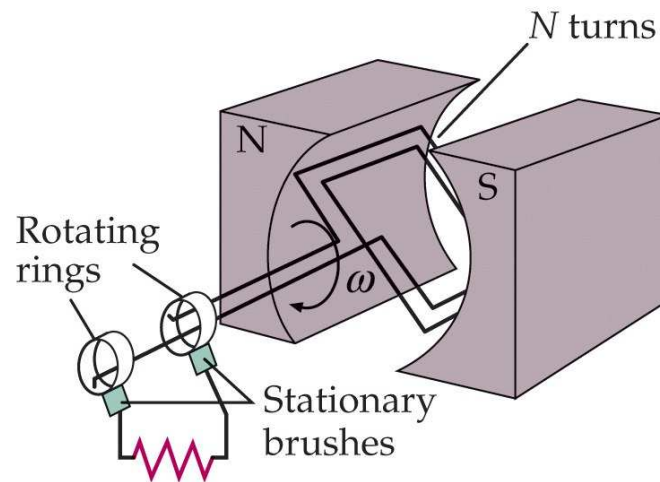

Coil of  $N$  turns and cross-sectional area  $A$  rotating with angular frequency  $\omega$  in uniform magnetic field  $\vec{B}$ .

- Angle between area vector and magnetic field vector:  $\theta = \omega t$ .
- Flux through coil:  $\Phi_B = NBA \cos(\omega t)$ .
- Induced EMF:  $\mathcal{E} = -\frac{d\Phi_B}{dt} = \mathcal{E}_{max} \sin(\omega t)$  with amplitude  $\mathcal{E}_{max} = NBA\omega$ .
- U.S. household outlet values:
  - $\mathcal{E}_{max} = 120V\sqrt{2} \simeq 170V$
  - $f = 60\text{Hz}$ ,  $\omega = 2\pi f \simeq 377\text{rad/s}$ .



# Single Device in AC Circuit: Resistor



Voltage of ac source :  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$




Current through device:  $I = I_{max} \cos(\omega t - \delta)$

## Resistor

$$V_R = RI = \mathcal{E}_{max} \cos \omega t \Rightarrow I = \frac{\mathcal{E}_{max}}{R} \cos \omega t$$

amplitude:  $I_{max} = \frac{\mathcal{E}_{max}}{R}$ , phase angle:  $\delta = 0$

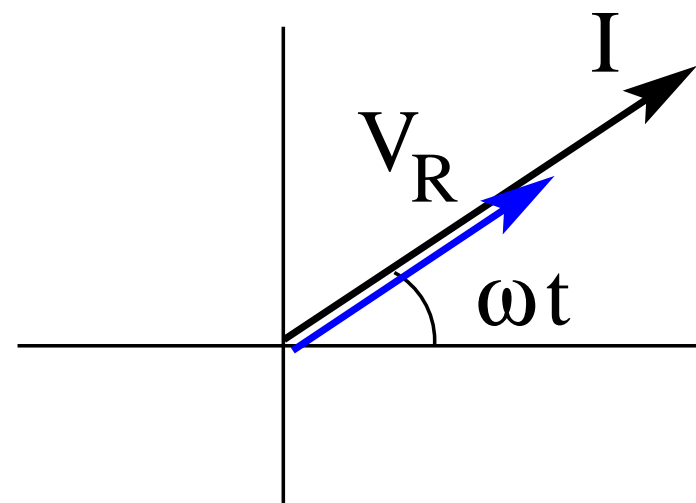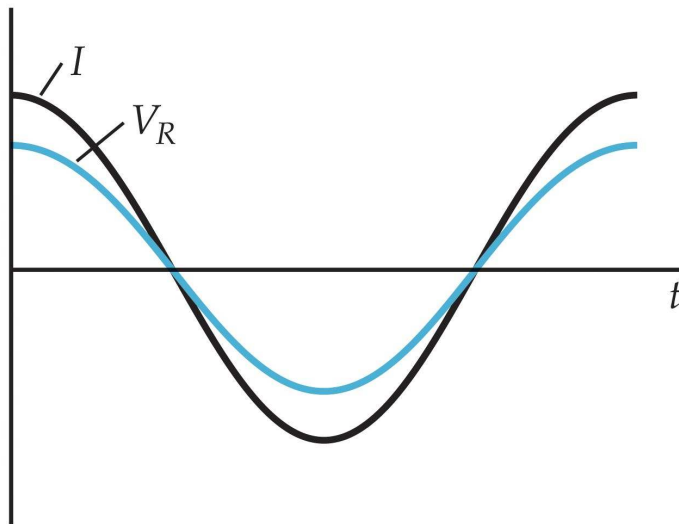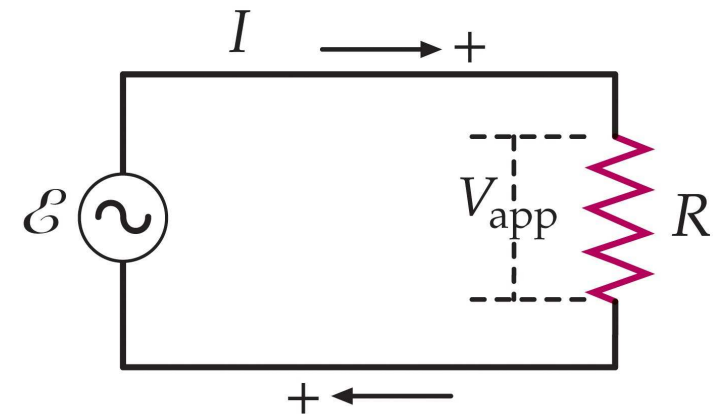impedance:  $X_R \equiv \frac{\mathcal{E}_{max}}{I_{max}} = R$  (resistance)



# Single Device in AC Circuit: Inductor



Voltage of ac source :  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$




Current through device:  $I = I_{max} \cos(\omega t - \delta)$

## Inductor

$$V_L = L \frac{dI}{dt} = \mathcal{E}_{max} \cos \omega t \Rightarrow I = \frac{\mathcal{E}_{max}}{\omega L} \sin(\omega t)$$

amplitude:  $I_{max} = \frac{\mathcal{E}_{max}}{\omega L}$ , phase angle:  $\delta = \frac{\pi}{2}$

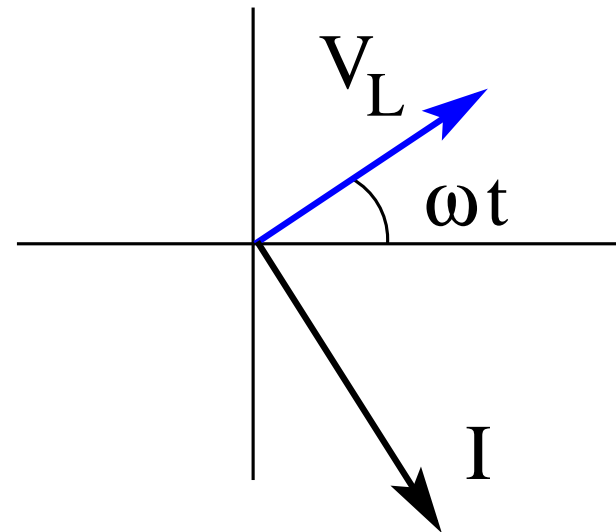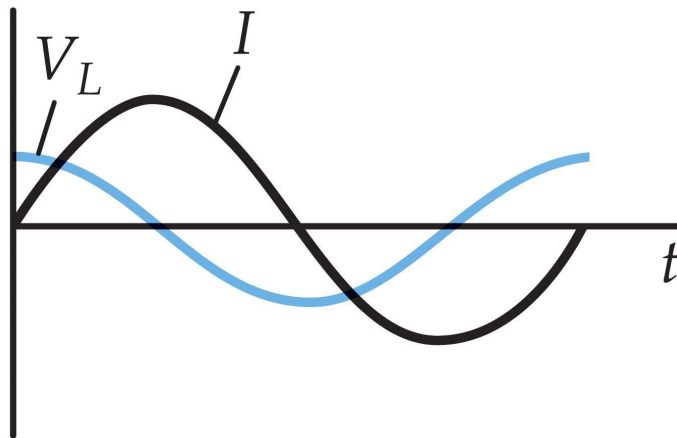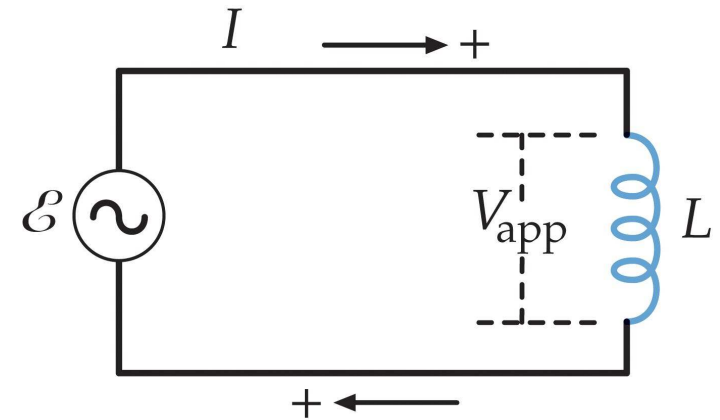impedance:  $X_L \equiv \frac{\mathcal{E}_{max}}{I_{max}} = \omega L$  (inductive reactance)



# Single Device in AC Circuit: Capacitor



Voltage of ac source :  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$




Current through device:  $I = I_{max} \cos(\omega t - \delta)$

## Capacitor

$$V_C = \frac{Q}{C} = \mathcal{E}_{max} \cos \omega t \Rightarrow I = \frac{dQ}{dt} = -\omega C \mathcal{E}_{max} \sin(\omega t)$$

amplitude:  $I_{max} = \omega C \mathcal{E}_{max}$ , phase angle:  $\delta = -\frac{\pi}{2}$

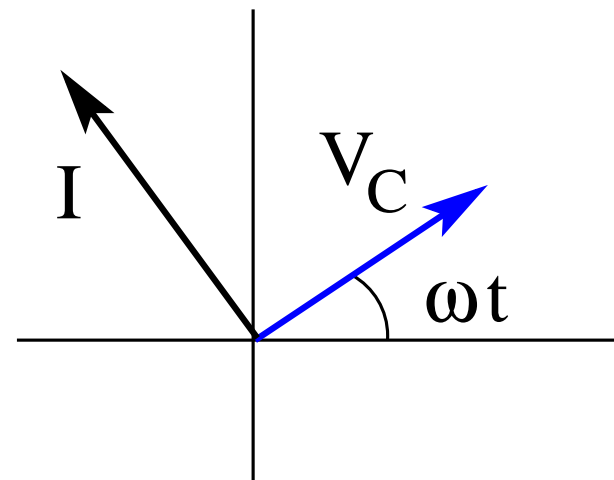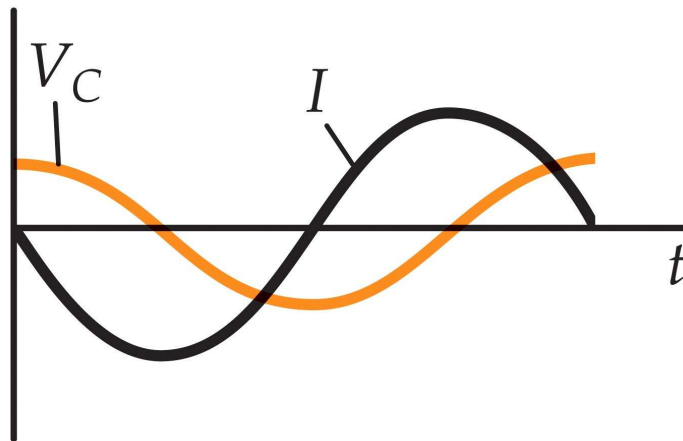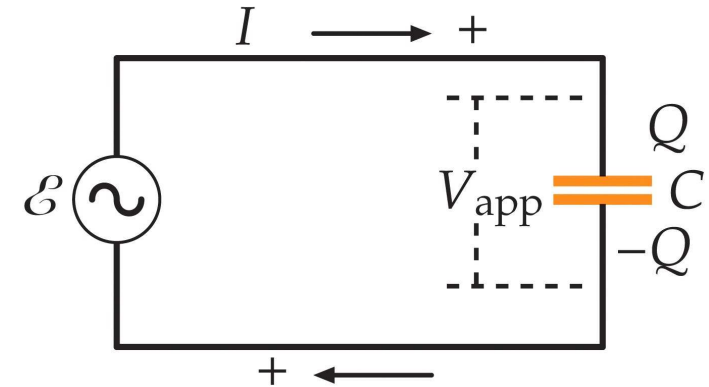impedance:  $X_C \equiv \frac{\mathcal{E}_{max}}{I_{max}} = \frac{1}{\omega C}$  (capacitive reactance)






# Single Device in AC Circuit: Application (1)



The ac voltage source  $\mathcal{E} = \mathcal{E}_{max} \sin \omega t$  has an amplitude of  $\mathcal{E}_{max} = 24\text{V}$  and an angular frequency of  $\omega = 10\text{rad/s}$ .

In each of the three circuits, find

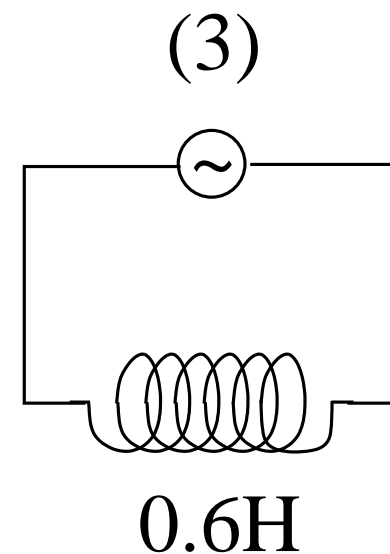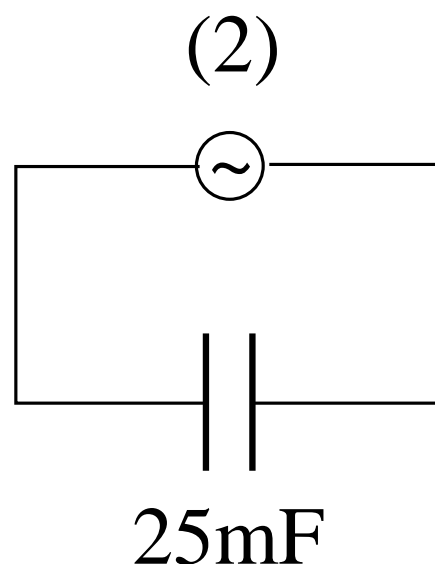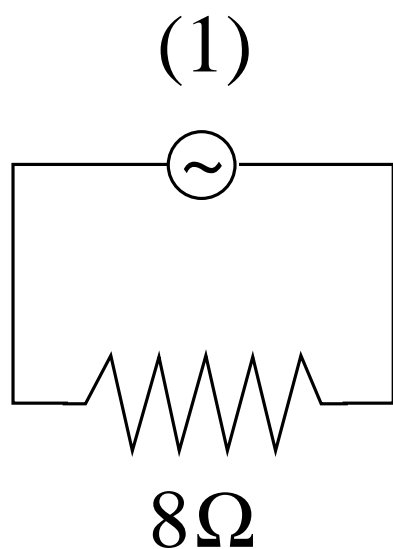- (a) the current amplitude  $I_{max}$ ,
- (b) the current  $I$  at time  $t = 1\text{s}$ .




## Single Device in AC Circuit: Application (2)



Consider an ac generator  $\mathcal{E}(t) = \mathcal{E}_{max} \cos(\omega t)$ ,  $\mathcal{E}_{max} = 25\text{V}$ ,  $\omega = 377\text{rad/s}$  connected to an inductor with inductance  $L = 12.7\text{H}$ .

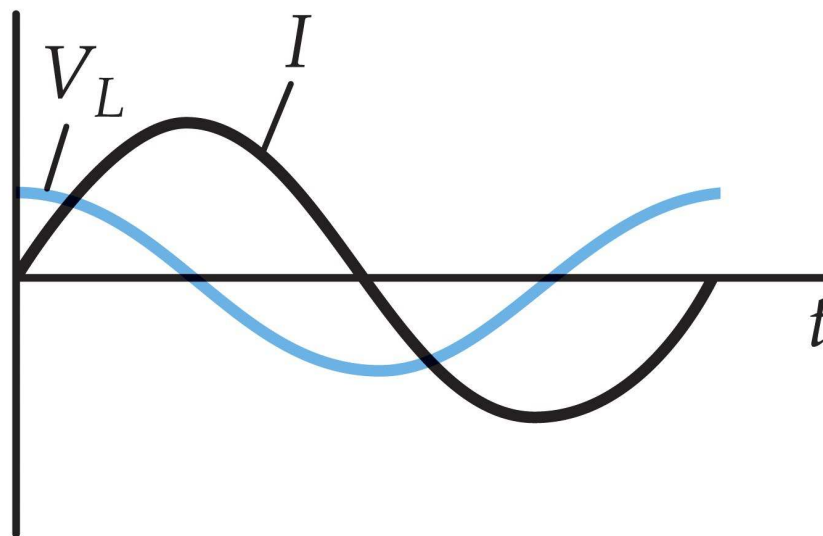- (a) Find the maximum value of the current.
- (b) Find the current when the emf is zero and decreasing.
- (c) Find the current when the emf is  $-12.5\text{V}$  and decreasing.
- (d) Find the power supplied by the generator at the instant described in (c).




## Single Device in AC Circuit: Application (3)



Consider an ac generator  $\mathcal{E}(t) = \mathcal{E}_{max} \cos(\omega t)$ ,  $\mathcal{E}_{max} = 25\text{V}$ ,  $\omega = 377\text{rad/s}$  connected to a capacitor with capacitance  $C = 4.15\mu\text{F}$ .

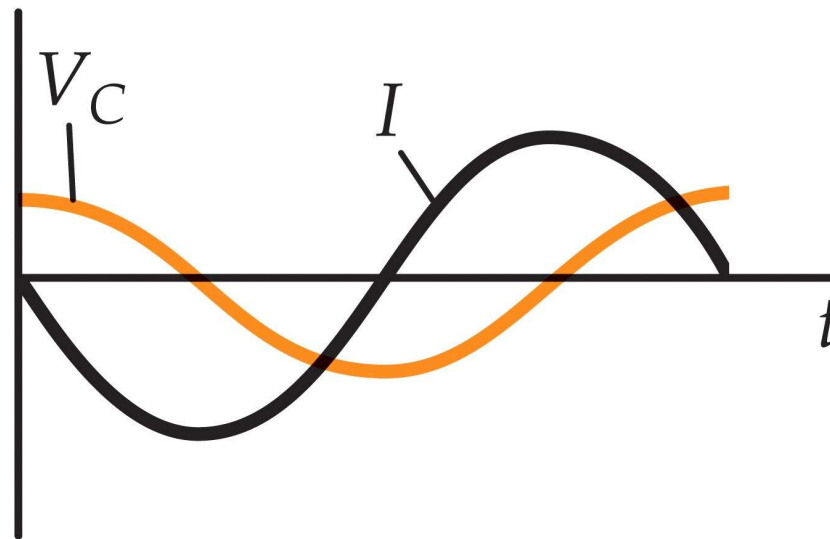- (a) Find the maximum value of the current.
- (b) Find the current when the emf is zero and decreasing.
- (c) Find the current when the emf is  $-12.5\text{V}$  and increasing.
- (d) Find the power supplied by the generator at the instant described in (c).



# RLC Series Circuit (1)



Applied alternating voltage:  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$

Resulting alternating current:  $I = I_{max} \cos(\omega t - \delta)$


Goals:

- Find  $I_{max}, \delta$  for given  $\mathcal{E}_{max}, \omega$ .
- Find voltages  $V_R, V_L, V_C$  across devices.

Loop rule:  $\mathcal{E} - V_R - V_C - V_L = 0$

Note:

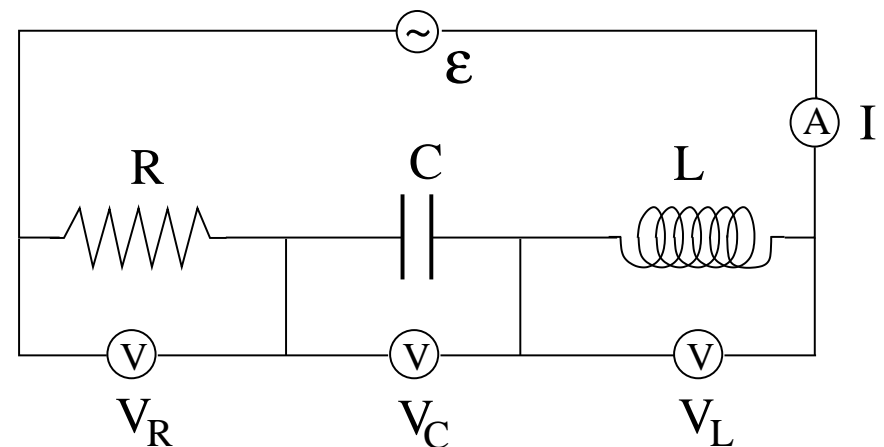- All voltages are time-dependent.
- In general, all voltages have a different phase.
- $V_R$  has the same phase as  $I$ .






## RLC Series Circuit (2)



Phasor diagram (for  $\omega t = \delta$ ):

Voltage amplitudes:

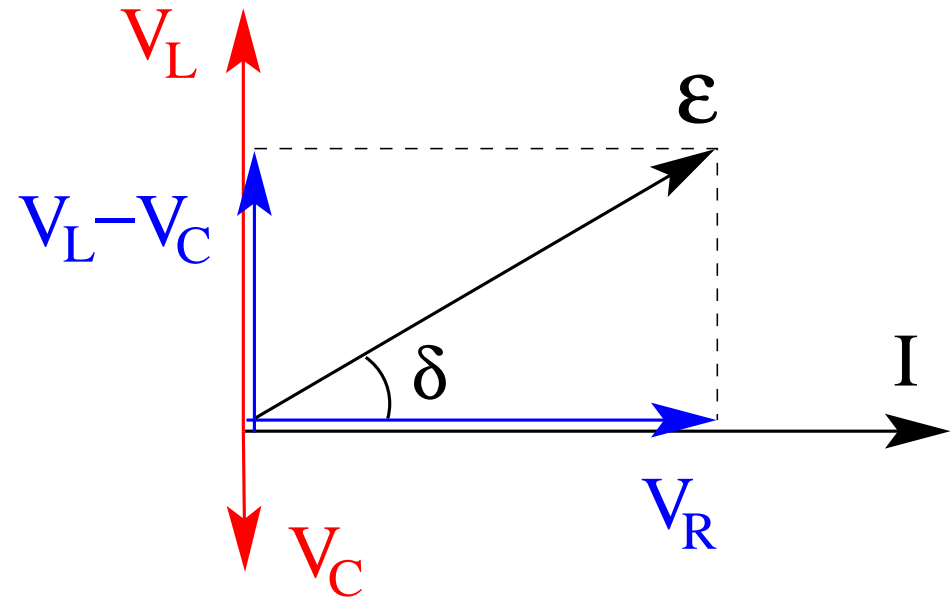- $V_{R,max} = I_{max}X_R = I_{max}R$
- $V_{L,max} = I_{max}X_L = I_{max}\omega L$
- $V_{C,max} = I_{max}X_C = \frac{I_{max}}{\omega C}$



Relation between  $\mathcal{E}_{max}$  and  $I_{max}$  from geometry:

$$\begin{aligned}\mathcal{E}_{max}^2 &= V_{R,max}^2 + (V_{L,max} - V_{C,max})^2 \\ &= I_{max}^2 \left[ R^2 + \left( \omega L - \frac{1}{\omega C} \right)^2 \right]\end{aligned}$$


# RLC Series Circuit (3)



Impedance:  $Z \equiv \frac{\mathcal{E}_{max}}{I_{max}} = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$

Current amplitude and phase angle:

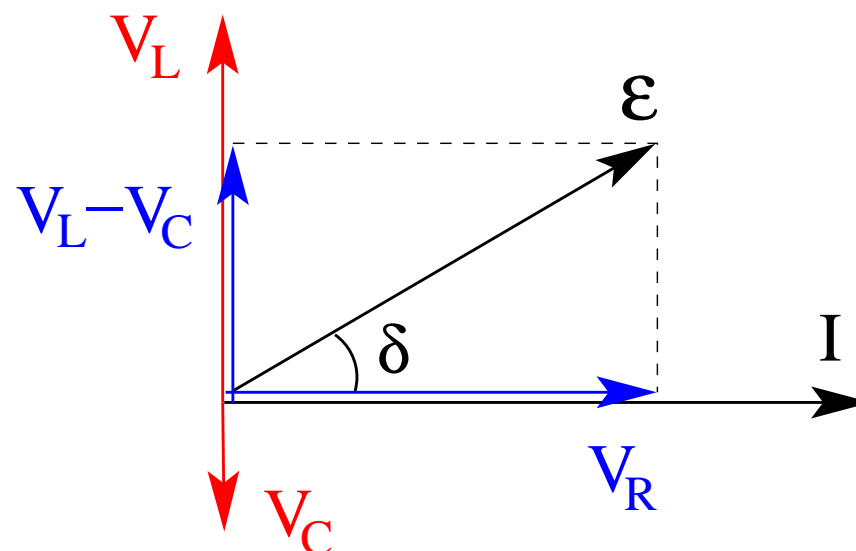- $I_{max} = \frac{\mathcal{E}_{max}}{Z} = \frac{\mathcal{E}_{max}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$
- $\tan \delta = \frac{V_{L,max} - V_{C,max}}{V_{R,max}} = \frac{\omega L - 1/\omega C}{R}$



Voltages across devices:

- $V_R = RI = RI_{max} \cos(\omega t - \delta) = V_{R,max} \cos(\omega t - \delta)$
- $V_L = L \frac{dI}{dt} = -\omega LI_{max} \sin(\omega t - \delta) = V_{L,max} \cos\left(\omega t - \delta + \frac{\pi}{2}\right)$
- $V_C = \frac{1}{C} \int I dt = \frac{I_{max}}{\omega C} \sin(\omega t - \delta) = V_{C,max} \cos\left(\omega t - \delta - \frac{\pi}{2}\right)$


# AC Circuit Application (1)



In this  $RLC$  circuit, the voltage amplitude is  $\mathcal{E}_{max} = 100\text{V}$ .

Find the impedance  $Z$ , the current amplitude  $I_{max}$ , and the voltage amplitudes  $V_R, V_C, V_L, V_{LC}$

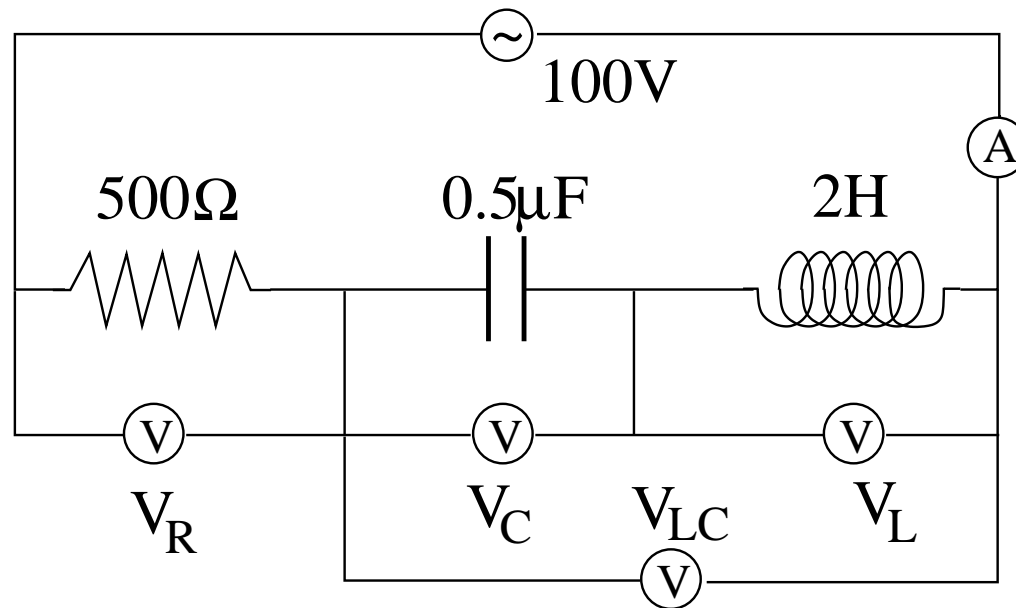- (a) for angular frequency is  $\omega = 1000\text{rad/s}$ ,
- (b) for angular frequency is  $\omega = 500\text{rad/s}$ .



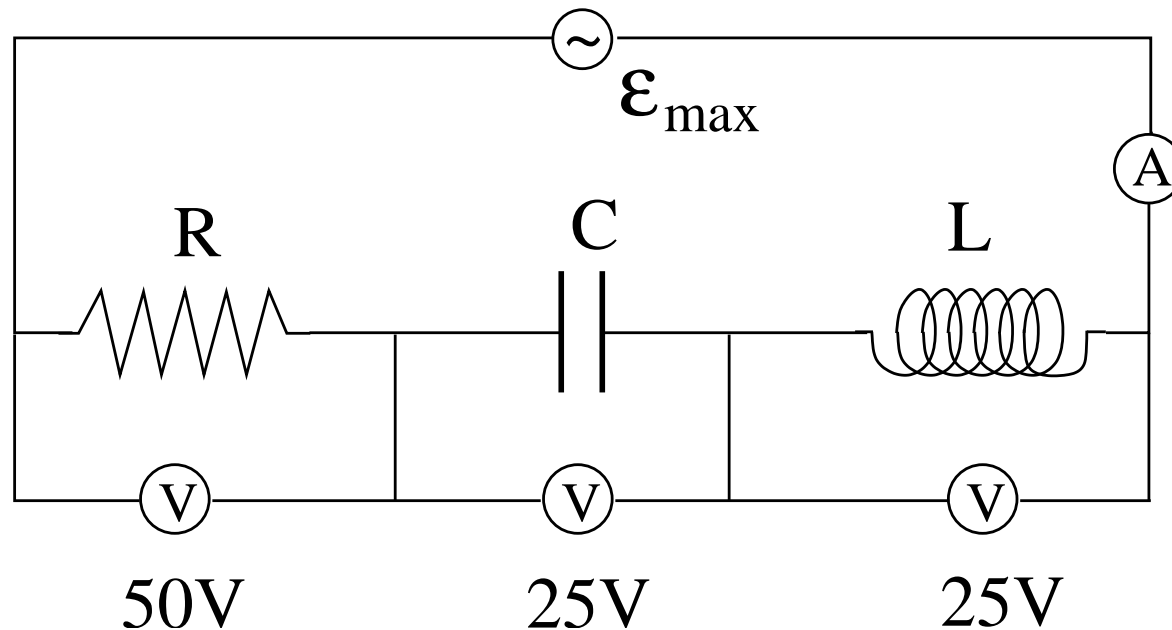
## AC Circuit Application (2)



In this  $RLC$  circuit, we know the voltage amplitudes  $V_R, V_C, V_L$  across each device, the current amplitude  $I_{max} = 5A$ , and the angular frequency  $\omega = 2\text{rad/s}$ .

- Find the device properties  $R, C, L$  and the voltage amplitude  $\mathcal{E}_{max}$  of the ac source.



# Impedances: RLC in Series (1)





$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

resonance at  $\omega_0 = \frac{1}{\sqrt{LC}}$

limit  $R \rightarrow 0$

$$Z = \left| \omega L - \frac{1}{\omega C} \right|$$

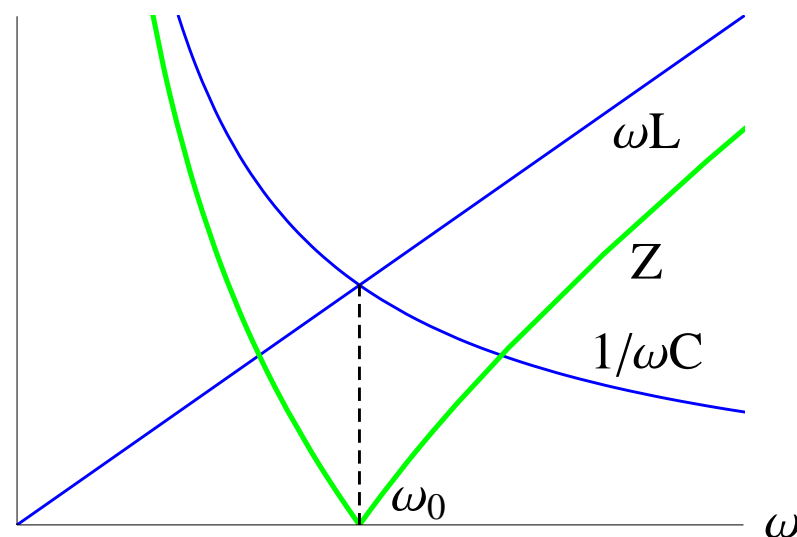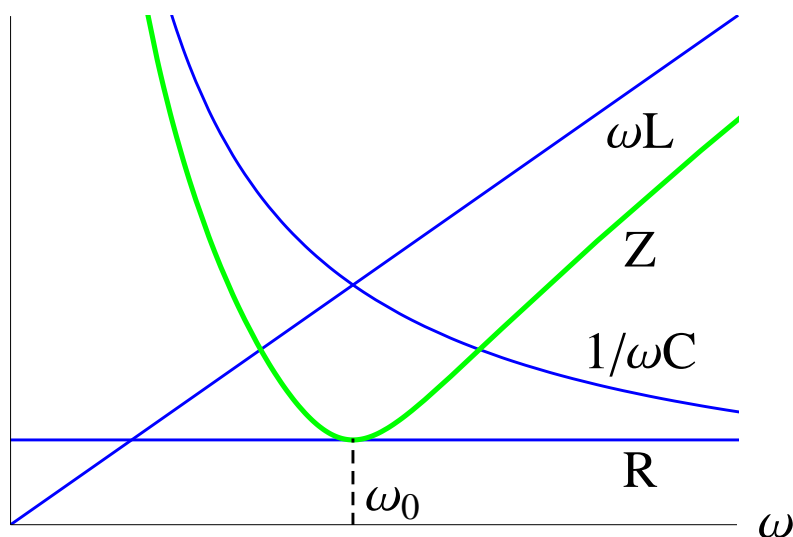


# Impedances: RLC in Series (2)




limit  $C \rightarrow \infty$

$$Z = \sqrt{R^2 + (\omega L)^2}$$


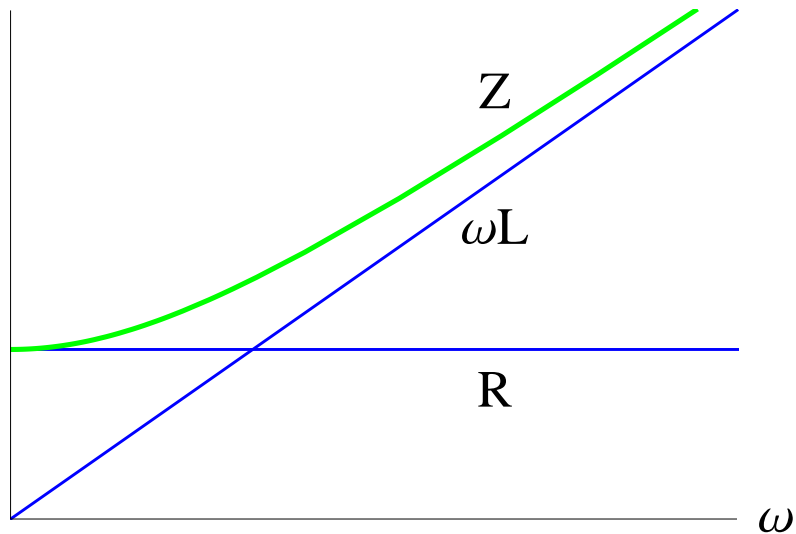


limit  $L \rightarrow 0$
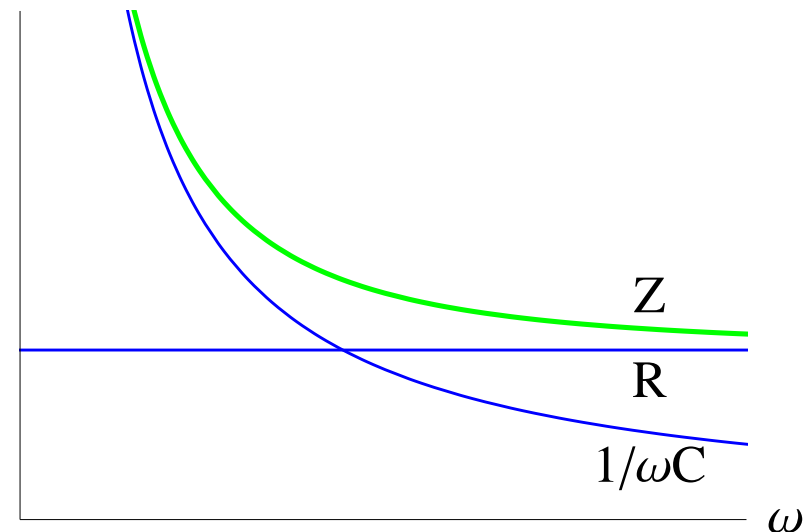
$$Z = \sqrt{R^2 + \frac{1}{(\omega C)^2}}$$



# Filters

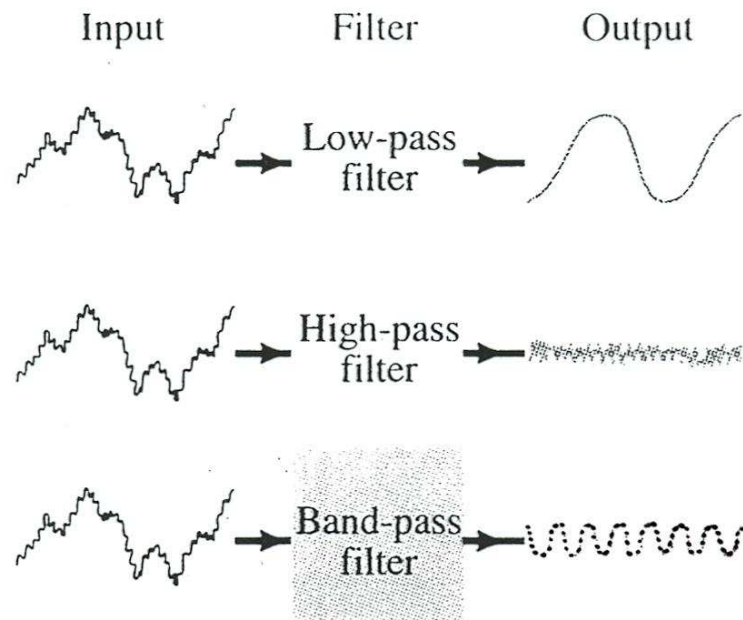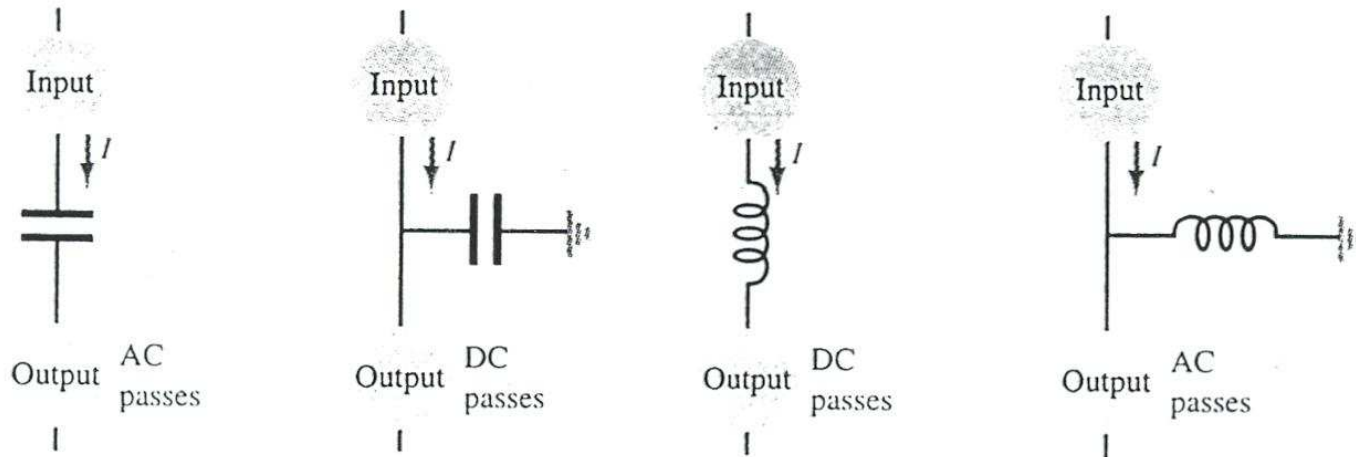

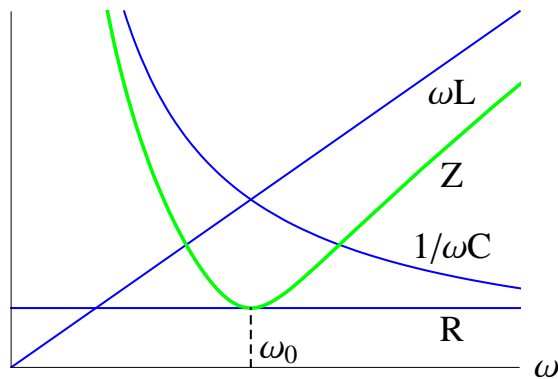
# RLC Series Resonance (1)




impedance

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$




current
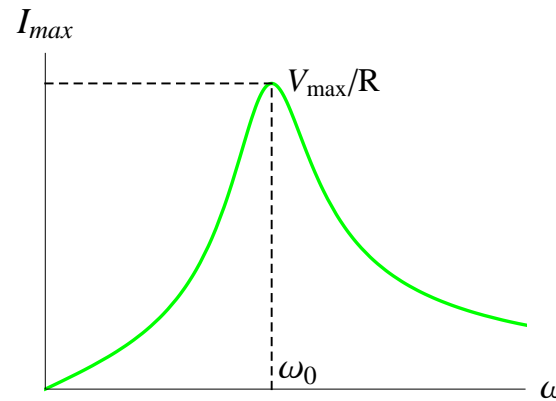
$$I_{max} = \frac{V_{max}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$



phase angle
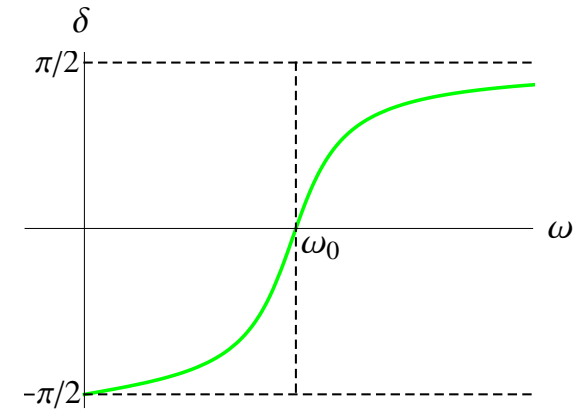
$$\delta = \frac{\omega L - 1/\omega C}{R}$$



resonance angular frequency:

$$\omega_0 = \frac{1}{\sqrt{LC}}$$




# RLC Series Resonance (2)




resistor

$$V_R^{max} = I_{max} R$$

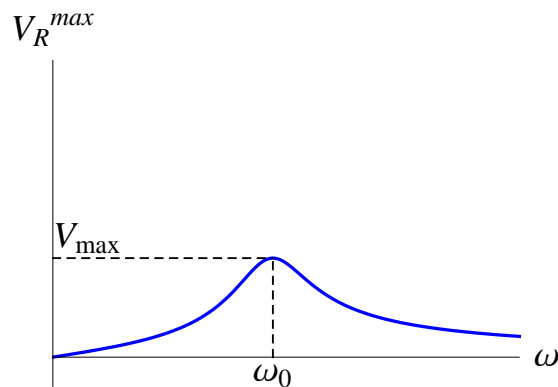


inductor

$$V_L^{max} = I_{max} \omega L$$

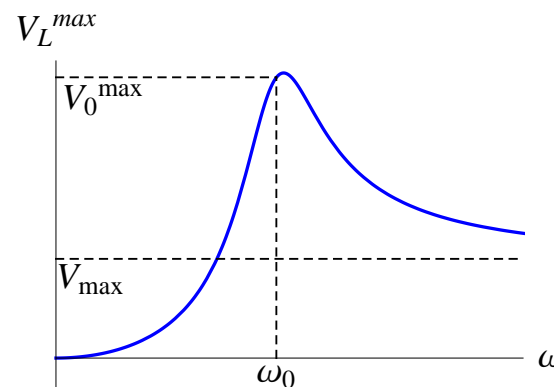

capacitor

$$V_C^{max} = I_{max} / \omega C$$

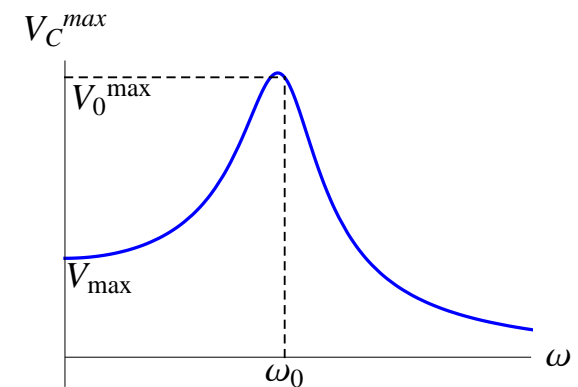

- relaxation times:  $\tau_{RC} = RC$ ,  $\tau_{RL} = L/R$

- angular frequencies:  $\omega_L = \frac{\omega_0}{\sqrt{1 - (\omega_0 \tau_{RC})^2/2}}$ ,  $\omega_C = \omega_0 \sqrt{1 - (\omega_0 \tau_{RC})^2/2}$

- voltages:  $V_0^{max} = V_{max} \omega_0 \tau_{RL}$ ,  $V_L^{max}(\omega_L) = V_C^{max}(\omega_C) = \frac{V_0^{max}}{\sqrt{1 - (\omega_0 \tau_{RC})^2/4}}$

# RLC Parallel Circuit (1)



Applied alternating voltage:  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$

Resulting alternating current:  $I = I_{max} \cos(\omega t - \delta)$


Goals:

- Find  $I_{max}, \delta$  for given  $\mathcal{E}_{max}, \omega$ .
- Find currents  $I_R, I_L, I_C$  through devices.

Junction rule:  $I = I_R + I_L + I_C$

Note:

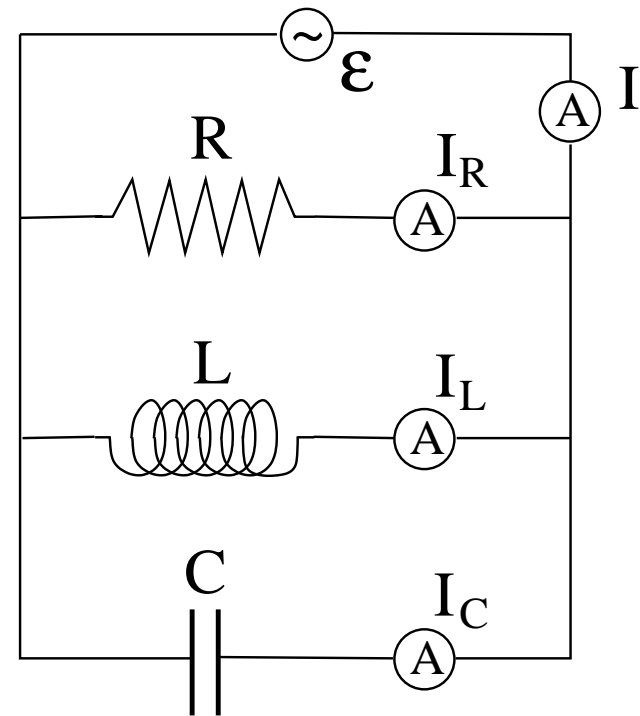- All currents are time-dependent.
- In general, each current has a different phase
- $I_R$  has the same phase as  $\mathcal{E}$ .




## RLC Parallel Circuit (2)



Phasor diagram (for  $\omega t = \delta$ ):

Current amplitudes:

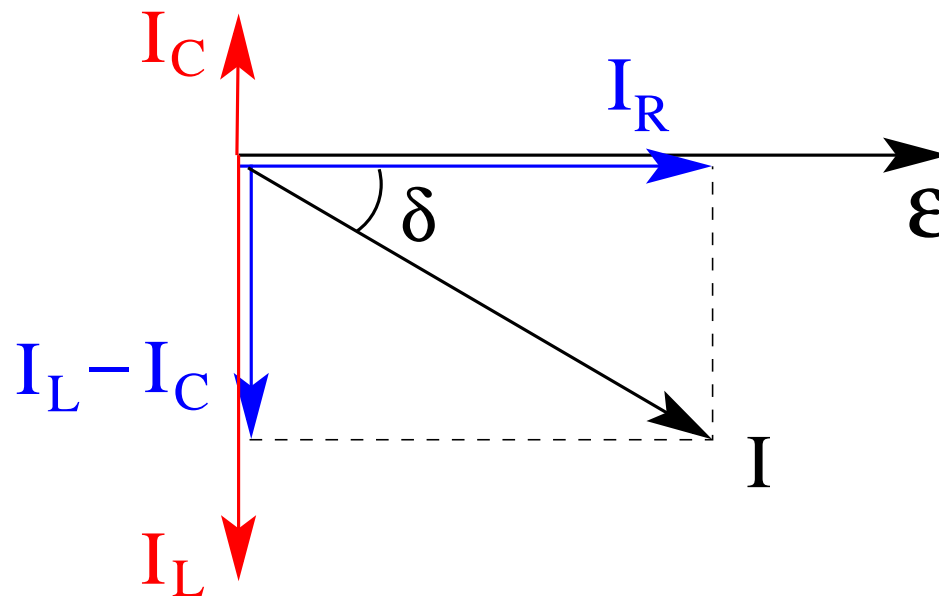- $I_{R,max} = \frac{\mathcal{E}_{max}}{X_R} = \frac{\mathcal{E}_{max}}{R}$
- $I_{L,max} = \frac{\mathcal{E}_{max}}{X_L} = \frac{\mathcal{E}_{max}}{\omega L}$
- $I_{C,max} = \frac{\mathcal{E}_{max}}{X_C} = \mathcal{E}_{max}\omega C$



Relation between  $\mathcal{E}_{max}$  and  $I_{max}$  from geometry:

$$\begin{aligned} I_{max}^2 &= I_{R,max}^2 + (I_{L,max} - I_{C,max})^2 \\ &= \mathcal{E}_{max}^2 \left[ \frac{1}{R^2} + \left( \frac{1}{\omega L} - \omega C \right)^2 \right] \end{aligned}$$


# RLC Parallel Circuit (3)



Impedance:  $\frac{1}{Z} \equiv \frac{I_{max}}{\mathcal{E}_{max}} = \sqrt{\frac{1}{R^2} + \left(\frac{1}{\omega L} - \omega C\right)^2}$

Current amplitude and phase angle:

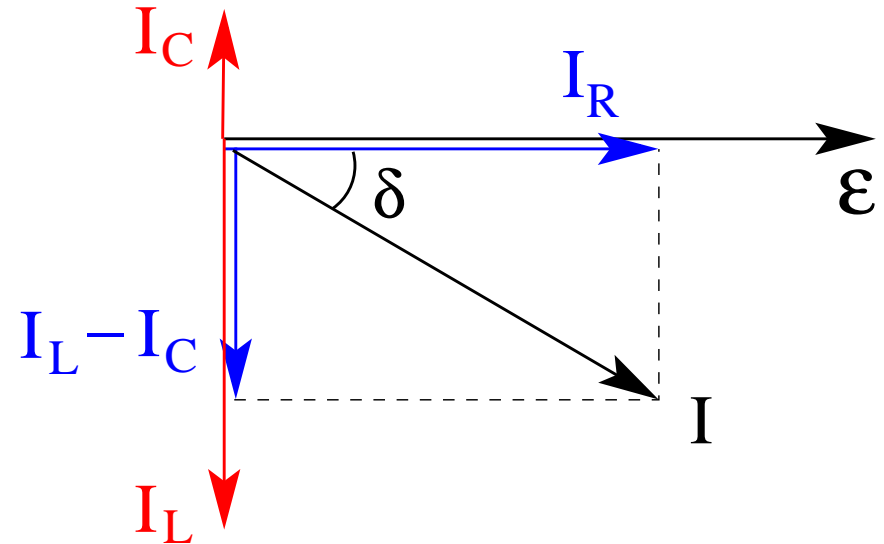- $I_{max} = \frac{\mathcal{E}_{max}}{Z} = \mathcal{E}_{max} \sqrt{\frac{1}{R^2} + \left(\frac{1}{\omega L} - \omega C\right)^2}$
- $\tan \delta = \frac{I_{L,max} - I_{C,max}}{I_{R,max}} = \frac{1/\omega L - \omega C}{1/R}$



Currents through devices:


- $I_R = \frac{\mathcal{E}}{R} = \frac{\mathcal{E}_{max}}{R} \cos(\omega t) = I_{R,max} \cos(\omega t)$
- $I_L = \frac{1}{L} \int \mathcal{E} dt = \frac{\mathcal{E}_{max}}{\omega L} \sin(\omega t) = I_{L,max} \cos\left(\omega t - \frac{\pi}{2}\right)$
- $I_C = C \frac{d\mathcal{E}}{dt} = -\omega C \mathcal{E}_{max} \sin(\omega t) = I_{C,max} \cos\left(\omega t + \frac{\pi}{2}\right)$

# AC Circuit Application (3)



Find the current amplitudes  $I_1, I_2, I_3$

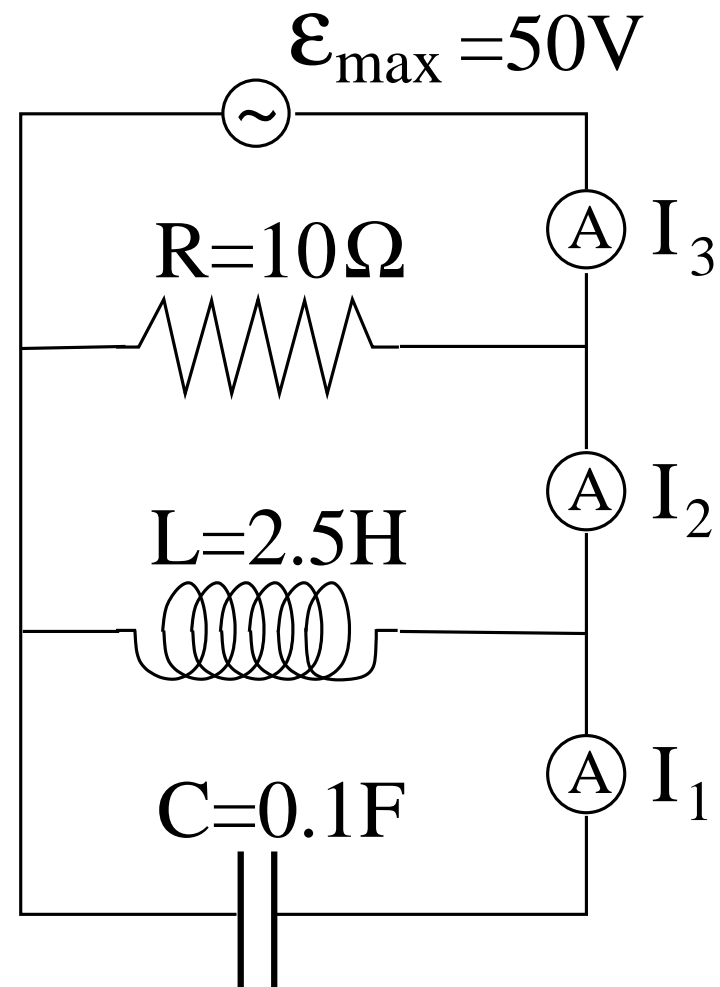
- (a) for angular frequency  $\omega = 2\text{rad/s}$ ,
- (b) for angular frequency  $\omega = 4\text{rad/s}$ .


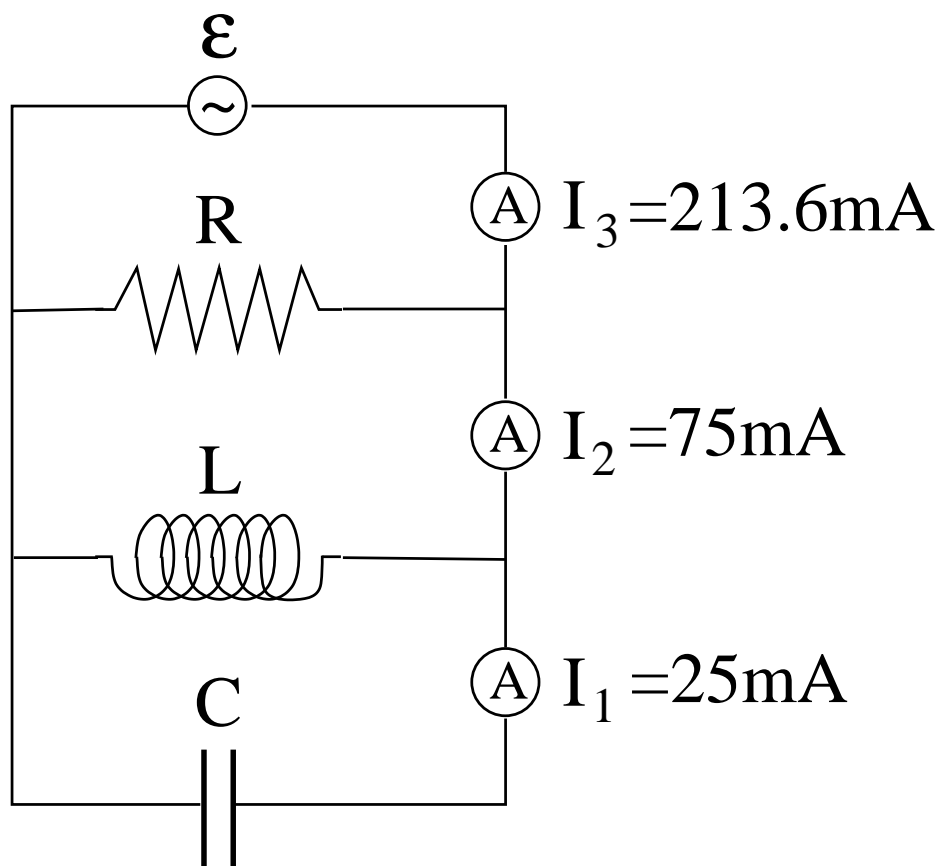
## AC Circuit Application (4)



Given the current amplitudes  $I_1, I_2, I_3$  through the three branches of this  $RLC$  circuit, and given the amplitude  $\mathcal{E}_{max} = 100\text{V}$  and angular frequency  $\omega = 500\text{rad/s}$  of the ac source, find the device properties  $R, L, C$ .



# Impedances: RLC in Parallel (1)





$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}$$

resonance at  $\omega_0 = \frac{1}{\sqrt{LC}}$

limit  $R \rightarrow \infty$

$$\frac{1}{Z} = \left| \omega C - \frac{1}{\omega L} \right|$$

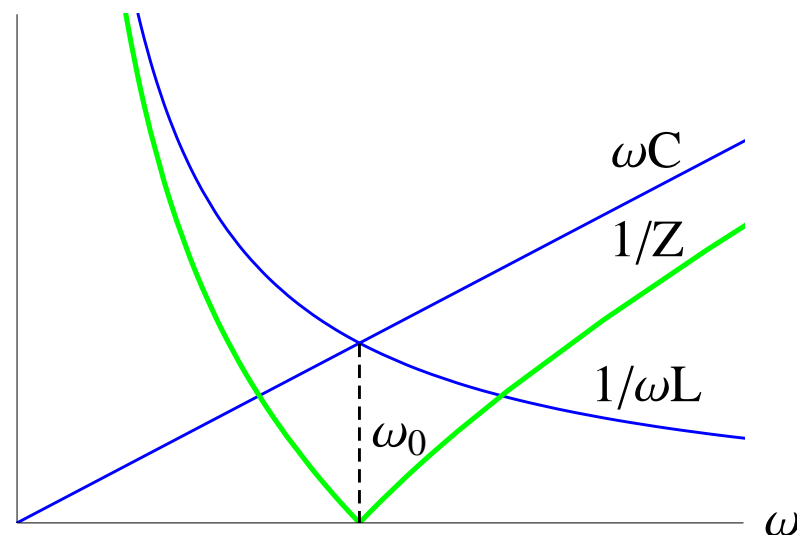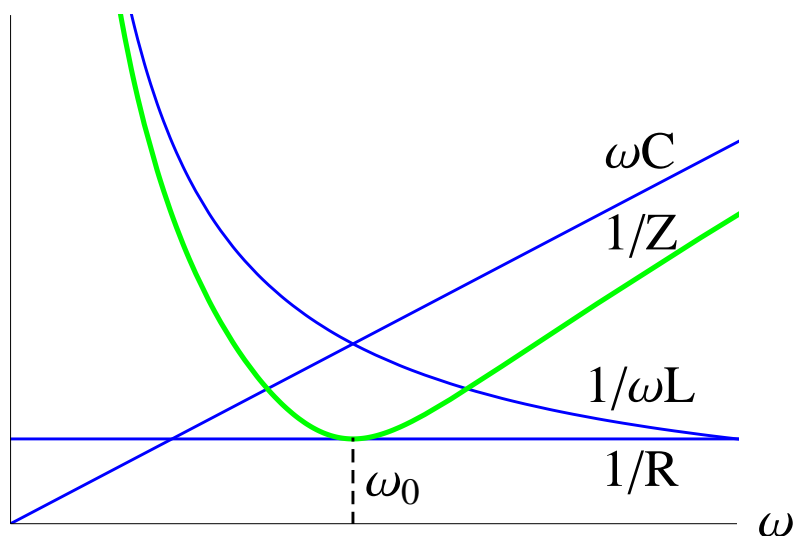

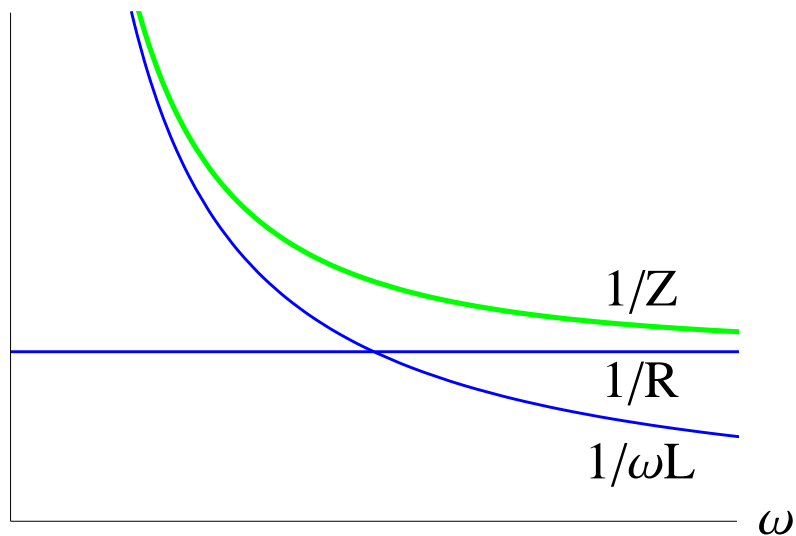
# Impedances: RLC in Parallel (2)




limit  $C \rightarrow 0$

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \frac{1}{(\omega L)^2}}$$



limit  $L \rightarrow \infty$
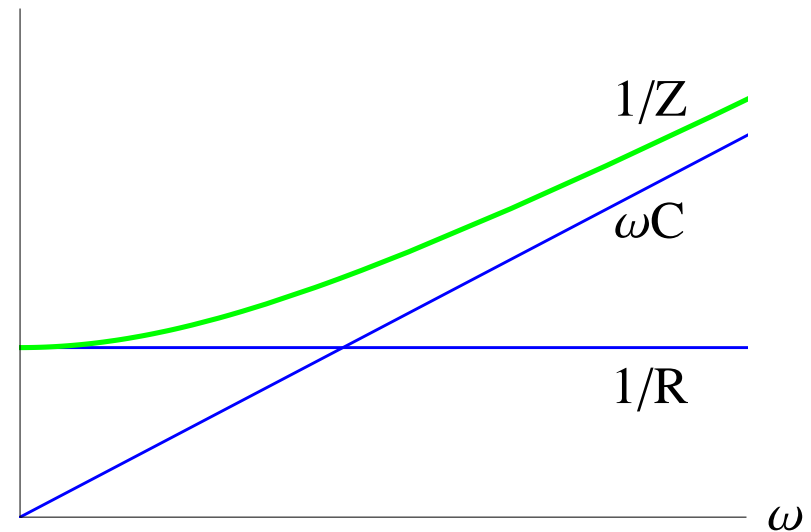
$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + (\omega C)^2}$$





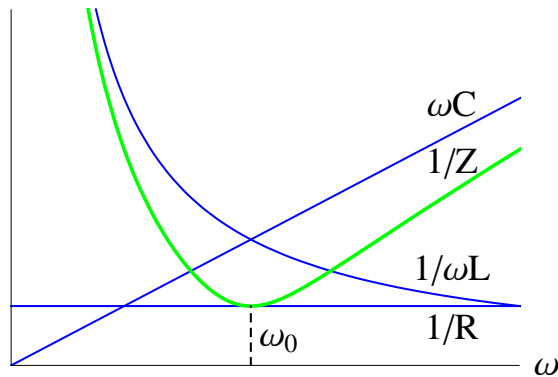
# RLC Parallel Resonance (1)




impedance

$$\frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}$$




current

$$I_{max} = \frac{V_{max}}{Z}$$

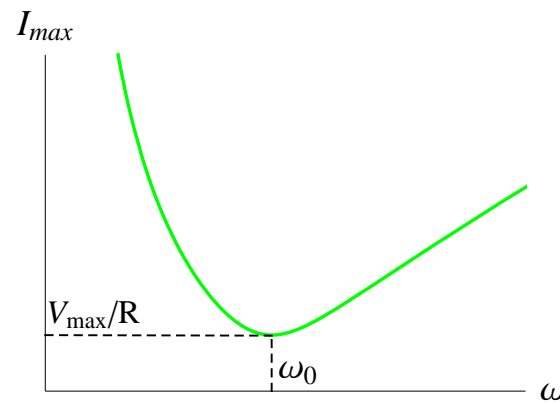

phase angle
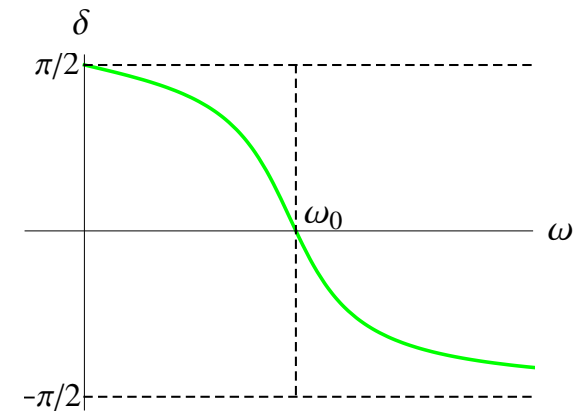
$$\delta = \frac{1/\omega L - \omega C}{1/R}$$



resonance angular frequency:


$$\omega_0 = \frac{1}{\sqrt{LC}}$$

# RLC Parallel Resonance (2)




resistor

$$I_R^{max} = V_{max}/R$$

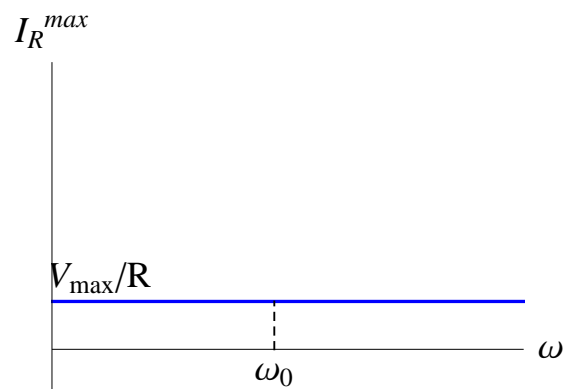


inductor

$$I_L^{max} = V_{max}/\omega L$$

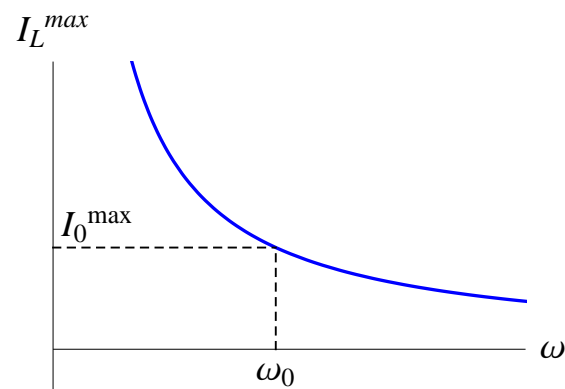

capacitor

$$I_C^{max} = V_{max} \omega C$$

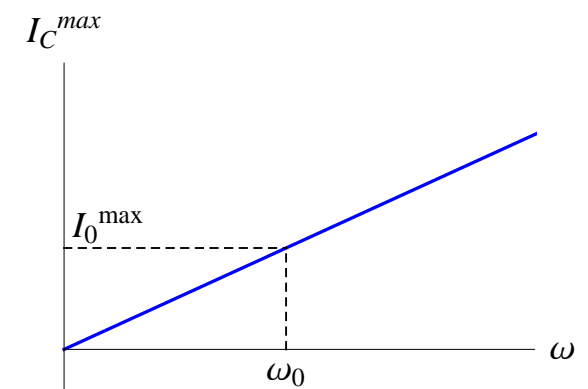

currents at resonance:

$$I_R^{max} = \frac{V_{max}}{R}, \quad I_L^{max} = I_C^{max} = I_0^{max} = V_{max} \sqrt{\frac{C}{L}}$$

# Power in AC Circuits



Voltage of ac source:  $\mathcal{E} = \mathcal{E}_{max} \cos \omega t$

Current through circuit:  $I = I_{max} \cos(\omega t - \delta)$

Instantaneous power supplied:  $P(t) = \mathcal{E}(t)I(t) = [\mathcal{E}_{max} \cos \omega t][I_{max} \cos(\omega t - \delta)]$



Use  $\cos(\omega t - \delta) = \cos \omega t \cos \delta + \sin \omega t \sin \delta$

$$\Rightarrow P(t) = \mathcal{E}_{max} I_{max} [\cos^2 \omega t \cos \delta + \cos \omega t \sin \omega t \sin \delta]$$

Time averages:  $[\cos^2 \omega t]_{AV} = \frac{1}{2}$ ,  $[\cos \omega t \sin \omega t]_{AV} = 0$

Average power supplied by source:  $P_{AV} = \frac{1}{2} \mathcal{E}_{max} I_{max} \cos \delta = \mathcal{E}_{rms} I_{rms} \cos \delta$

Power factor:  $\cos \delta$

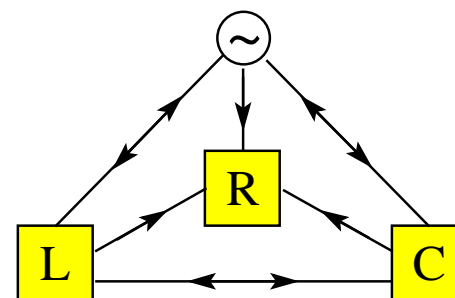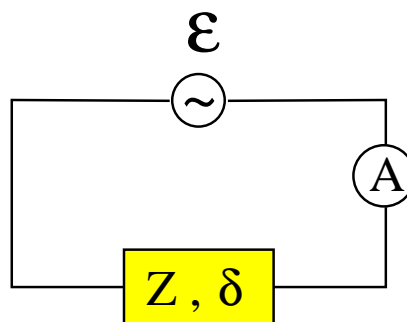

# Transformer



- Primary winding:  $N_1$  turns


$$V_1(t) = V_1^{(rms)} \cos(\omega t), \quad I_1(t) = I_1^{(rms)} \cos(\omega t - \delta_1)$$

- Secondary winding:  $N_2$  turns

$$V_2(t) = V_2^{(rms)} \cos(\omega t), \quad I_2(t) = I_2^{(rms)} \cos(\omega t - \delta_2)$$

- Voltage amplitude ratio:  $\frac{V_1^{(rms)}}{V_2^{(rms)}} = \frac{N_1}{N_2}$




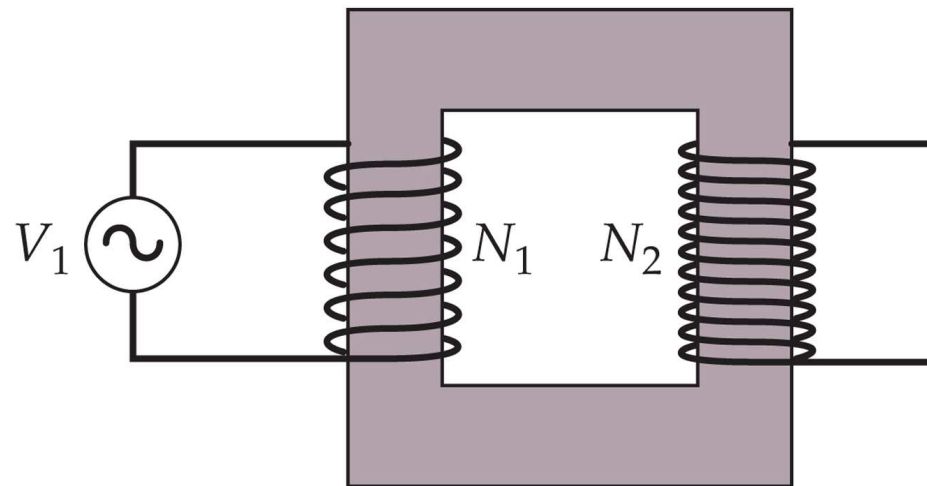
- Power transfer:  $V_1^{(rms)} I_1^{(rms)} \cos \delta_1 = V_2^{(rms)} I_2^{(rms)} \cos \delta_2$


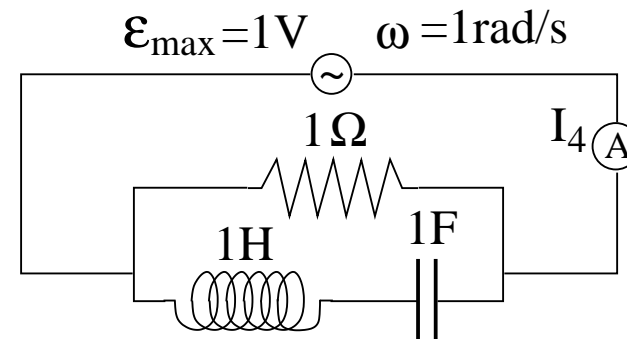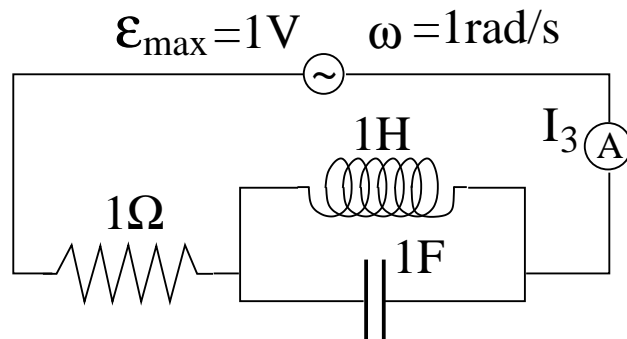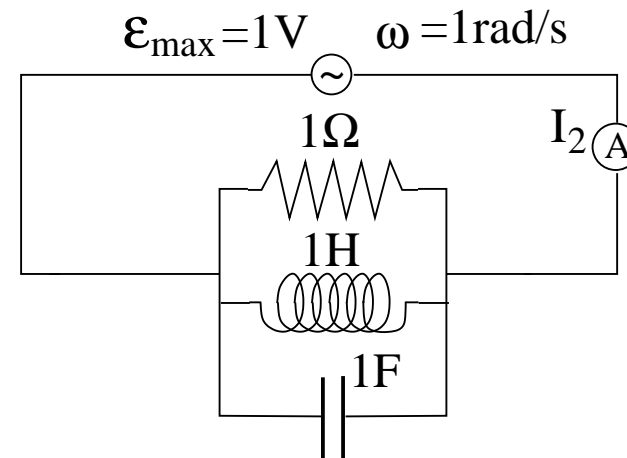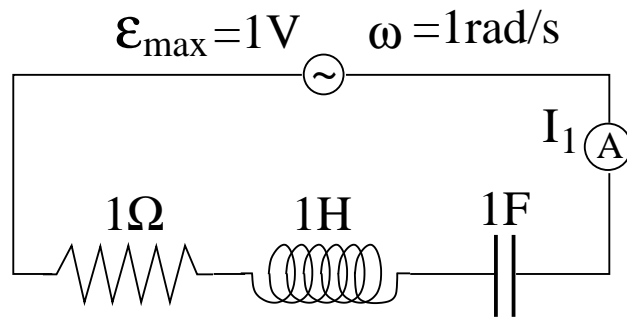
# AC Circuit Application (5)



Find the current amplitudes  $I_1, I_2, I_3, I_4$  in the four  $RLC$  circuits shown.



## AC Circuit Application (6)



Consider an  $RLC$  series circuit with inductance  $L = 88\text{mH}$ , capacitance  $C = 0.94\mu\text{F}$ , and unknown resistance  $R$ .

The ac generator  $\mathcal{E} = \mathcal{E}_{max} \sin(\omega t)$  has amplitude  $\mathcal{E}_{max} = 24\text{V}$  and frequency  $f = 930\text{Hz}$ . The phase angle is  $\delta = 75^\circ$ .



- (a) Find the resistance  $R$ .
- (b) Find the current amplitude  $I_{max}$ .
- (c) Find the maximum energy  $U_L^{max}$  stored in the inductor.
- (d) Find the maximum energy  $U_C^{max}$  stored in the capacitor.
- (e) Find the time  $t_1$  at which the current has its maximum value  $I_{max}$ .
- (f) Find the time  $t_2$  at which the charge on the capacitor has its maximum value  $Q_{max}$ .

# AC Circuit Application (7)



Consider the two ac circuits shown.

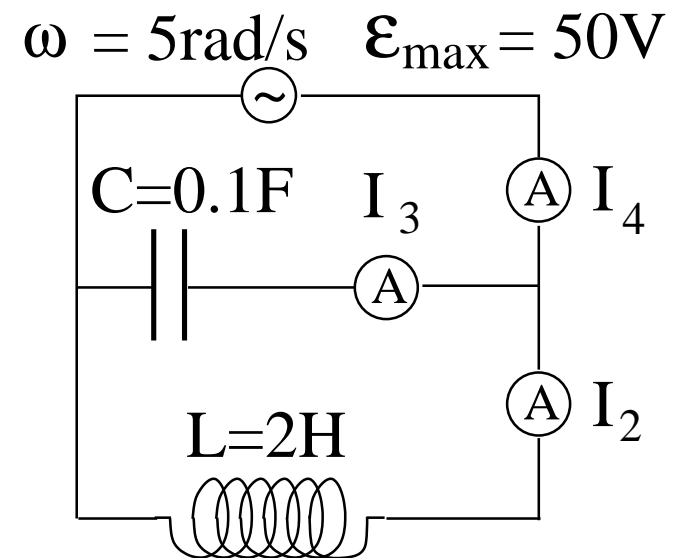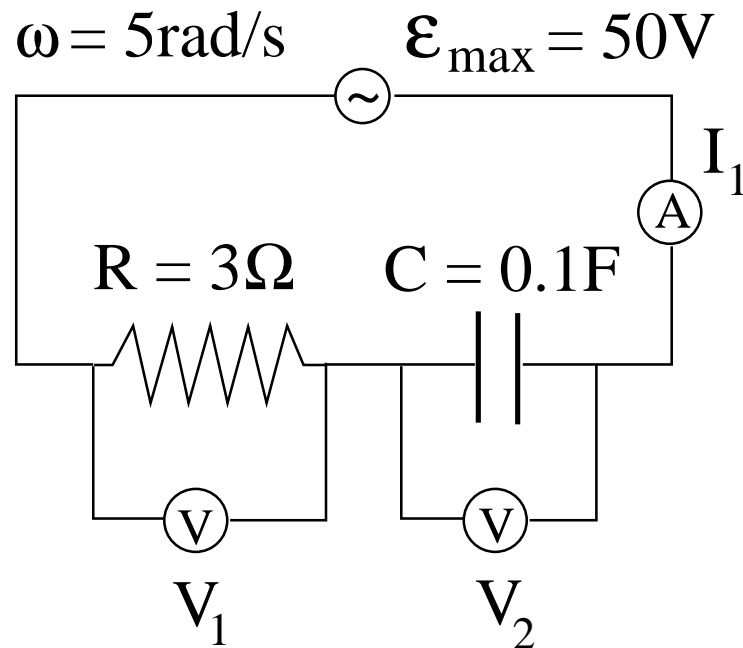- (a) In the circuit on the left, determine the current amplitude  $I_1$  and the voltage amplitudes  $V_1$  and  $V_2$ .
- (b) In the circuit on the right, determine the current amplitudes  $I_2$ ,  $I_3$ , and  $I_4$ .





# AC Circuit Application (8)



Consider the two ac circuits shown.

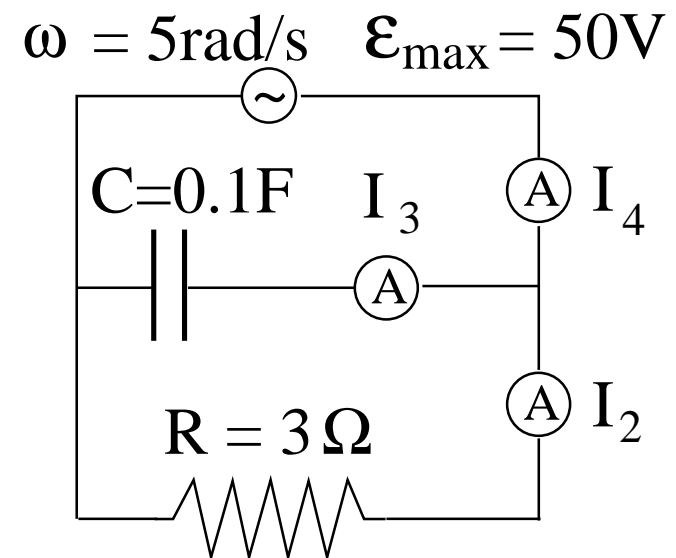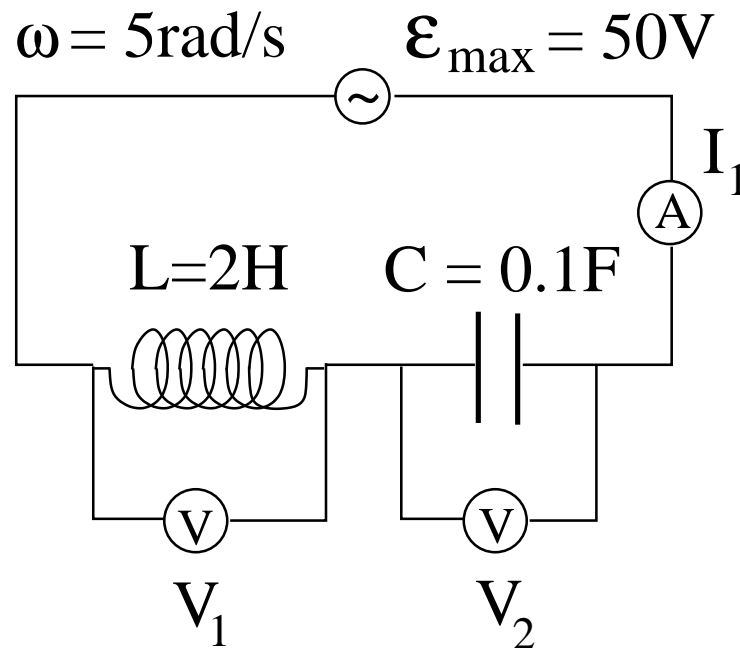- (a) In the circuit on the left, determine the maximum value of current  $I_1$  and the maximum value of voltages  $V_1$  and  $V_2$ .
- (b) In the circuit on the right, determine the maximum value of currents  $I_2$ ,  $I_3$ , and  $I_4$ .







# AC Circuit Application (9)



In the two ac circuits shown the ammeter and voltmeter readings are rms values.

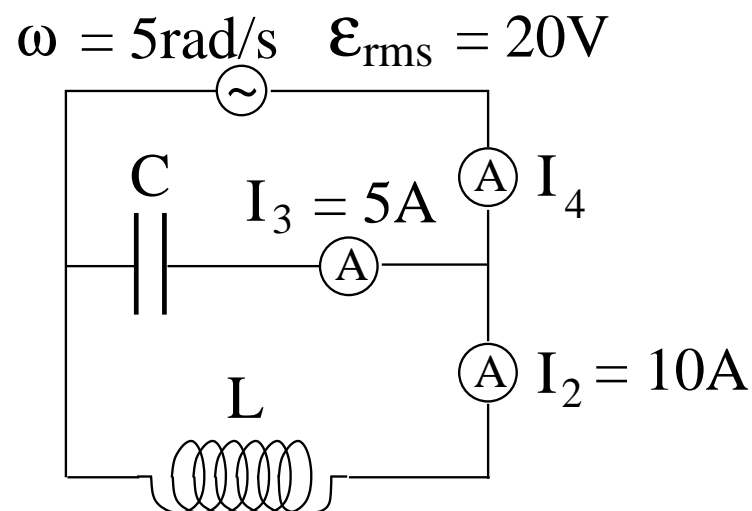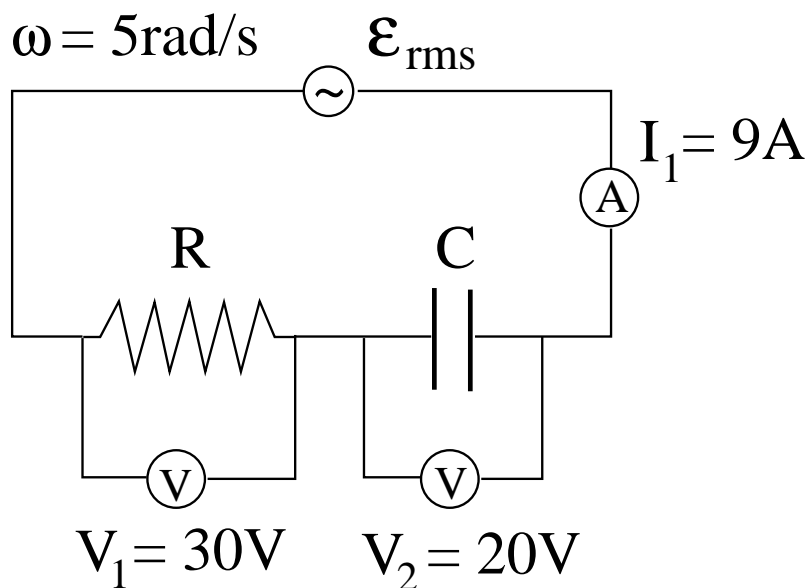- (a) In the circuit on the left, find the resistance  $R$  of the resistor, the capacitance  $C$  of the capacitor, the impedance  $Z$  of the two devices combined, and the voltage  $\mathcal{E}_{rms}$  of the power source.
- (b) In the circuit on the right, find the capacitance  $C$  of the capacitor, the inductance  $L$  of the inductor, the impedance  $Z$  of the two devices combined, and the rms value of the current  $I_4$ .



# AC Circuit Application (10)



In the two ac circuits shown the ammeter and voltmeter readings are rms values.

- (a) In the circuit on the left, find the capacitance  $C$  of the capacitor, the inductance  $L$  of the inductor, the impedance  $Z$  of the two devices combined, and the voltage  $\mathcal{E}_{rms}$  of the power source.
- (b) In the circuit on the right, find the capacitance  $C$  of the capacitor, the resistance  $R$  of the resistor, the impedance  $Z$  of the two devices combined, and the rms value of the current  $I_4$ .

