

Capacitor with Dielectric






Most capacitors have a dielectric (insulating solid or liquid material) in the space between the conductors. This has several advantages:

- Physical separation of the conductors.
- Prevention of dielectric breakdown.
- Enhancement of capacitance.

The dielectric is polarized by the electric field between the capacitor plates.

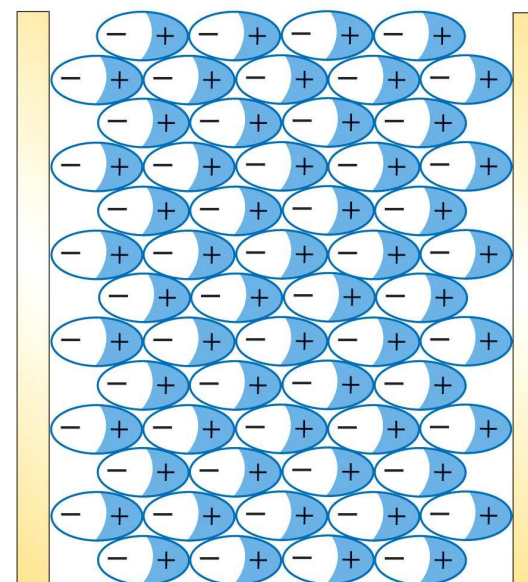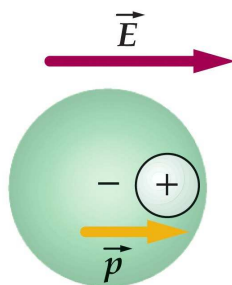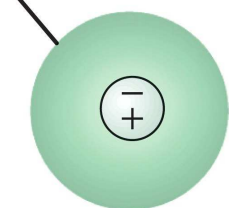
Center of negative charge
coincides with center of
positive charge



Parallel-Plate Capacitor with Dielectric (1)



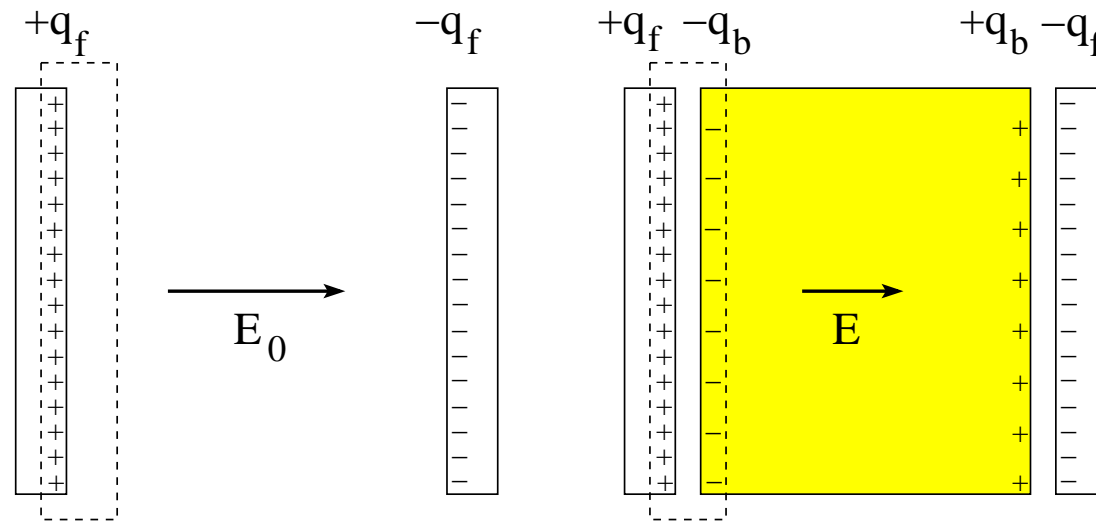The polarization produces a bound charge on the surface of the dielectric.




The bound surface charge has the effect of reducing the electric field between the plates from \vec{E}_0 to \vec{E} .

- A : area of plates
- d : separation between plates
- $\pm q_f$: free charge on plate
- $\pm q_b$: bound charge on surface of dielectric
- \vec{E}_0 : electric field in vacuum
- \vec{E} : electric field in dielectric

Parallel-Plate Capacitor with Dielectric (2)



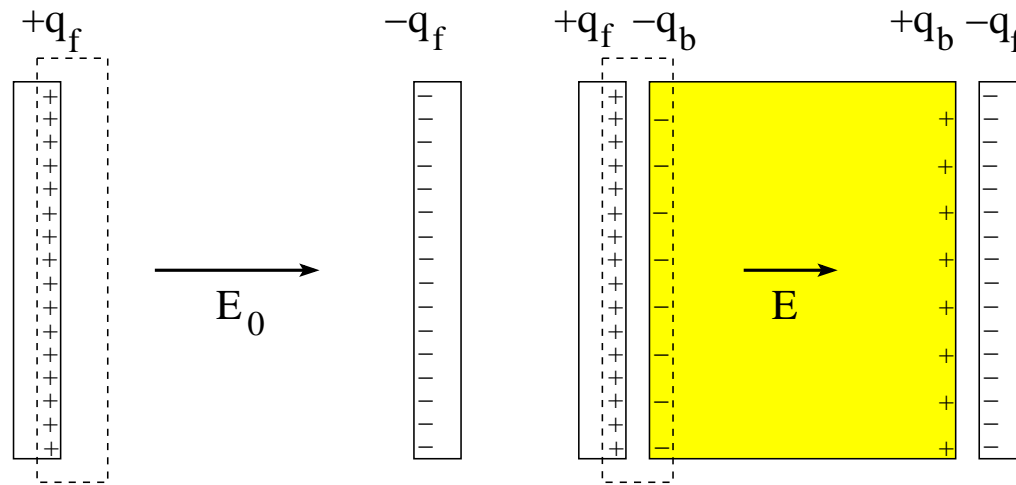Use Gauss' law to determine the electric fields \vec{E}_0 and \vec{E} .



- Field in vacuum: $E_0 A = \frac{q_f}{\epsilon_0} \Rightarrow E_0 = \frac{q_f}{\epsilon_0 A}$
- Field in dielectric: $E A = \frac{q_f - q_b}{\epsilon_0} \Rightarrow E = \frac{q_f - q_b}{\epsilon_0 A} < E_0$
- Voltage: $V_0 = E_0 d$ (vacuum), $V = E d = \frac{V_0}{\kappa} < V_0$ (dielectric)

Dielectric constant: $\kappa \equiv \frac{E_0}{E} = \frac{q_f}{q_f - q_b} > 1$. Permittivity of dielectric: $\epsilon = \kappa \epsilon_0$.



TABLE 24-1

Dielectric Constants and Dielectric Strengths of Various Materials

Material	Dielectric Constant κ	Dielectric Strength, kV/mm
Air	1.00059	3
Bakelite	4.9	24
Glass (Pyrex)	5.6	14
Mica	5.4	10–100
Neoprene	6.9	12
Paper	3.7	16
Paraffin	2.1–2.5	10
Plexiglas	3.4	40
Polystyrene	2.55	24
Porcelain	7	5.7
Transformer oil	2.24	12

- Dielectrics increase the capacitance: $C/C_0 = \kappa$.
- The capacitor is discharged spontaneously across the dielectric if the electric field exceeds the value quoted as dielectric strength.

Impact of Dielectric (1)



What happens when a dielectric is placed into a capacitor with the charge on the capacitor kept constant?

	vacuum	dielectric
charge	Q_0	$Q = Q_0$
electric field	E_0	$E = \frac{E_0}{\kappa} < E_0$
voltage	V_0	$V = \frac{V_0}{\kappa} < V_0$
capacitance	$C_0 = \frac{Q_0}{V_0}$	$C = \frac{Q}{V} = \kappa C_0 > C_0$
potential energy	$U_0 = \frac{Q_0^2}{2C_0}$	$U = \frac{Q^2}{2C} = \frac{U_0}{\kappa} < U_0$
energy density	$u_E^{(0)} = \frac{1}{2} \epsilon_0 E_0^2$	$u_E = \frac{u_E^{(0)}}{\kappa} = \frac{1}{2} \kappa \epsilon_0 E^2 < u_E^{(0)}$

Impact of Dielectric (2)



What happens when a dielectric is placed into a capacitor with the voltage across the capacitor kept constant?

	vacuum	dielectric
charge	Q_0	$Q = \kappa Q_0$
electric field	E_0	$E = E_0$
voltage	V_0	$V = V_0$
capacitance	$C_0 = \frac{Q_0}{V_0}$	$C = \frac{Q}{V} = \kappa C_0 > C_0$
potential energy	$U_0 = \frac{1}{2} C_0 V_0^2$	$U = \frac{1}{2} C V^2 = \kappa U_0 > U_0$
energy density	$u_E^{(0)} = \frac{1}{2} \epsilon_0 E_0^2$	$u_E = \kappa u_E^{(0)} = \frac{1}{2} \kappa \epsilon_0 E^2 > u_E^{(0)}$

Stacked Dielectrics



Consider a parallel-plate capacitor with area A of each plate and spacing d .

- Capacitance without dielectric: $C_0 = \frac{\epsilon_0 A}{d}$.
- Dielectrics stacked in parallel: $C = C_1 + C_2$



with $C_1 = \kappa_1 \epsilon_0 \frac{A/2}{d}$, $C_2 = \kappa_2 \epsilon_0 \frac{A/2}{d}$.

$\Rightarrow C = \frac{1}{2}(\kappa_1 + \kappa_2)C_0$.

- Dielectrics stacked in series: $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2}$

with $C_1 = \kappa_1 \epsilon_0 \frac{A}{d/2}$, $C_2 = \kappa_2 \epsilon_0 \frac{A}{d/2}$

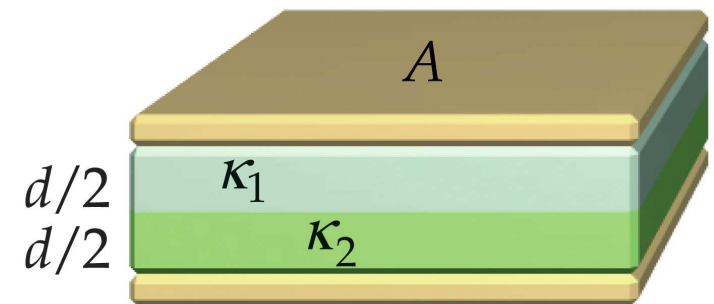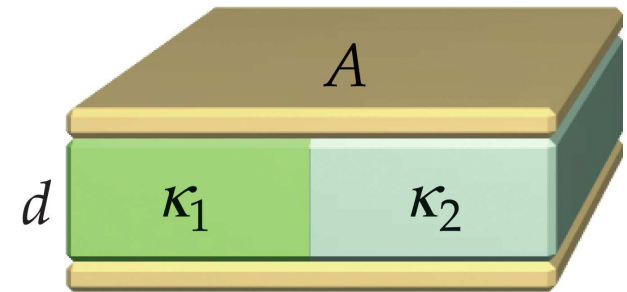$\Rightarrow C = \frac{2\kappa_1\kappa_2}{\kappa_1 + \kappa_2} C_0$.



Lateral Force on Dielectric




Consider two charged capacitors with dielectrics only halfway between the plates.

In configuration (a) any lateral motion of the dielectric takes place at **constant voltage** across the plates.

In configuration (b) any lateral motion of the dielectric takes place at **constant charge** on the plates.

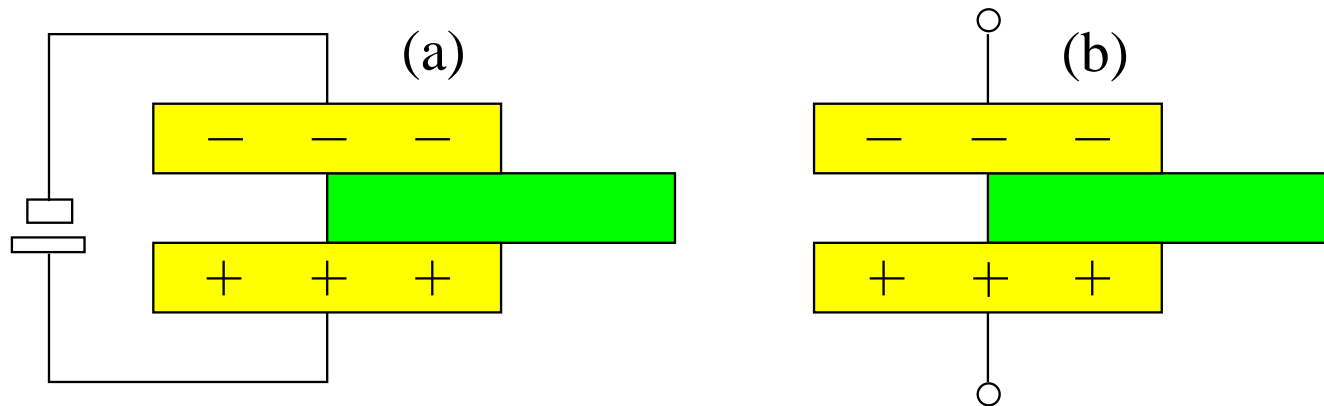Determine in each case the direction (left/zero/right) of the lateral force experienced by the dielectric.




Geiger Counter



Radioactive atomic nuclei produce high-energy particles of three different kinds:

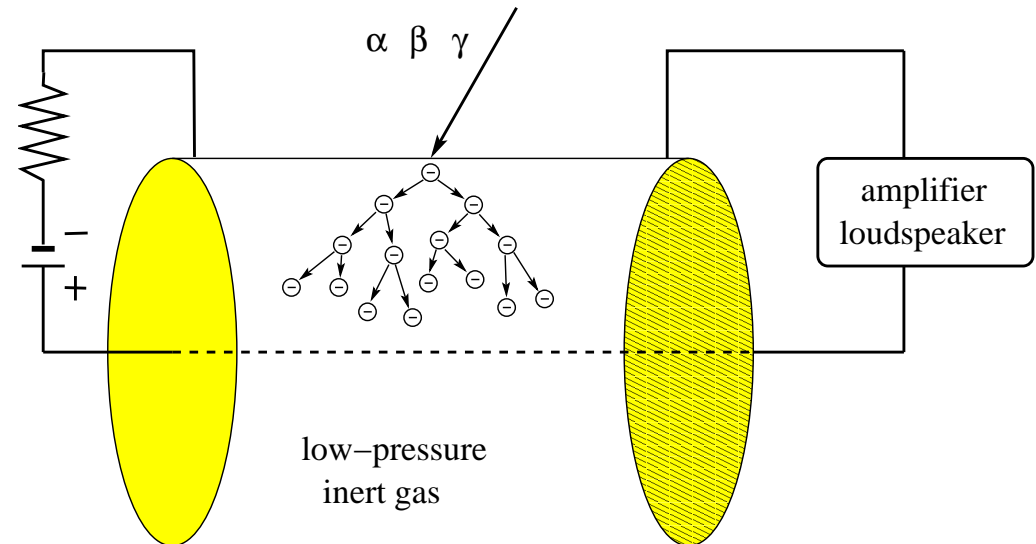- α -particles are ${}^4\text{He}$ nuclei.
- β -particles are electrons or positrons.
- γ -particles are high-energy photons.




- Free electrons produced by ionizing radiation are strongly accelerated toward the central wire.
- Collisions with gas atoms produce further free electrons, which are accelerated in the same direction.
- An avalanche of electrons reaching the wire produces a current pulse in the circuit.

Intermediate Exam II: Problem #1 (Spring '05)



The circuit of capacitors connected to a battery is at equilibrium.

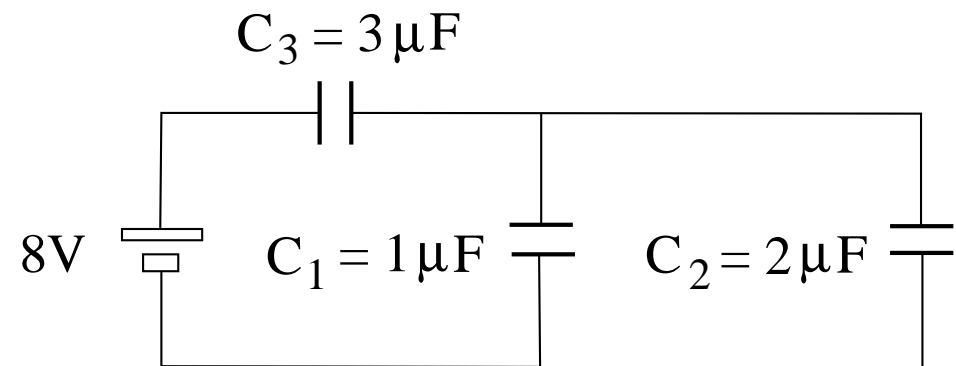- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the voltage V_3 across capacitor C_3 .
- (c) Find the charge Q_2 on capacitor C_2 .




Intermediate Exam II: Problem #1 (Spring '05)



The circuit of capacitors connected to a battery is at equilibrium.

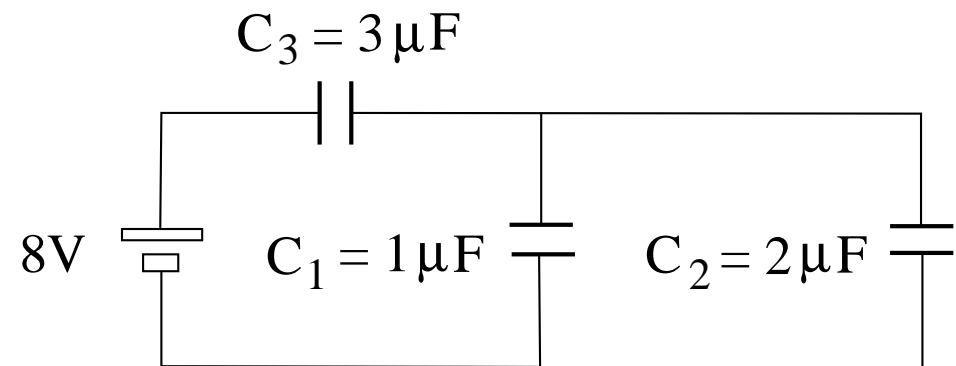- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the voltage V_3 across capacitor C_3 .
- (c) Find the charge Q_2 on capacitor C_2 .



Solution:


(a) $C_{12} = C_1 + C_2 = 3\mu\text{F}$, $C_{eq} = \left(\frac{1}{C_{12}} + \frac{1}{C_3} \right)^{-1} = 1.5\mu\text{F}$.

Intermediate Exam II: Problem #1 (Spring '05)



The circuit of capacitors connected to a battery is at equilibrium.

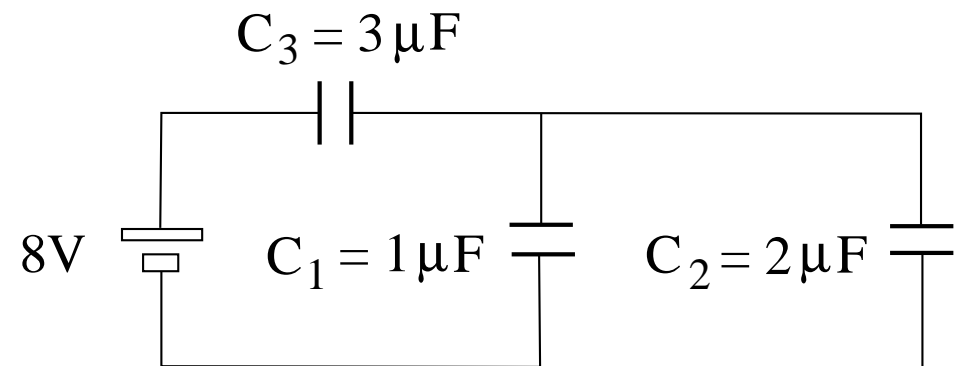- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the voltage V_3 across capacitor C_3 .
- (c) Find the charge Q_2 on capacitor C_2 .



Solution:

$$(a) \quad C_{12} = C_1 + C_2 = 3 \mu\text{F}, \quad C_{eq} = \left(\frac{1}{C_{12}} + \frac{1}{C_3} \right)^{-1} = 1.5 \mu\text{F}.$$


$$(b) \quad Q_3 = Q_{12} = Q_{eq} = C_{eq}(8\text{V}) = 12 \mu\text{C}$$
$$\Rightarrow V_3 = \frac{Q_3}{C_3} = \frac{12 \mu\text{C}}{3 \mu\text{F}} = 4\text{V}.$$

Intermediate Exam II: Problem #1 (Spring '05)



The circuit of capacitors connected to a battery is at equilibrium.

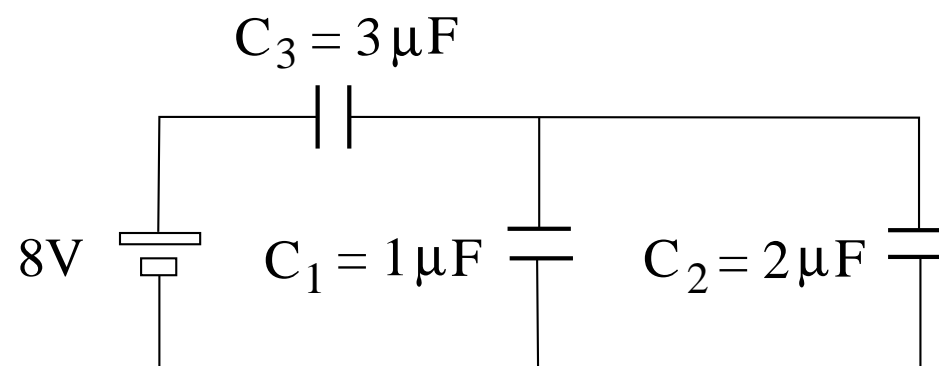- (a) Find the equivalent capacitance C_{eq} .
- (b) Find the voltage V_3 across capacitor C_3 .
- (c) Find the the charge Q_2 on capacitor C_2 .



Solution:

$$(a) \quad C_{12} = C_1 + C_2 = 3\mu\text{F}, \quad C_{eq} = \left(\frac{1}{C_{12}} + \frac{1}{C_3} \right)^{-1} = 1.5\mu\text{F}.$$

$$(b) \quad Q_3 = Q_{12} = Q_{eq} = C_{eq}(8\text{V}) = 12\mu\text{C}$$
$$\Rightarrow V_3 = \frac{Q_3}{C_3} = \frac{12\mu\text{C}}{3\mu\text{F}} = 4\text{V}.$$


$$(c) \quad Q_2 = V_2 C_2 = 8\mu\text{C}.$$

Unit Exam II: Problem #1 (Spring '07)



Consider the configuration of two point charges as shown.

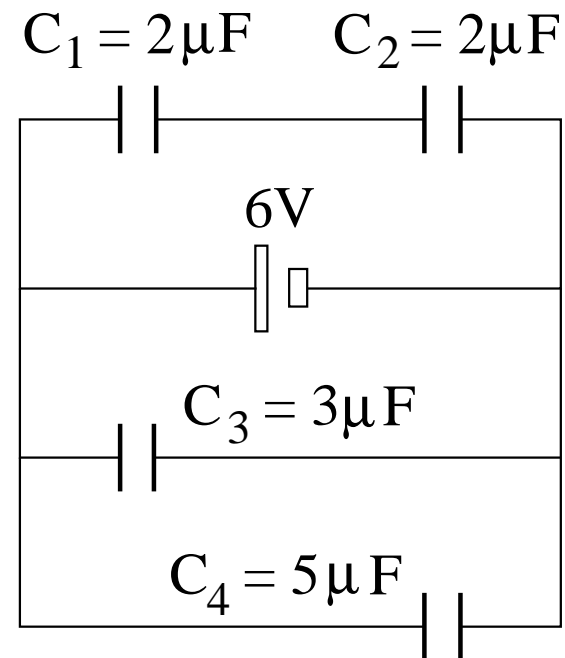- (a) Find the energy U_3 stored on capacitor C_3 .
- (b) Find the voltage V_4 across capacitor C_4 .
- (c) Find the voltage V_2 across capacitor C_2 .
- (d) Find the charge Q_1 on capacitor C_1 .



Unit Exam II: Problem #1 (Spring '07)




Consider the configuration of two point charges as shown.

- (a) Find the energy U_3 stored on capacitor C_3 .
- (b) Find the voltage V_4 across capacitor C_4 .
- (c) Find the voltage V_2 across capacitor C_2 .
- (d) Find the charge Q_1 on capacitor C_1 .

Solution:

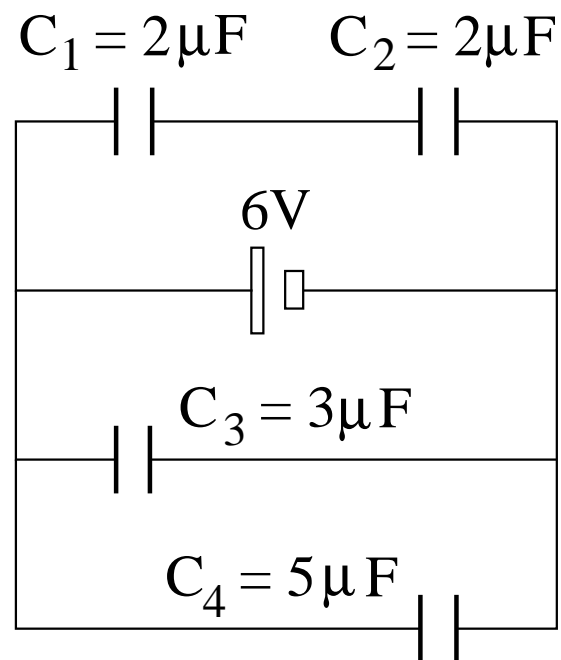(a) $U_3 = \frac{1}{2}(3\mu\text{F})(6\text{V})^2 = 54\mu\text{J}.$



Unit Exam II: Problem #1 (Spring '07)




Consider the configuration of two point charges as shown.

- (a) Find the energy U_3 stored on capacitor C_3 .
- (b) Find the voltage V_4 across capacitor C_4 .
- (c) Find the voltage V_2 across capacitor C_2 .
- (d) Find the charge Q_1 on capacitor C_1 .

Solution:

(a) $U_3 = \frac{1}{2}(3\mu\text{F})(6\text{V})^2 = 54\mu\text{J}.$

(b) $V_4 = 6\text{V}.$

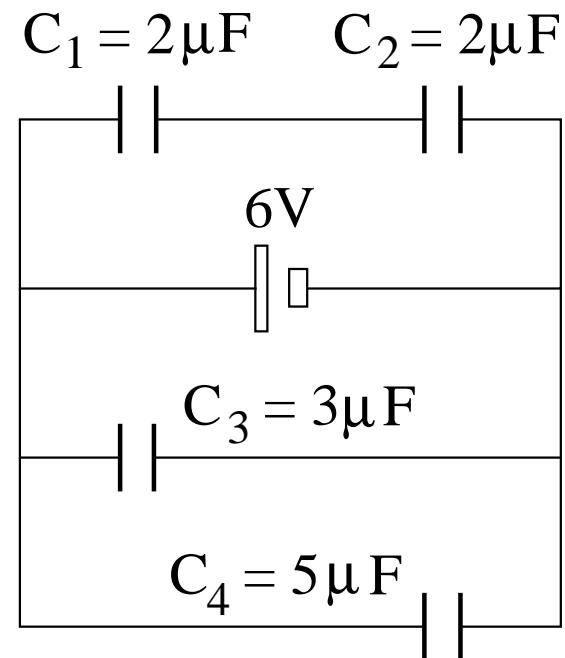

Unit Exam II: Problem #1 (Spring '07)



Consider the configuration of two point charges as shown.


- (a) Find the energy U_3 stored on capacitor C_3 .
- (b) Find the voltage V_4 across capacitor C_4 .
- (c) Find the voltage V_2 across capacitor C_2 .
- (d) Find the charge Q_1 on capacitor C_1 .

Solution:

(a) $U_3 = \frac{1}{2}(3\mu\text{F})(6\text{V})^2 = 54\mu\text{J}.$

(b) $V_4 = 6\text{V}.$

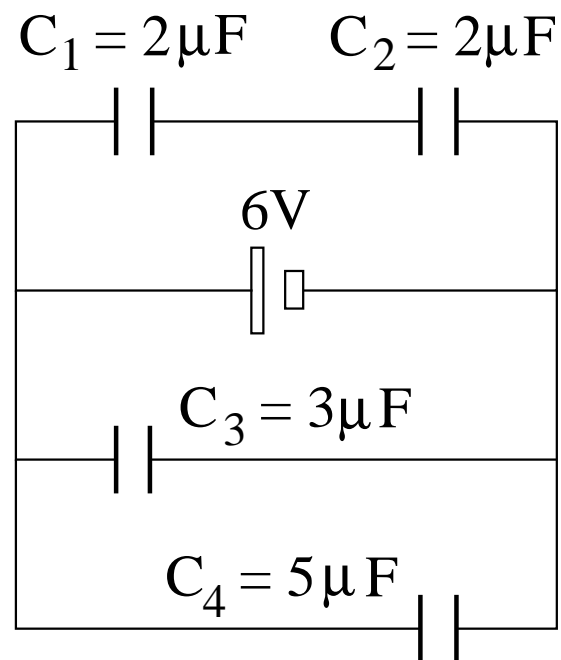(c) $V_2 = \frac{1}{2}6\text{V} = 3\text{V}.$



Unit Exam II: Problem #1 (Spring '07)




Consider the configuration of two point charges as shown.

- (a) Find the energy U_3 stored on capacitor C_3 .
- (b) Find the voltage V_4 across capacitor C_4 .
- (c) Find the voltage V_2 across capacitor C_2 .
- (d) Find the charge Q_1 on capacitor C_1 .

Solution:

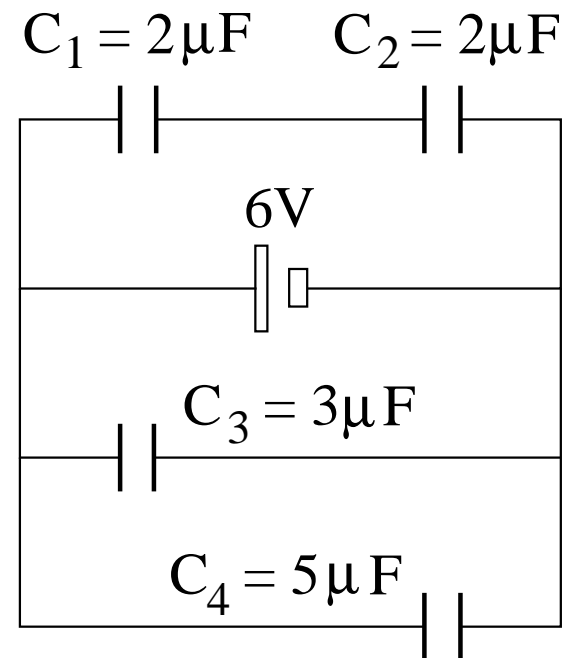- (a) $U_3 = \frac{1}{2}(3\mu\text{F})(6\text{V})^2 = 54\mu\text{J}.$
- (b) $V_4 = 6\text{V}.$
- (c) $V_2 = \frac{1}{2}6\text{V} = 3\text{V}.$
- (d) $Q_1 = (2\mu\text{F})(3\text{V}) = 6\mu\text{C}.$




Unit Exam II: Problem #1 (Spring '08)



The circuit of capacitors is at equilibrium.

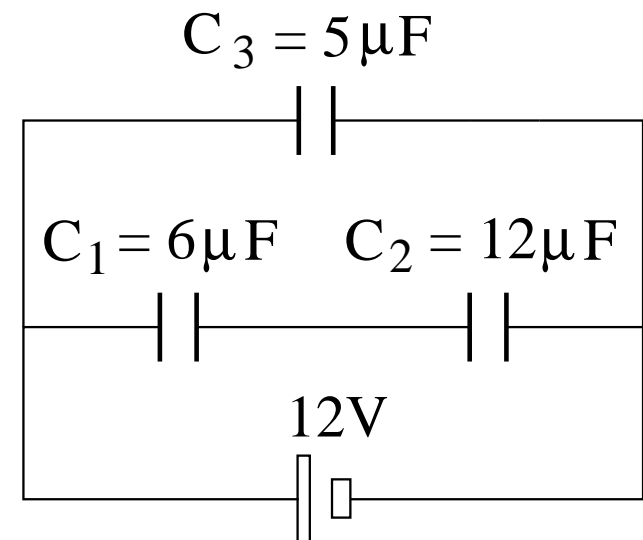- Find the charge Q_1 on capacitor 1 and the charge Q_2 on capacitor 2.
- Find the voltage V_1 across capacitor 1 and the voltage V_2 across capacitor 2.
- Find the charge Q_3 and the energy U_3 on capacitor 3.



Unit Exam II: Problem #1 (Spring '08)




The circuit of capacitors is at equilibrium.

- Find the charge Q_1 on capacitor 1 and the charge Q_2 on capacitor 2.
- Find the voltage V_1 across capacitor 1 and the voltage V_2 across capacitor 2.
- Find the charge Q_3 and the energy U_3 on capacitor 3.

Solution:
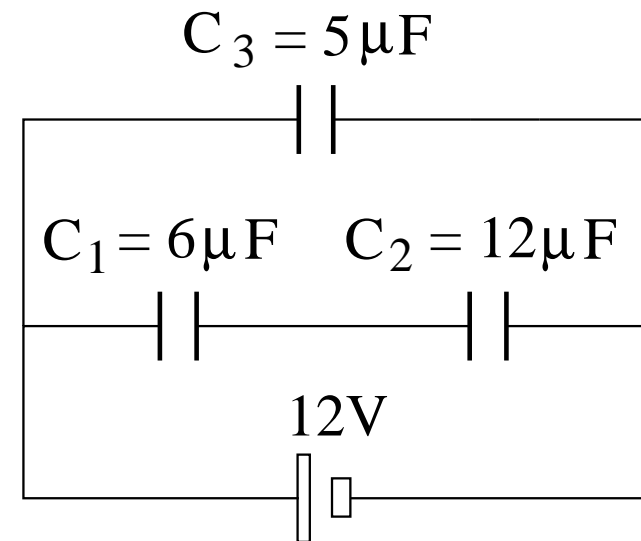
$$(a) \quad C_{12} = \left(\frac{1}{6\mu\text{F}} + \frac{1}{12\mu\text{F}} \right)^{-1} = 4\mu\text{F},$$
$$Q_1 = Q_2 = Q_{12} = (4\mu\text{F})(12\text{V}) = 48\mu\text{C}.$$



Unit Exam II: Problem #1 (Spring '08)



The circuit of capacitors is at equilibrium.

- Find the charge Q_1 on capacitor 1 and the charge Q_2 on capacitor 2.
- Find the voltage V_1 across capacitor 1 and the voltage V_2 across capacitor 2.
- Find the charge Q_3 and the energy U_3 on capacitor 3.


Solution:

$$(a) \quad C_{12} = \left(\frac{1}{6\mu\text{F}} + \frac{1}{12\mu\text{F}} \right)^{-1} = 4\mu\text{F},$$

$$Q_1 = Q_2 = Q_{12} = (4\mu\text{F})(12\text{V}) = 48\mu\text{C}.$$

$$(b) \quad V_1 = \frac{Q_1}{C_1} = \frac{48\mu\text{C}}{6\mu\text{F}} = 8\text{V},$$
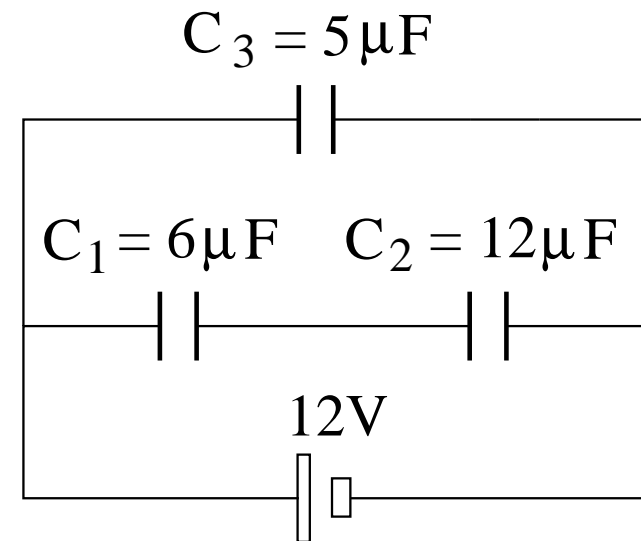
$$V_2 = \frac{Q_2}{C_2} = \frac{48\mu\text{C}}{12\mu\text{F}} = 4\text{V}.$$



Unit Exam II: Problem #1 (Spring '08)



The circuit of capacitors is at equilibrium.

- Find the charge Q_1 on capacitor 1 and the charge Q_2 on capacitor 2.
- Find the voltage V_1 across capacitor 1 and the voltage V_2 across capacitor 2.
- Find the charge Q_3 and the energy U_3 on capacitor 3.

Solution:

$$(a) \quad C_{12} = \left(\frac{1}{6\mu\text{F}} + \frac{1}{12\mu\text{F}} \right)^{-1} = 4\mu\text{F},$$


$$Q_1 = Q_2 = Q_{12} = (4\mu\text{F})(12\text{V}) = 48\mu\text{C}.$$

$$(b) \quad V_1 = \frac{Q_1}{C_1} = \frac{48\mu\text{C}}{6\mu\text{F}} = 8\text{V},$$

$$V_2 = \frac{Q_2}{C_2} = \frac{48\mu\text{C}}{12\mu\text{F}} = 4\text{V}.$$

$$(c) \quad Q_3 = (5\mu\text{F})(12\text{V}) = 60\mu\text{C},$$
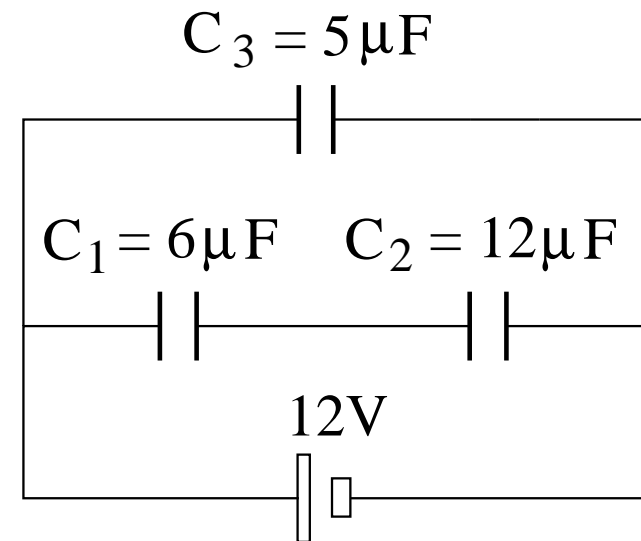
$$U_3 = \frac{1}{2}(5\mu\text{F})(12\text{V})^2 = 360\mu\text{J}.$$




Unit Exam II: Problem #2 (Spring '12)



Consider a parallel-plate capacitor of capacitance $C = 6\text{pF}$ with plates separated a distance $d = 1\text{mm}$ and a potential difference $V = V_+ - V_- = 3\text{V}$ between them.

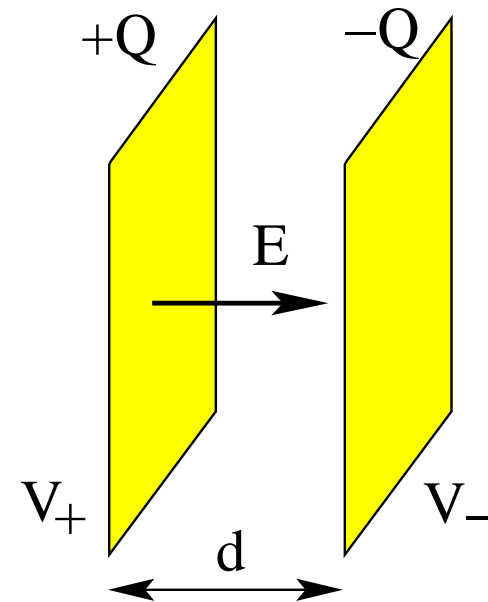- (a) Find the magnitude E of the electric field between the plates.
- (b) Find the amount Q of charge on each plate.
- (c) Find the energy U stored on the capacitor.
- (d) Find the area A of each plate.



Unit Exam II: Problem #2 (Spring '12)




Consider a parallel-plate capacitor of capacitance $C = 6\text{pF}$ with plates separated a distance $d = 1\text{mm}$ and a potential difference $V = V_+ - V_- = 3\text{V}$ between them.

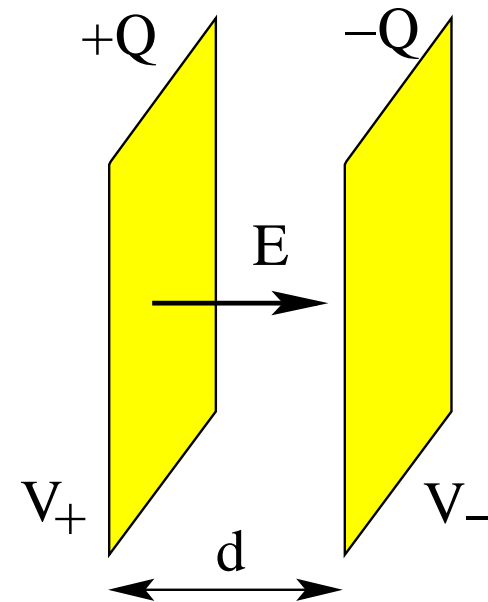- (a) Find the magnitude E of the electric field between the plates.
- (b) Find the amount Q of charge on each plate.
- (c) Find the energy U stored on the capacitor.
- (d) Find the area A of each plate.

Solution:

$$(a) \quad E = \frac{V}{d} = \frac{3\text{V}}{1\text{mm}} = 3000\text{V/m}.$$



Unit Exam II: Problem #2 (Spring '12)




Consider a parallel-plate capacitor of capacitance $C = 6\text{pF}$ with plates separated a distance $d = 1\text{mm}$ and a potential difference $V = V_+ - V_- = 3\text{V}$ between them.

- (a) Find the magnitude E of the electric field between the plates.
- (b) Find the amount Q of charge on each plate.
- (c) Find the energy U stored on the capacitor.
- (d) Find the area A of each plate.

Solution:

$$(a) \quad E = \frac{V}{d} = \frac{3\text{V}}{1\text{mm}} = 3000\text{V/m.}$$
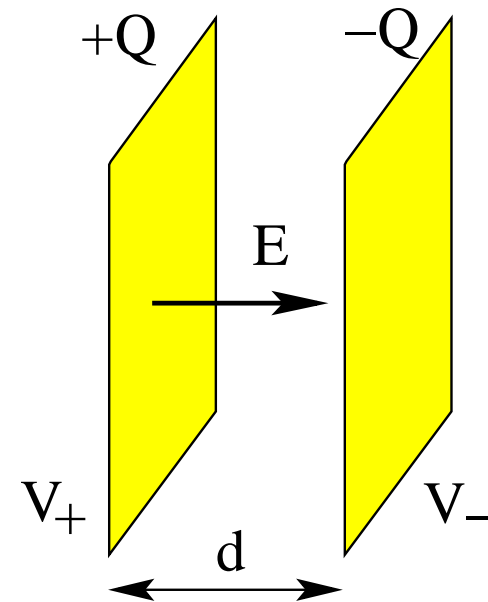
$$(b) \quad Q = CV = (6\text{pF})(3\text{V}) = 18\text{pC.}$$



Unit Exam II: Problem #2 (Spring '12)



Consider a parallel-plate capacitor of capacitance $C = 6\text{pF}$ with plates separated a distance $d = 1\text{mm}$ and a potential difference $V = V_+ - V_- = 3\text{V}$ between them.


- Find the magnitude E of the electric field between the plates.
- Find the amount Q of charge on each plate.
- Find the energy U stored on the capacitor.
- Find the area A of each plate.

Solution:

$$(a) \quad E = \frac{V}{d} = \frac{3\text{V}}{1\text{mm}} = 3000\text{V/m}.$$

$$(b) \quad Q = CV = (6\text{pF})(3\text{V}) = 18\text{pC}.$$
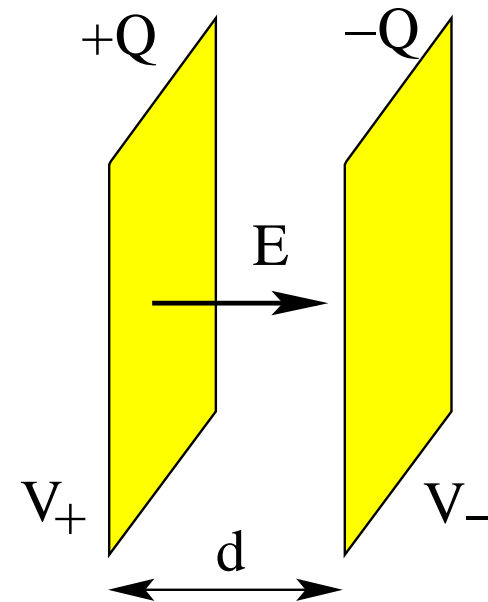
$$(c) \quad U = \frac{1}{2}QV = 0.5(18\text{pC})(3\text{V}) = 27\text{pJ}.$$



Unit Exam II: Problem #2 (Spring '12)



Consider a parallel-plate capacitor of capacitance $C = 6\text{pF}$ with plates separated a distance $d = 1\text{mm}$ and a potential difference $V = V_+ - V_- = 3\text{V}$ between them.

- Find the magnitude E of the electric field between the plates.
- Find the amount Q of charge on each plate.
- Find the energy U stored on the capacitor.
- Find the area A of each plate.

Solution:

$$(a) \quad E = \frac{V}{d} = \frac{3\text{V}}{1\text{mm}} = 3000\text{V/m}.$$

$$(b) \quad Q = CV = (6\text{pF})(3\text{V}) = 18\text{pC}.$$

$$(c) \quad U = \frac{1}{2}QV = 0.5(18\text{pC})(3\text{V}) = 27\text{pJ}.$$

$$(d) \quad A = \frac{Cd}{\epsilon_0} = \frac{(6\text{pF})(1\text{mm})}{8.85 \times 10^{-12}\text{C}^2\text{N}^{-1}\text{m}^{-2}} = 6.78 \times 10^{-4}\text{m}^2.$$

