


# Capacitor Problem (1)



Consider two oppositely charged parallel plates separated by a very small distance  $d$ .

What happens when the plates are pulled apart a fraction of  $d$ ? Will the quantities listed below increase or decrease in magnitude or stay unchanged?

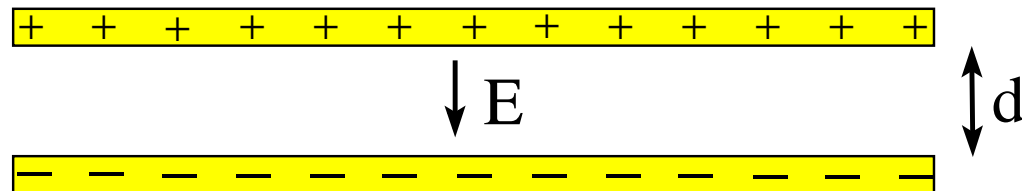- (a) Electric field  $\vec{E}$  between the plates.
- (b) Voltage  $V$  across the plates.
- (c) Capacitance  $C$  of the device.
- (d) Energy  $U$  stored in the device.



## Capacitor Problem (2)



Consider two equal capacitors connected in series.

- (a) Find the voltages  $V_A - V_B$ ,  $V_B - V_C$ ,  $V_A - V_D$ .
- (b) Find the charge  $Q_A$  on plate  $A$ .
- (c) Find the electric field  $E$  between plates  $C$  and  $D$ .

