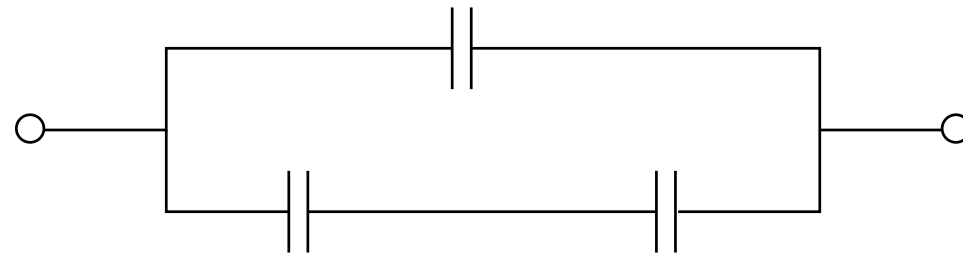


Capacitor Circuit (1)




Find the equivalent capacitances of the two capacitor networks.
All capacitors have a capacitance of $1\mu F$.

(a)



(b)

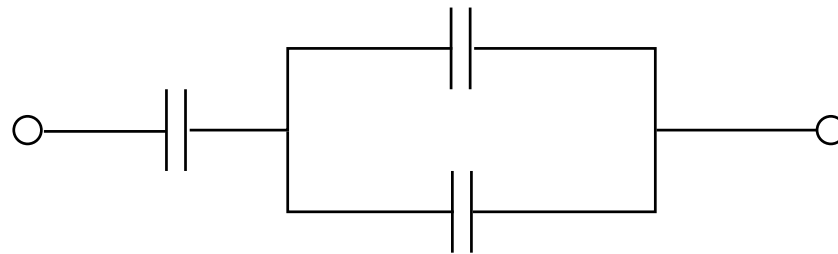


Capacitor Circuit (2)




Consider the two capacitors connected in parallel.

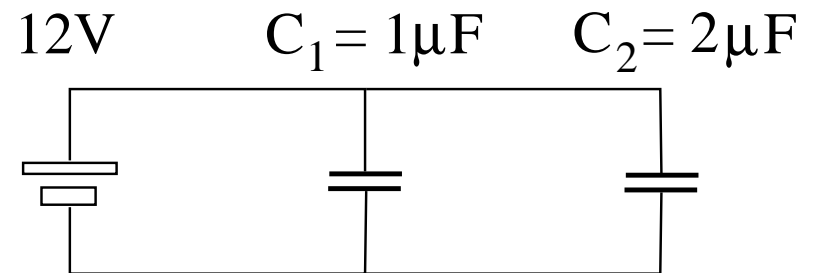- (a) Which capacitor has the higher voltage?
- (b) Which capacitor has more charge?
- (c) Which capacitor has more energy?



Consider the two capacitors connected in series.


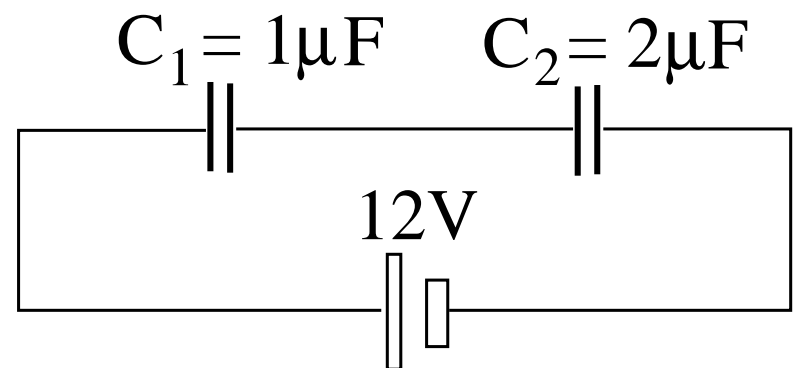
- (d) Which capacitor has the higher voltage?
- (e) Which capacitor has more charge?
- (f) Which capacitor has more energy?



Capacitor Circuit (3)



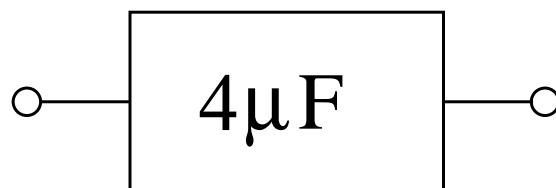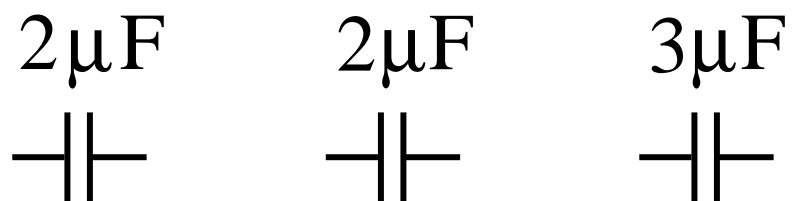
Connect the three capacitors in such a way that the equivalent capacitance is $C_{eq} = 4\mu\text{F}$. Draw the circuit diagram.



Capacitor Circuit (4)




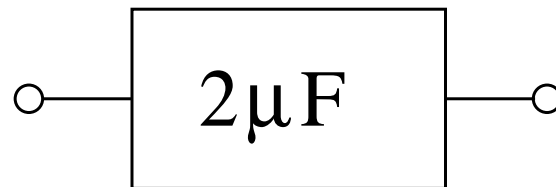
Connect the three capacitors in such a way that the equivalent capacitance is $C_{eq} = 2\mu\text{F}$. Draw the circuit diagram.



Capacitor Circuit (5)



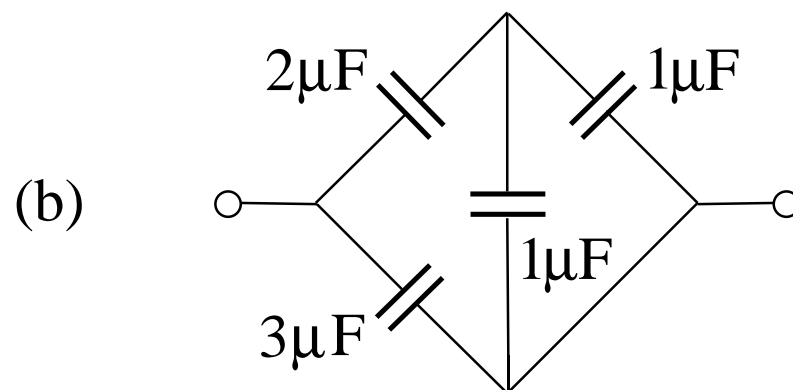
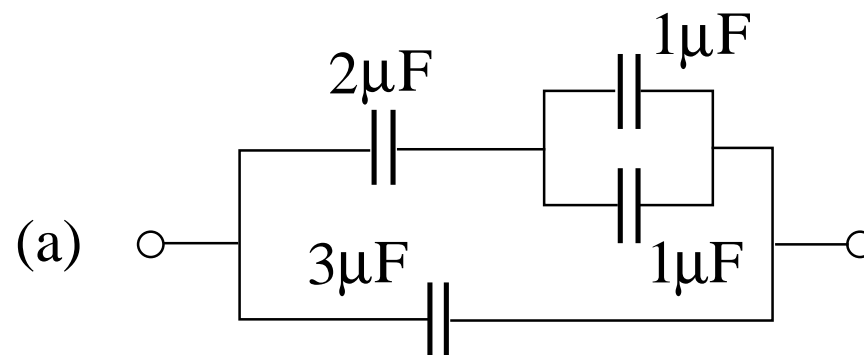
Find the equivalent capacitances of the following circuits.



Capacitor Circuit (6)



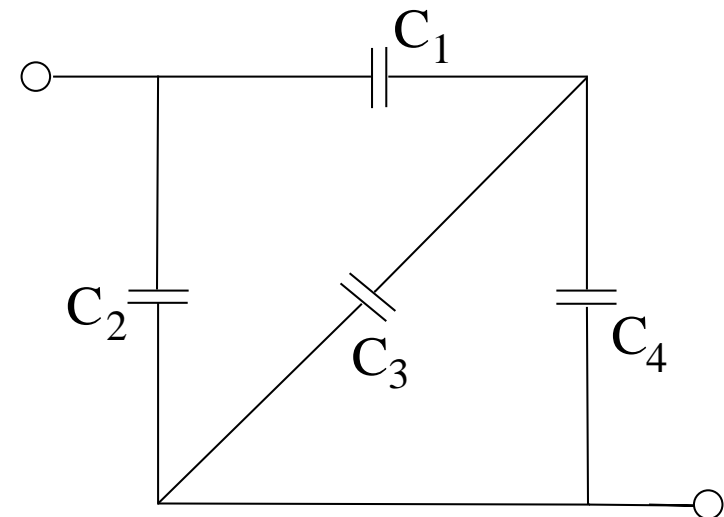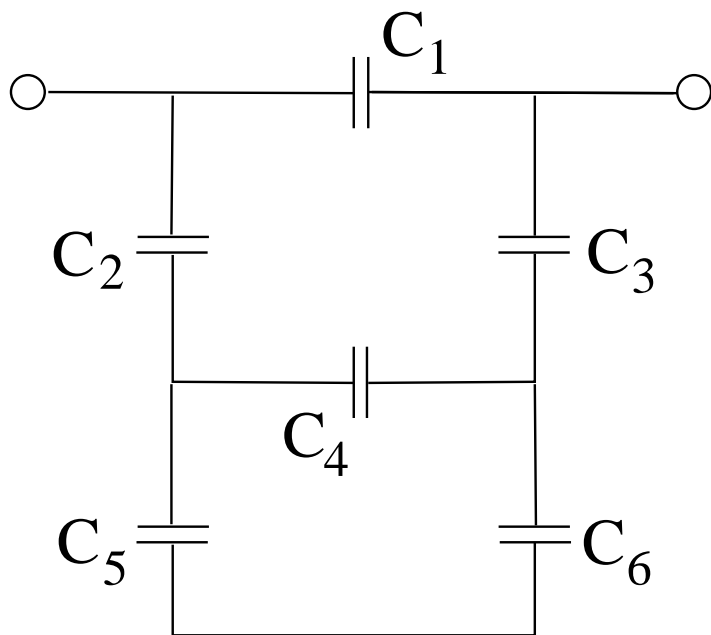
- (a) Name two capacitors from the circuit on the **left** that are connected in **series**.
- (b) Name two capacitors from the circuit on the **right** that are connected in **parallel**.



Capacitor Circuit (7)



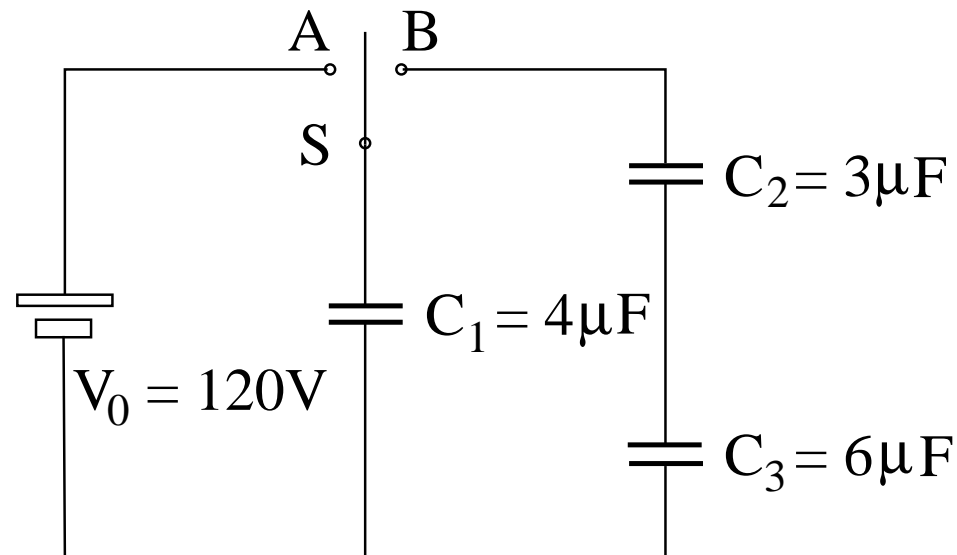- (a) In the circuit shown the switch is first thrown to A . Find the charge Q_0 and the energy U_A on the capacitor C_1 once it is charged up.
- (b) Then the switch is thrown to B , which charges up the capacitors C_2 and C_3 . The capacitor C_1 is partially discharged in the process. Find the charges Q_1, Q_2, Q_3 on all three capacitors and the voltages V_1, V_2, V_3 across each capacitor once equilibrium has been reached again. What is the energy U_B now stored in the circuit?



Capacitor Circuit (8)



In the circuit shown find the charges Q_1, Q_2, Q_3, Q_4 on each capacitor and the voltages V_1, V_2, V_3, V_4 across each capacitor

- (a) when the switch S is open,
- (b) when the switch S is closed.

