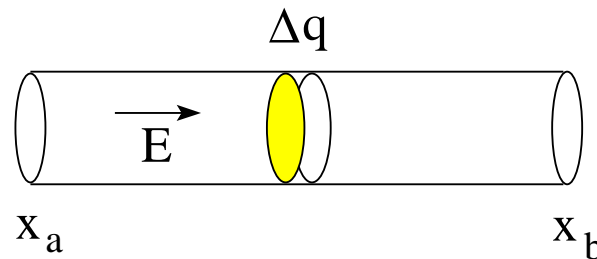


# Power Dissipation in Resistor



Consider a resistor in the form of a uniform wire.

- Voltage between ends:  $V \equiv V_a - V_b = E(x_b - x_a)$
- Displaced charge:  $\Delta q = I \Delta t$



- Work done by electric field  $\vec{E}$  on displaced charge  $\Delta q$ :

$$W_E = F(x_b - x_a) = E \Delta q (x_b - x_a) = V \Delta q = VI \Delta t$$

- Power dissipated in resistor:  $P = \frac{W_E}{\Delta t} = VI = I^2 R = \frac{V^2}{R}$
- SI unit:  $1V \cdot 1A = (1J/C) \cdot (1C/s) = 1J/s = 1W$  (Watt)

