


# Direct Current Circuit




Consider a wire with resistance  $R = \rho l/A$  connected to a battery.

- **Resistor rule:** In the direction of  $I$  across a resistor with resistance  $R$ , the electric potential drops:  $\Delta V = -IR$ .
- **EMF rule:** From the  $(-)$  terminal to the  $(+)$  terminal in an ideal source of emf, the potential rises:  $\Delta V = \mathcal{E}$ .
- **Loop rule:** The algebraic sum of the changes in potential encountered in a complete traversal of any loop in a circuit must be zero:  $\sum \Delta V_i = 0$ .

physical system

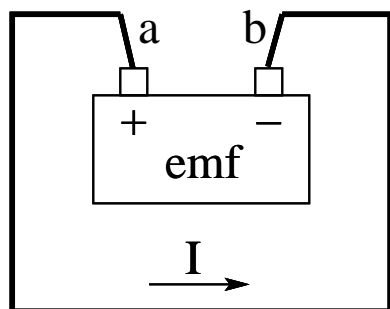

circuit diagram

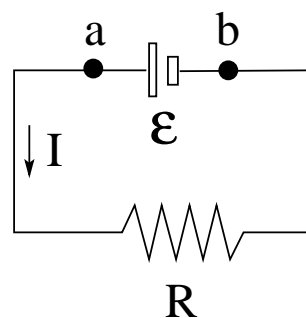

electric potential

