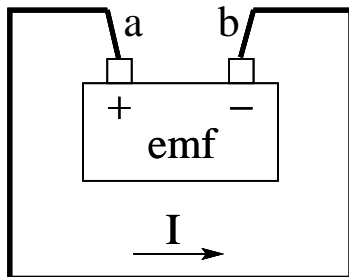


Battery with Internal Resistance




- Real batteries have an internal resistance r .
- The terminal voltage $V_{ba} \equiv V_a - V_b$ is smaller than the emf \mathcal{E} written on the label if a current flows through the battery.
- Usage of the battery increases its internal resistance.
- Current from loop rule: $\mathcal{E} - Ir - IR = 0 \Rightarrow I = \frac{\mathcal{E}}{R + r}$
- Current from terminal voltage: $V_{ba} = \mathcal{E} - Ir = IR \Rightarrow I = \frac{V_{ba}}{R}$

physical system



circuit diagram

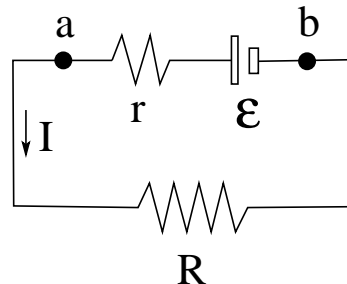

electric potential

