

Impedance Matching



A battery providing an emf \mathcal{E} with internal resistance r is connected to an external resistor of resistance R as shown.

For what value of R does the battery deliver the maximum power to the external resistor?

- Electric current: $\mathcal{E} - Ir - IR = 0 \Rightarrow I = \frac{\mathcal{E}}{R + r}$
- Power delivered to external resistor: $P = I^2 R = \frac{\mathcal{E}^2 R}{(R + r)^2}$
- Condition for maximum power: $\frac{dP}{dR} = 0 \Rightarrow R = r$

