

# Applying the Junction Rule



In the circuit of steady currents, use the junction rule to find the unknown currents  $I_1, \dots, I_6$ .

