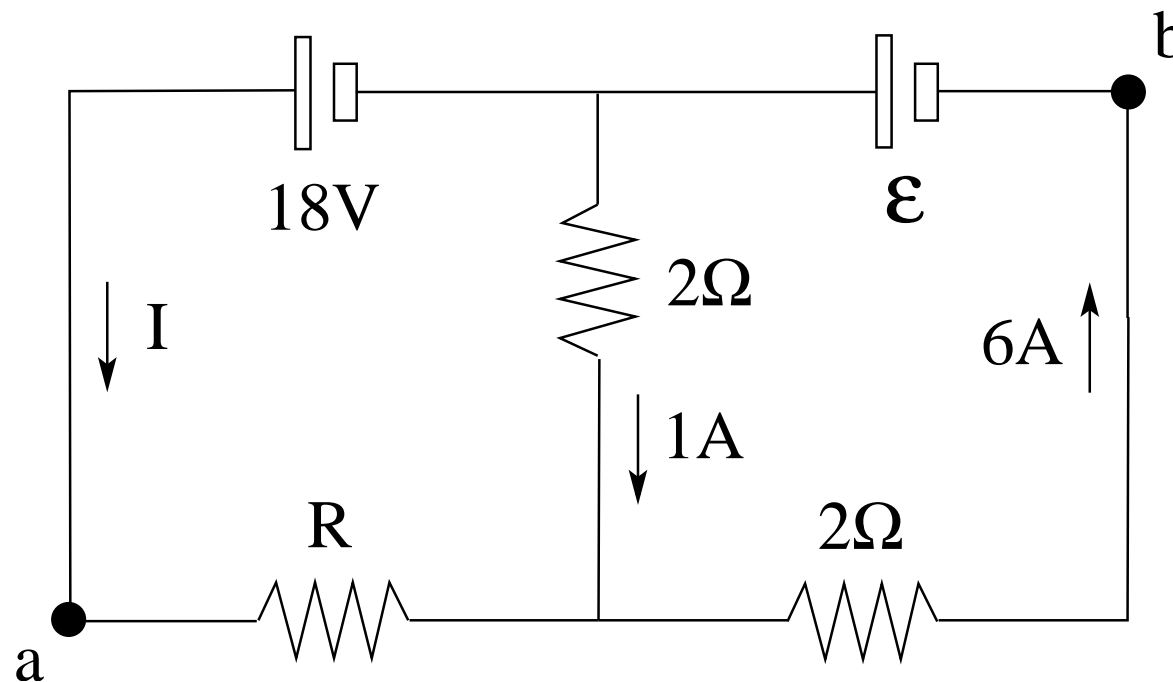


Resistor Circuit (9)



Use Kirchhoff's rules to find

- (a) the current I ,
- (b) the resistance R ,
- (c) the emf \mathcal{E} ,
- (d) the voltage $V_{ab} \equiv V_b - V_a$.




Resistor Circuit (10)



Consider the electric circuit shown.

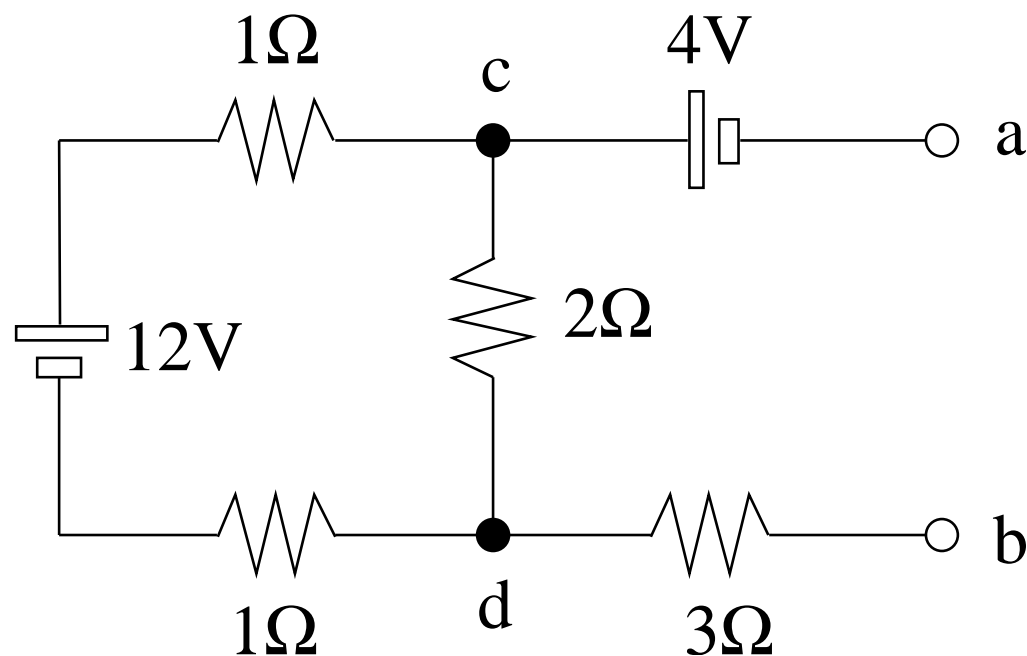- (a) Find the current through the 12V battery.
- (b) Find the current through the 2Ω resistor.
- (c) Find the total power dissipated.
- (d) Find the voltage $V_{cd} \equiv V_d - V_c$.
- (e) Find the voltage $V_{ab} \equiv V_b - V_a$.




Resistor Circuit (11)



Consider the electric circuit shown.

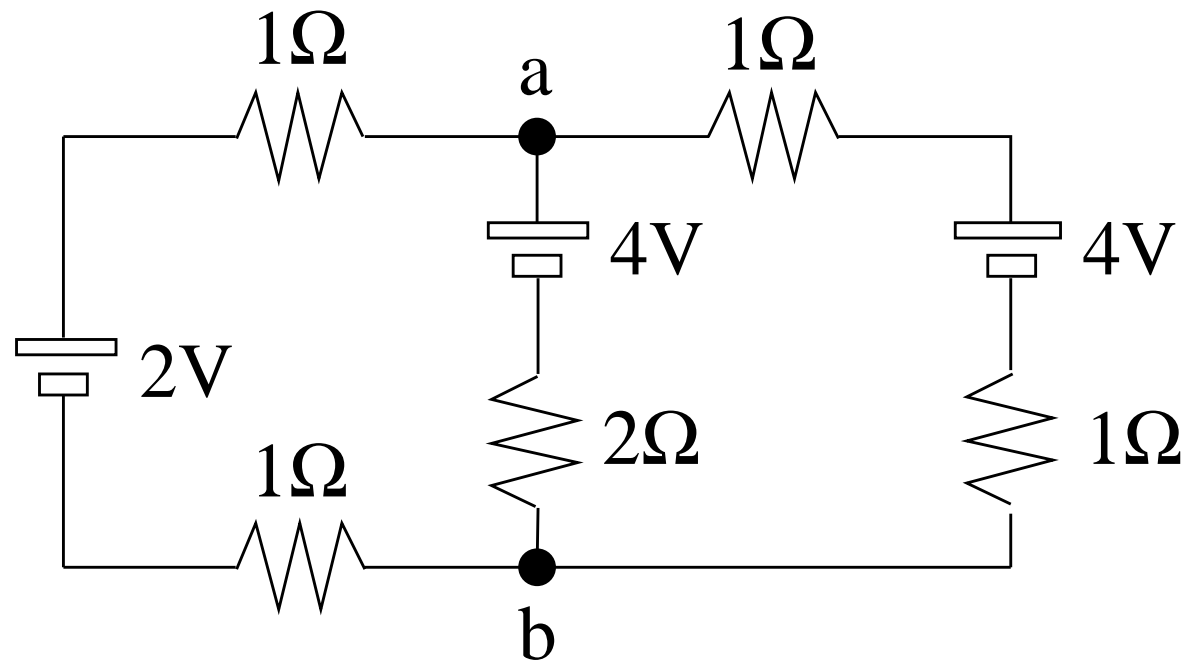- Identify all independent currents via junction rule.
- Determine the independent currents via loop rule.
- Find the Potential difference $V_{ab} = V_b - V_a$.



Resistor Circuit (12)



Consider the electric circuit shown.

- Find the equivalent resistance R_{eq} of the circuit.
- Find the total power P dissipated in the circuit.

