

RL Circuit: Fundamentals




Specifications:

- \mathcal{E} (emf)
- R (resistance)
- L (inductance)

Switch S :

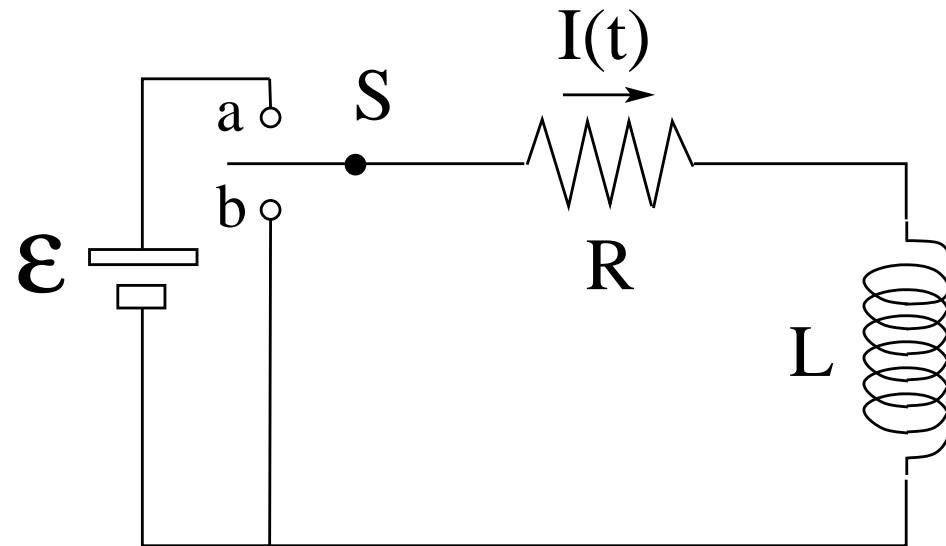- a: current buildup
- b: current shutdown



Time-dependent quantities:

- $I(t)$: instantaneous current through inductor
- $\frac{dI}{dt}$: rate of change of instantaneous current
- $V_R(t) = I(t)R$: instantaneous voltage across resistor
- $V_L(t) = L \frac{dI}{dt}$: instantaneous voltage across inductor