




Single Device in AC Circuit: Application (1)



The ac voltage source $\mathcal{E} = \mathcal{E}_{max} \sin \omega t$ has an amplitude of $\mathcal{E}_{max} = 24V$ and an angular frequency of $\omega = 10\text{rad/s}$.

In each of the three circuits, find

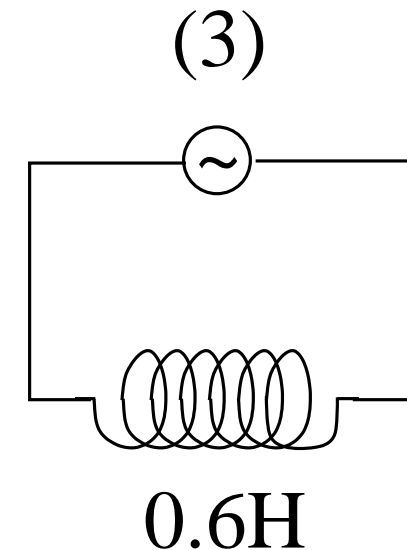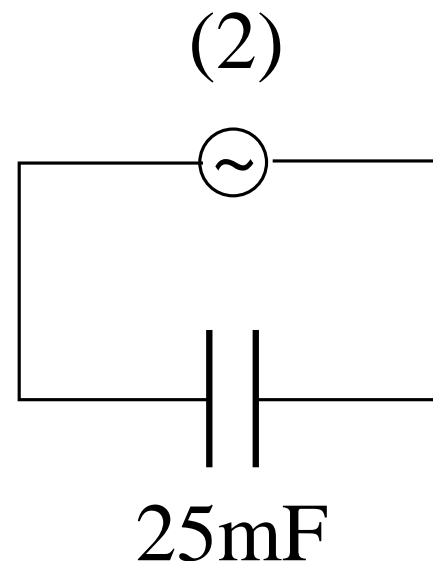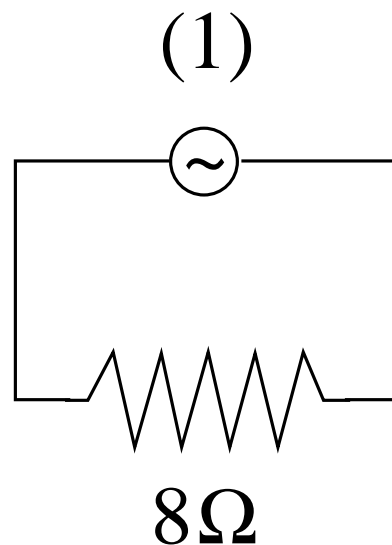- (a) the current amplitude I_{max} ,
- (b) the current I at time $t = 1\text{s}$.




Single Device in AC Circuit: Application (2)



Consider an ac generator $\mathcal{E}(t) = \mathcal{E}_{max} \cos(\omega t)$, $\mathcal{E}_{max} = 25\text{V}$, $\omega = 377\text{rad/s}$ connected to an inductor with inductance $L = 12.7\text{H}$.

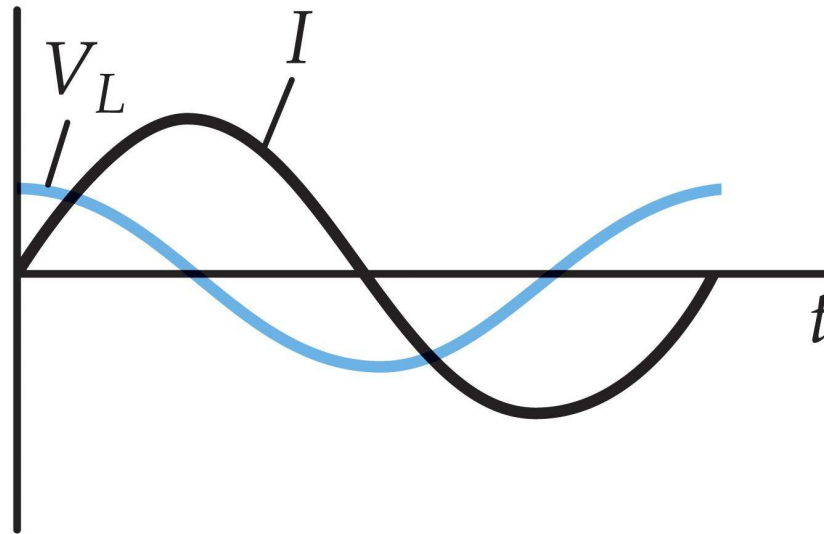- (a) Find the maximum value of the current.
- (b) Find the current when the emf is zero and decreasing.
- (c) Find the current when the emf is -12.5V and decreasing.
- (d) Find the power supplied by the generator at the instant described in (c).



Single Device in AC Circuit: Application (3)



Consider an ac generator $\mathcal{E}(t) = \mathcal{E}_{max} \cos(\omega t)$, $\mathcal{E}_{max} = 25\text{V}$, $\omega = 377\text{rad/s}$ connected to a capacitor with capacitance $C = 4.15\mu\text{F}$.

- (a) Find the maximum value of the current.
- (b) Find the current when the emf is zero and decreasing.
- (c) Find the current when the emf is -12.5V and increasing.
- (d) Find the power supplied by the generator at the instant described in (c).

