


AC Circuit Application (1)



In this RLC circuit, the voltage amplitude is $\mathcal{E}_{max} = 100\text{V}$.

Find the impedance Z , the current amplitude I_{max} ,
and the voltage amplitudes V_R, V_C, V_L, V_{LC}

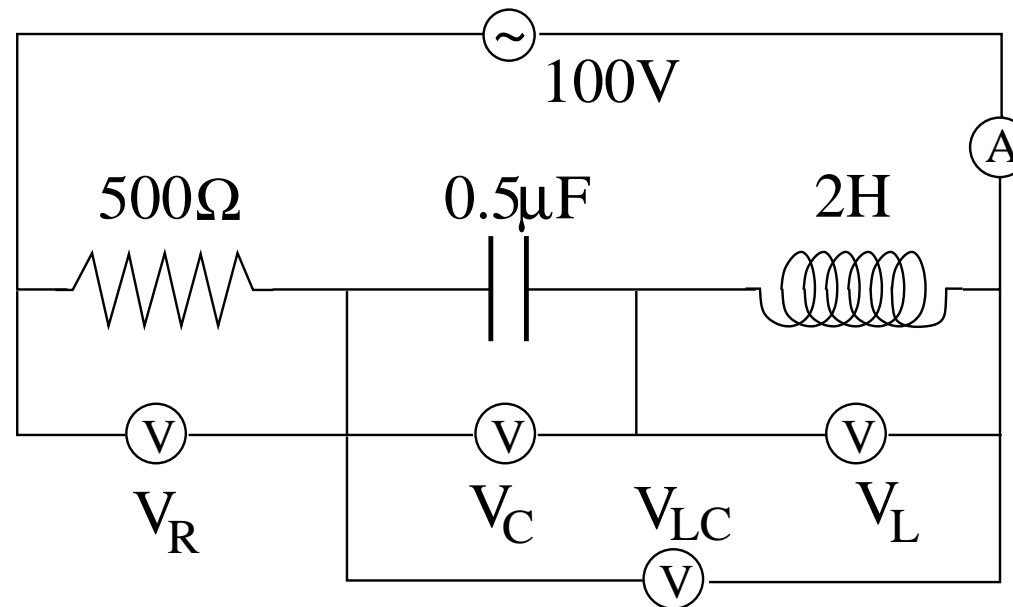- (a) for angular frequency is $\omega = 1000\text{rad/s}$,
- (b) for angular frequency is $\omega = 500\text{rad/s}$.



AC Circuit Application (2)



In this RLC circuit, we know the voltage amplitudes V_R, V_C, V_L across each device, the current amplitude $I_{max} = 5A$, and the angular frequency $\omega = 2\text{rad/s}$.

- Find the device properties R, C, L and the voltage amplitude \mathcal{E}_{max} of the ac source.

