


AC Circuit Application (3)



Find the current amplitudes I_1, I_2, I_3

(a) for angular frequency $\omega = 2\text{rad/s}$,

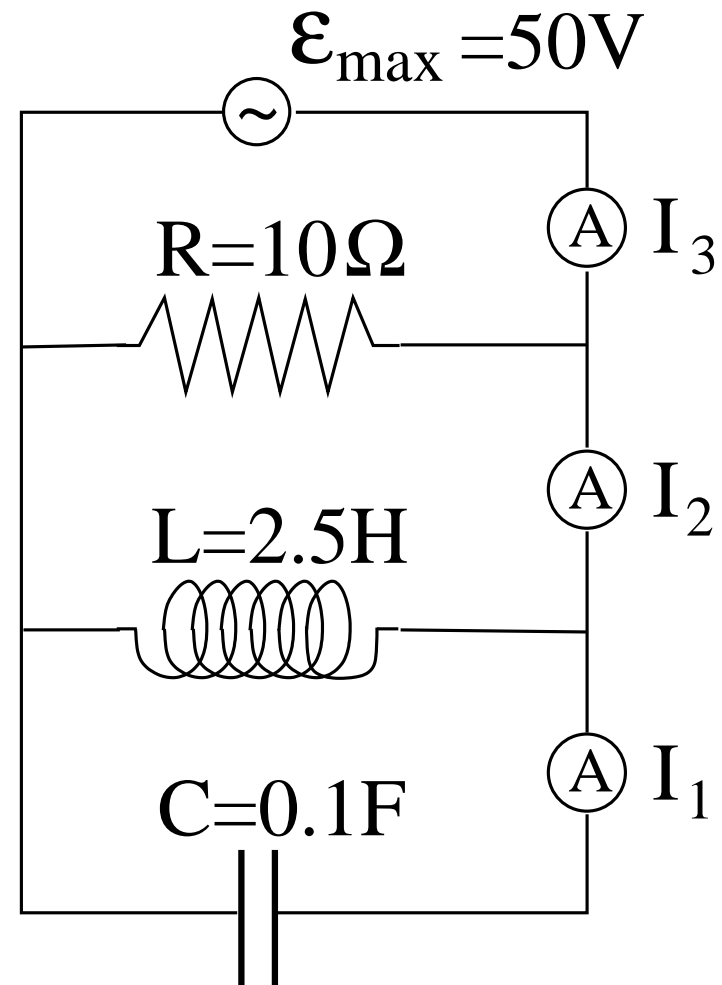
(b) for angular frequency $\omega = 4\text{rad/s}$.



AC Circuit Application (4)






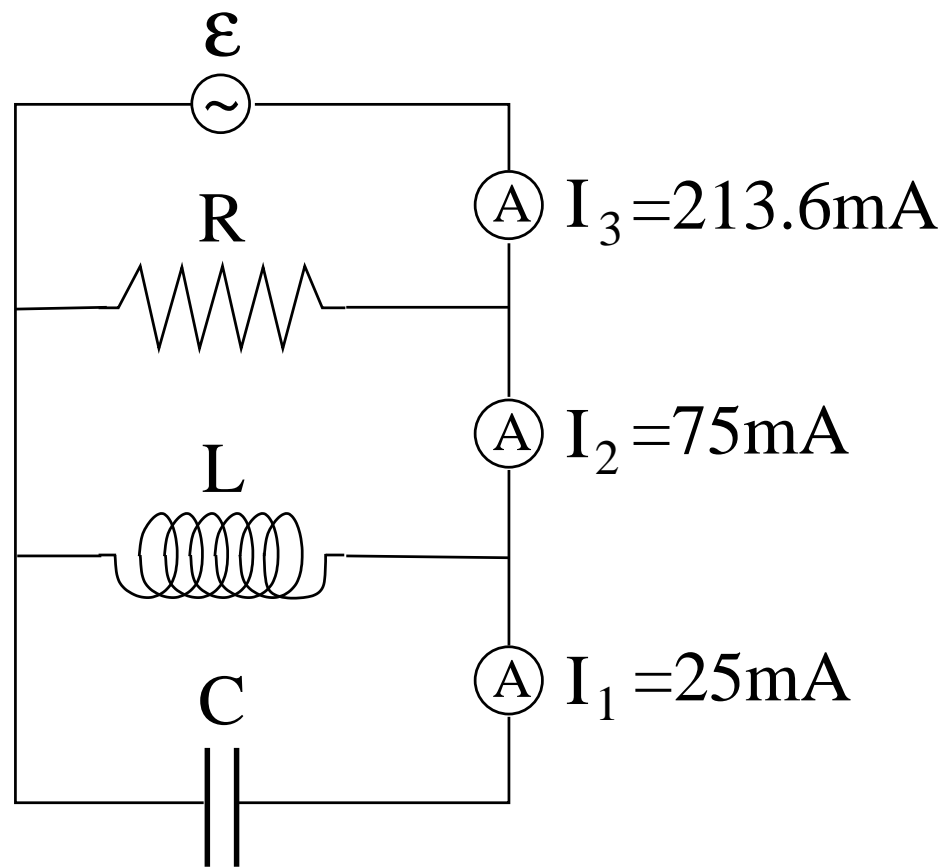
Given the current amplitudes I_1, I_2, I_3 through the three branches of this RLC circuit, and given the amplitude $\mathcal{E}_{max} = 100\text{V}$ and angular frequency $\omega = 500\text{rad/s}$ of the ac source, find the device properties R, L, C .



AC Circuit Application (5)



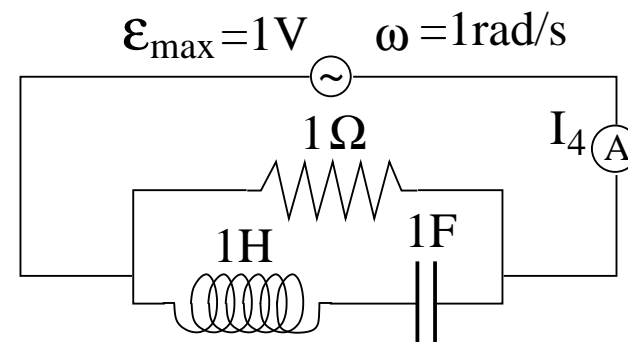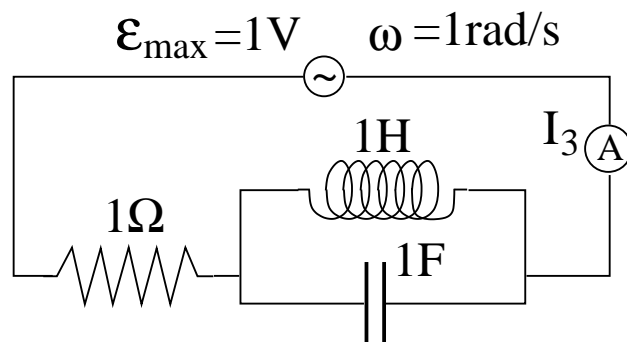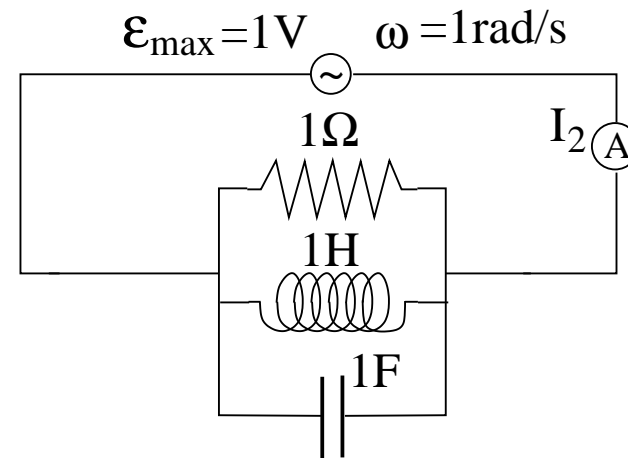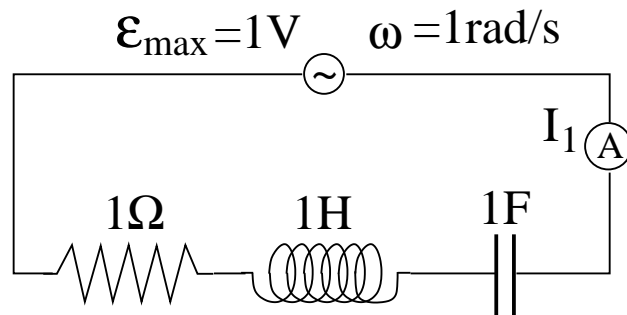Find the current amplitudes I_1, I_2, I_3, I_4 in the four RLC circuits shown.



AC Circuit Application (6)



Consider an RLC series circuit with inductance $L = 88\text{mH}$, capacitance $C = 0.94\mu\text{F}$, and unknown resistance R .

The ac generator $\mathcal{E} = \mathcal{E}_{max} \sin(\omega t)$ has amplitude $\mathcal{E}_{max} = 24\text{V}$ and frequency $f = 930\text{Hz}$. The phase angle is $\delta = 75^\circ$.

- (a) Find the resistance R .
- (b) Find the current amplitude I_{max} .
- (c) Find the maximum energy U_L^{max} stored in the inductor.
- (d) Find the maximum energy U_C^{max} stored in the capacitor.
- (e) Find the time t_1 at which the current has its maximum value I_{max} .
- (f) Find the time t_2 at which the charge on the capacitor has its maximum value Q_{max} .