

## Intermediate Exam III: Problem #1 (Spring '05)




An infinitely long straight current of magnitude  $I = 6\text{A}$  is directed into the plane ( $\otimes$ ) and located a distance  $d = 0.4\text{m}$  from the coordinate origin (somewhere on the dashed circle). The magnetic field  $\vec{B}$  generated by this current is in the negative  $y$ -direction as shown.

- (a) Find the magnitude  $B$  of the magnetic field.
- (b) Mark the location of the position of the current  $\otimes$  on the dashed circle.

**Solution:**

(a) 
$$B = \frac{\mu_0 I}{2\pi d} = 3\mu\text{T}.$$

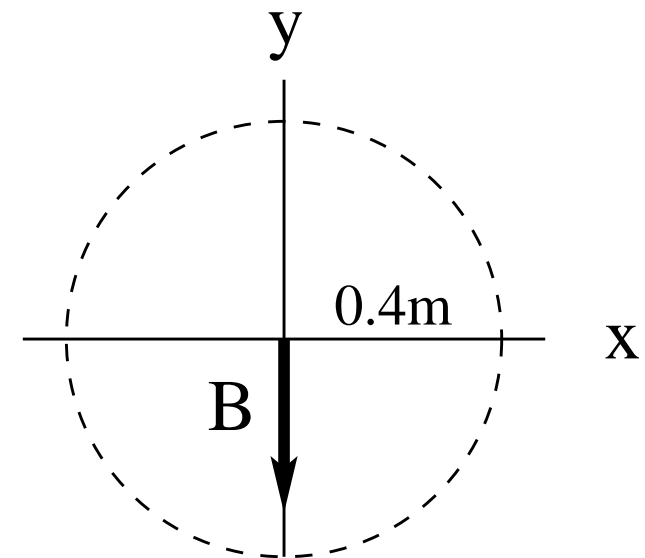(b) Position of current  $\otimes$  is at  $y = 0, x = -0.4\text{m}$ .




## Intermediate Exam III: Problem #2 (Spring '05)



In the circuit shown we close the switch  $S$  at time  $t = 0$ . Find the current  $I$  through the battery and the voltage  $V_L$  across the inductor

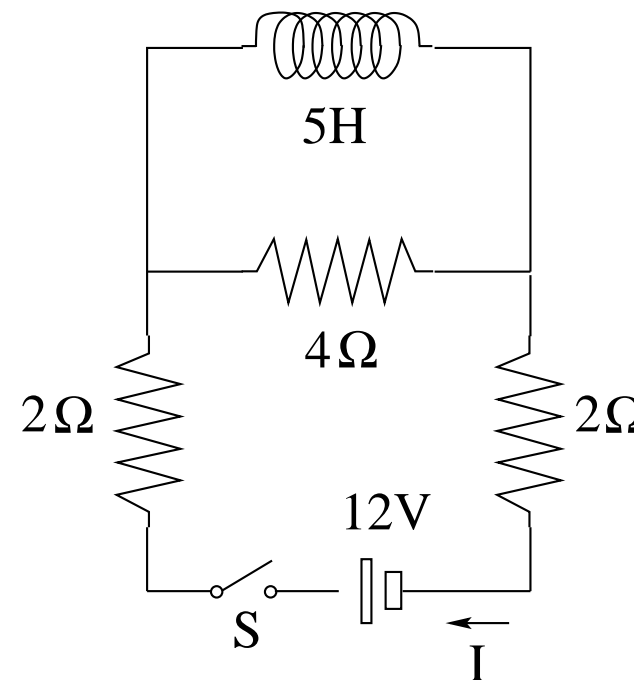- (a) immediately after the switch has been closed,
- (b) a very long time later.



**Solution:**

$$(a) \quad I = \frac{12V}{2\Omega + 4\Omega + 2\Omega} = 1.5A, \quad V_L = (4\Omega)(1.5A) = 6V.$$

$$(b) \quad I = \frac{12V}{2\Omega + 2\Omega} = 3A, \quad V_L = 0.$$

## Intermediate Exam III: Problem #3 (Spring '05)



At time  $t = 0$  the capacitor is charged to  $Q_{max} = 3\mu\text{C}$  and the current is instantaneously zero.


- (a) How much energy is stored in the capacitor at time  $t = 0$ ?
- (b) At what time  $t_1$  does the current reach its maximum value?
- (c) How much energy is stored in the inductor at time  $t_1$ ?

**Solution:**

$$(a) U_C = \frac{Q_{max}^2}{2C} = 0.5\mu\text{J}.$$

$$(b) T = \frac{2\pi}{\omega} = 2\pi\sqrt{LC} = 3.77\text{ms}, \quad t_1 = \frac{T}{4} = 0.942\text{ms}.$$
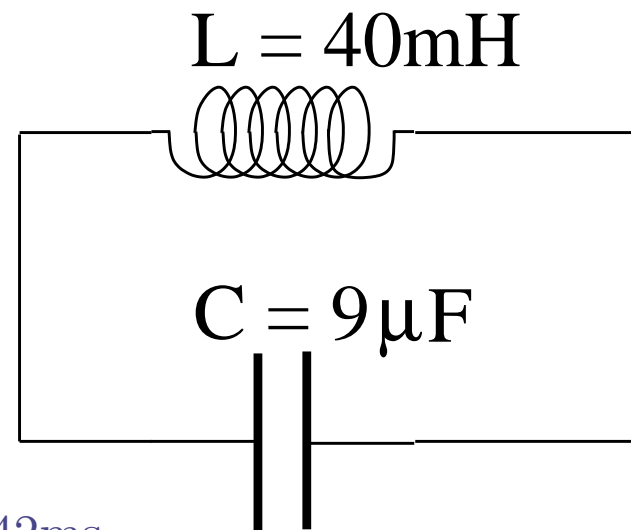
$$(c) U_L = U_C = 0.5\mu\text{J} \quad (\text{energy conservation.})$$



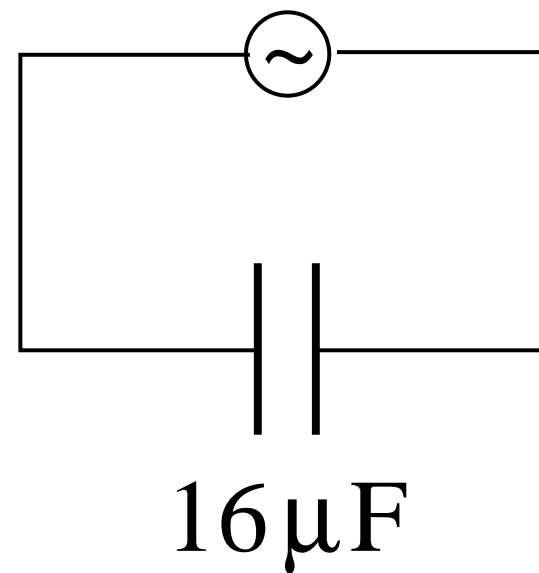
## Intermediate Exam III: Problem #4 (Spring '05)



Consider the circuit shown. The *ac* voltage supplied is  $\mathcal{E} = \mathcal{E}_{max} \cos(\omega t)$  with  $\mathcal{E}_{max} = 170\text{V}$  and  $\omega = 377\text{rad/s}$ .

- What is the maximum value  $I_{max}$  of the current?
- What is the emf  $\mathcal{E}(t)$  at  $t = 0.01\text{s}$ ?
- What is the current  $I(t)$  at  $t = 0.01\text{s}$ ?



**Solution:**

$$(a) I_{max} = \frac{\mathcal{E}_{max}}{X_C} = \mathcal{E}_{max}\omega C = 1.03\text{A}.$$

$$(b) \mathcal{E} = (170\text{V}) \cos(3.77\text{rad}) = (170\text{V})(-0.809) = -138\text{V}.$$

$$(c) I = \mathcal{E}_{max}\omega C \cos(3.77\text{rad} + \pi/2) = (1.03\text{A})(0.588) = 0.605\text{A}.$$