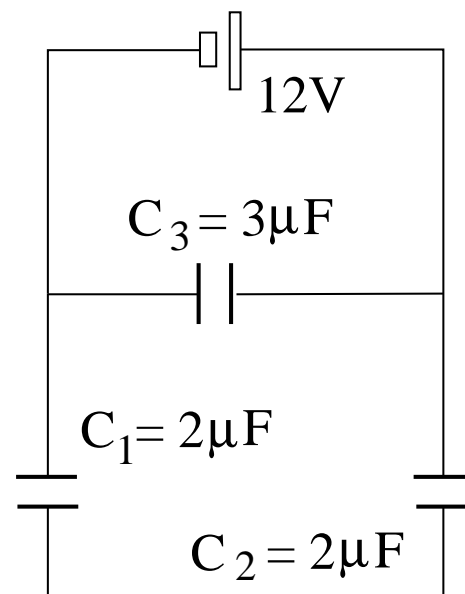


Intermediate Exam II: Problem #1 (Spring '06)



The circuit of capacitors connected to a battery is at equilibrium.

- (a) Find the charge Q_3 on capacitor C_3 .
- (b) Find the charge Q_2 on capacitor C_2 .



Solution:


- (a) $Q_3 = C_3(12\text{V}) = (3\mu\text{F})(12\text{V}) = 36\mu\text{C}$.
- (b) $Q_2 = Q_{12} = C_{12}(12\text{V}) = (1\mu\text{F})(12\text{V}) = 12\mu\text{C}$.

Intermediate Exam II: Problem #2 (Spring '06)



Consider the two-loop circuit shown.

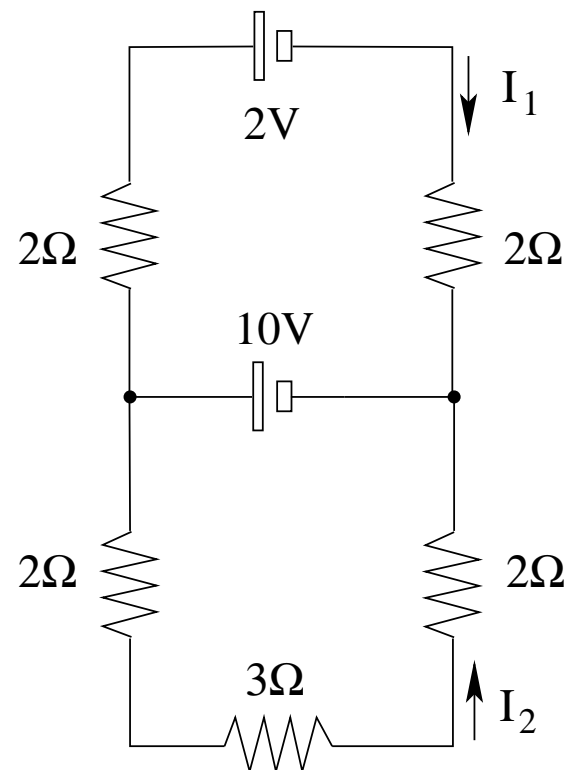- (a) Find the current I_1 .
- (b) Find the current I_2 .



Solution:

$$(a) \quad -(2\Omega)(I_1) + 10V - (2\Omega)(I_1) - 2V = 0 \quad \Rightarrow \quad I_1 = \frac{8V}{4\Omega} = 2A.$$


$$(b) \quad -(2\Omega)(I_2) + 10V - (2\Omega)(I_2) - (3\Omega)(I_2) = 0 \quad \Rightarrow \quad I_2 = \frac{10V}{7\Omega} = 1.43A.$$

Intermediate Exam II: Problem #3 (Spring '06)



In this RC circuit the switch S is initially open as shown.

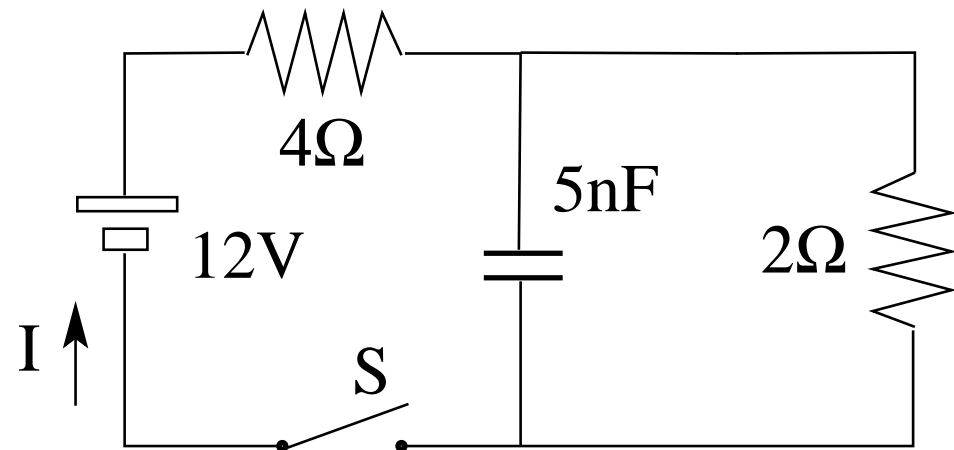- (a) Find the current I right after the switch has been closed.
- (b) Find the current I a very long time later.



Solution:


- (a) No current through 2Ω -resistor: $I = \frac{12\text{V}}{4\Omega} = 3\text{A}$.
- (b) No current through capacitor: $I = \frac{12\text{V}}{6\Omega} = 2\text{A}$.

Intermediate Exam II: Problem #4 (Spring '06)



A current loop in the form of a right triangle is placed in a uniform magnetic field of magnitude $B = 30\text{mT}$ as shown. The current in the loop is $I = 0.4\text{A}$ in the direction indicated.

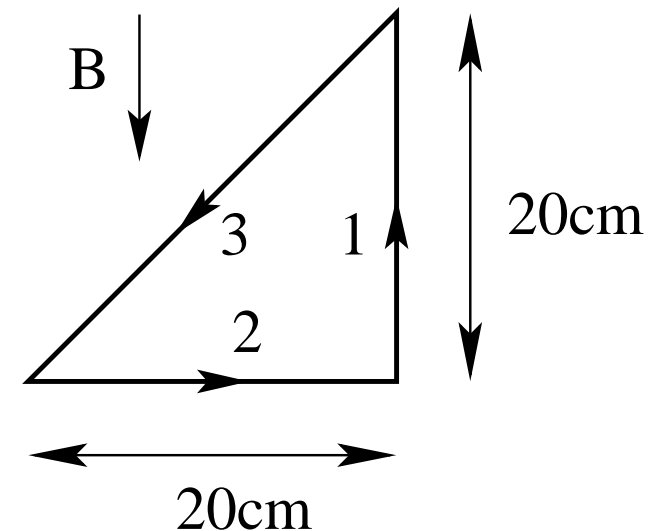- (a) Find magnitude and direction of the force \vec{F}_1 on side 1 of the triangle.
- (b) Find magnitude and direction of the force \vec{F}_2 on side 2 of the triangle.



Solution:

- (a) $\vec{F}_1 = I\vec{L} \times \vec{B} = 0$ (angle between \vec{L} and \vec{B} is 180°).
- (b) $F_2 = ILB = (0.4\text{A})(0.2\text{m})(30 \times 10^{-3}\text{T}) = 2.4 \times 10^{-3}\text{N}$.
Direction of \vec{F}_2 : \otimes (into plane).