


Intermediate Exam III: Problem #1 (Spring '06)



Consider two infinitely long, straight wires with currents of equal magnitude $I_1 = I_2 = 5A$ in the directions shown.

Find the direction (in/out) and the magnitude of the magnetic fields B_1 and B_2 at the points marked in the graph.

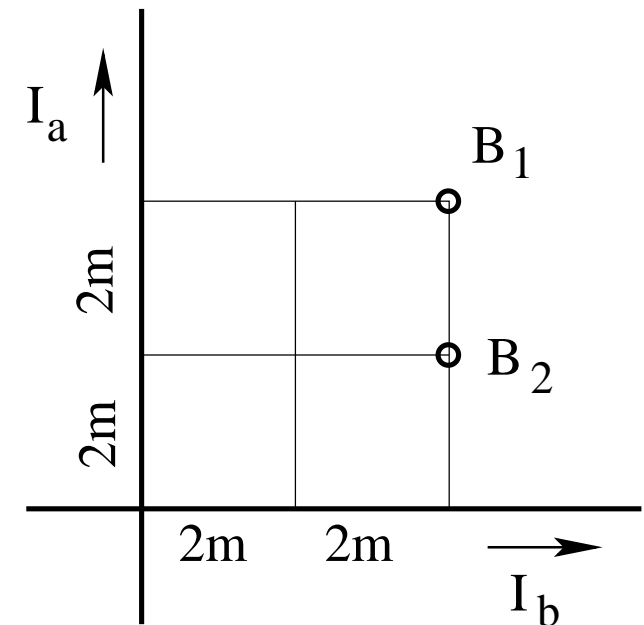- $B_1 = \frac{\mu_0}{2\pi} \left(\frac{5A}{4m} - \frac{5A}{4m} \right) = 0$ (no direction).
- $B_2 = \frac{\mu_0}{2\pi} \left(\frac{5A}{2m} - \frac{5A}{4m} \right) = 0.25\mu T$ (out of plane).




Intermediate Exam III: Problem #2 (Spring '06)



A conducting loop in the shape of a square with area $A = 4\text{m}^2$ and resistance $R = 5\Omega$ is placed in the yz -plane as shown. A time-dependent magnetic field $\mathbf{B} = B_x \hat{\mathbf{i}}$ is present. The dependence of B_x on time is shown graphically.

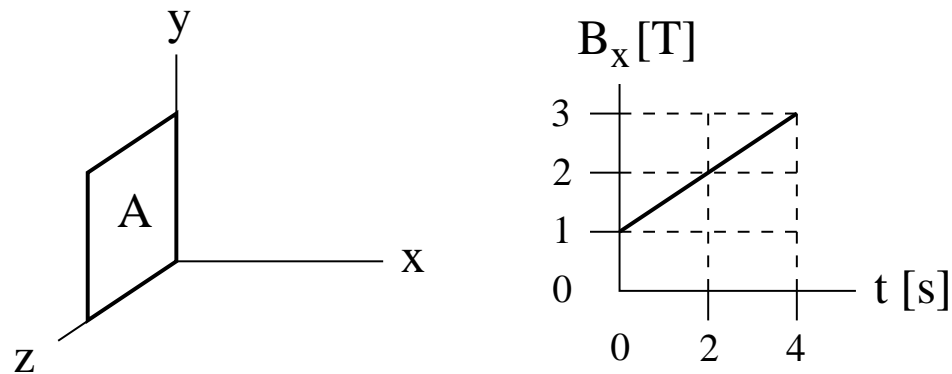- (a) Find the magnetic flux Φ_B through the loop at time $t = 0$.
(b) Find magnitude and direction (cw/ccw) of the induced current I at time $t = 2\text{s}$.



Choice of area vector: $\odot/\otimes \Rightarrow$ positive direction = ccw/cw.

(a) $\Phi_B = \pm(1\text{T})(4\text{m}^2) = \pm 4\text{Tm}^2$.


(b) $\frac{d\Phi_B}{dt} = \pm(0.5\text{T/s})(4\text{m}^2) = \pm 2\text{V} \quad \Rightarrow \quad \mathcal{E} = -\frac{d\Phi_B}{dt} = \mp 2\text{V}.$

$\Rightarrow I = \frac{\mathcal{E}}{R} = \mp \frac{2\text{V}}{5\Omega} = \mp 0.4\text{A} \quad (\text{cw}).$

Intermediate Exam III: Problem #3 (Spring '06)



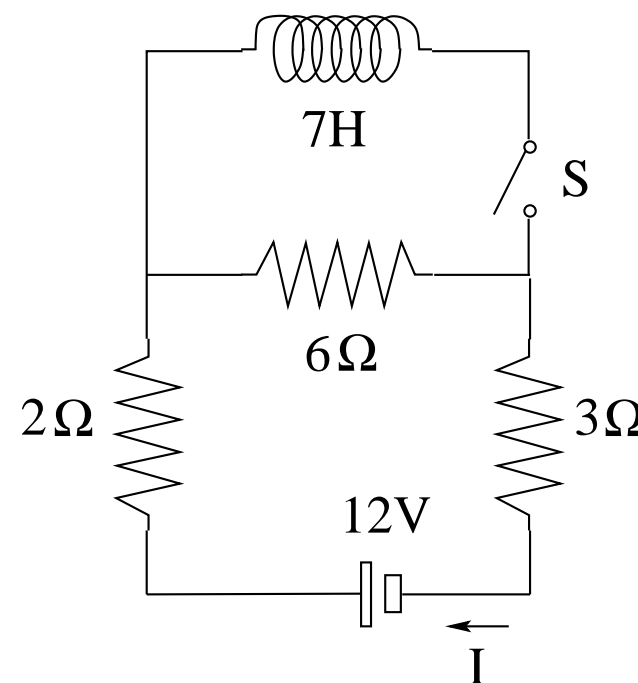In the circuit shown the switch S is initially open.
Find the current I through the battery
(a) while the switch is open,
(b) immediately after the switch has been closed,
(c) a very long time later.



$$(a) \quad I = \frac{12\text{V}}{2\Omega + 3\Omega + 6\Omega} = 1.09\text{A}.$$

$$(b) \quad I = \frac{12\text{V}}{2\Omega + 3\Omega + 6\Omega} = 1.09\text{A}.$$


$$(c) \quad I = \frac{12\text{V}}{2\Omega + 3\Omega} = 2.4\text{A}.$$

Intermediate Exam III: Problem #4 (Spring '06)



Consider the circuit shown. The *ac* voltage supplied is $\mathcal{E} = \mathcal{E}_{max} \cos(\omega t)$ with $\mathcal{E}_{max} = 170\text{V}$ and $\omega = 377\text{rad/s}$.

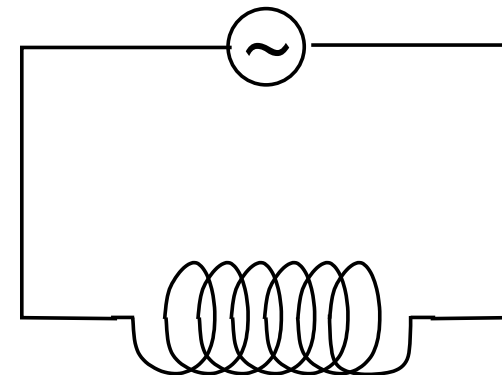- (a) What is the maximum value I_{max} of the current?
- (b) What is the emf \mathcal{E} at $t = 0.02\text{s}$?
- (c) What is the current I at $t = 0.02\text{s}$?



$$L = 30\text{mH}$$

$$(a) \quad I_{max} = \frac{\mathcal{E}_{max}}{X_L} = \frac{\mathcal{E}_{max}}{\omega L} = \frac{170\text{V}}{11.3\Omega} = 15.0\text{A}.$$

$$(b) \quad \mathcal{E} = \mathcal{E}_{max} \cos(7.54\text{rad}) = (170\text{V})(0.309) = 52.5\text{V}.$$

$$(c) \quad I = I_{max} \cos(7.54\text{rad} - \pi/2) = (15.0\text{A})(0.951) = 14.3\text{A}.$$