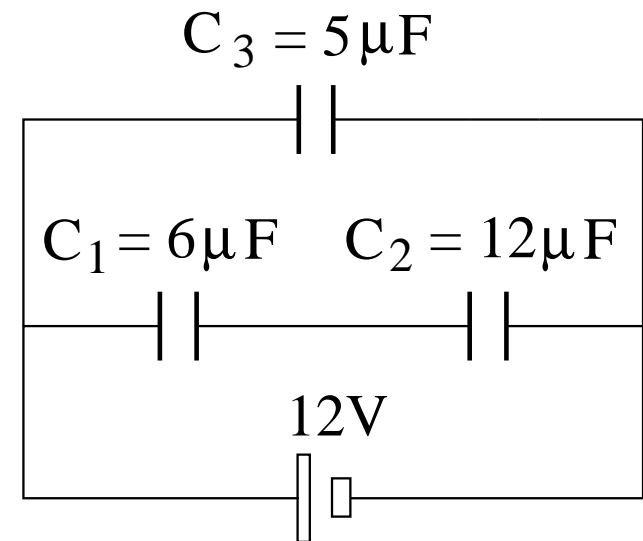


Unit Exam II: Problem #1 (Spring '08)



The circuit of capacitors is at equilibrium.

- Find the charge Q_1 on capacitor 1 and the charge Q_2 on capacitor 2.
- Find the voltage V_1 across capacitor 1 and the voltage V_2 across capacitor 2.
- Find the charge Q_3 and the energy U_3 on capacitor 3.



Unit Exam II: Problem #1 (Spring '08)



The circuit of capacitors is at equilibrium.

- Find the charge Q_1 on capacitor 1 and the charge Q_2 on capacitor 2.
- Find the voltage V_1 across capacitor 1 and the voltage V_2 across capacitor 2.
- Find the charge Q_3 and the energy U_3 on capacitor 3.

Solution:

$$(a) C_{12} = \left(\frac{1}{6\mu\text{F}} + \frac{1}{12\mu\text{F}} \right)^{-1} = 4\mu\text{F},$$


$$Q_1 = Q_2 = Q_{12} = (4\mu\text{F})(12\text{V}) = 48\mu\text{C}.$$

$$(b) V_1 = \frac{Q_1}{C_1} = \frac{48\mu\text{C}}{6\mu\text{F}} = 8\text{V},$$

$$V_2 = \frac{Q_2}{C_2} = \frac{48\mu\text{C}}{12\mu\text{F}} = 4\text{V}.$$

$$(c) Q_3 = (5\mu\text{F})(12\text{V}) = 60\mu\text{C},$$
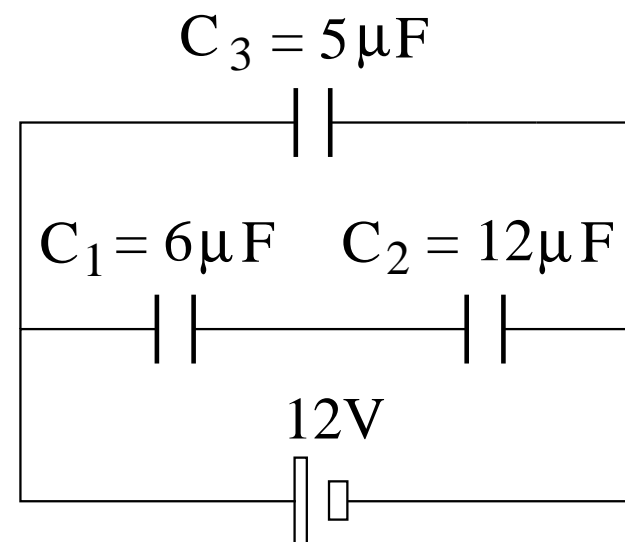
$$U_3 = \frac{1}{2}(5\mu\text{F})(12\text{V})^2 = 360\mu\text{J}.$$




Unit Exam II: Problem #2 (Spring '08)



Consider the electric circuit shown. Find the current I_1 through resistor 1 and the voltage V_1 across it

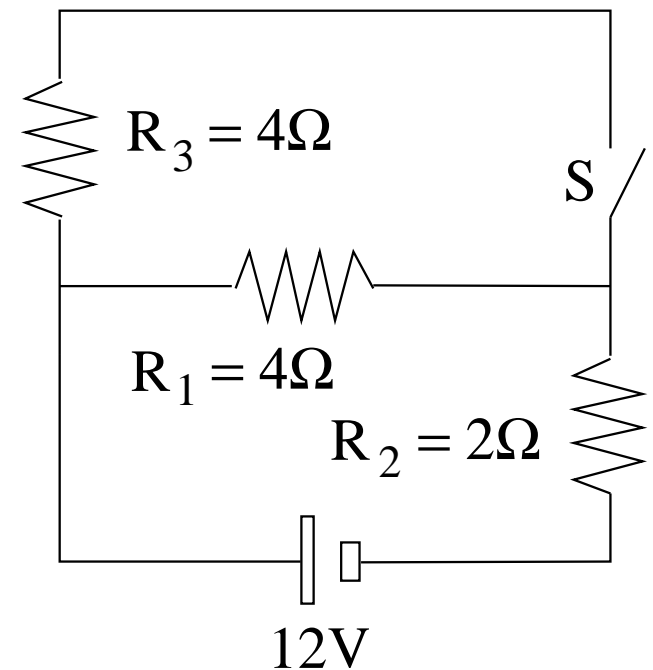- (a) when the switch S is open,
- (b) when the switch S is closed.
- (c) Find the equivalent resistance R_{eq} of the circuit and the total power P dissipated in it when the switch S is closed.



Unit Exam II: Problem #2 (Spring '08)



Consider the electric circuit shown. Find the current I_1 through resistor 1 and the voltage V_1 across it

- (a) when the switch S is open,
- (b) when the switch S is closed.
- (c) Find the equivalent resistance R_{eq} of the circuit and the total power P dissipated in it when the switch S is closed.


Solution:

$$(a) \quad I_1 = \frac{12V}{4\Omega + 2\Omega} = 2A, \quad V_1 = (4\Omega)(2A) = 8V.$$

$$(b) \quad I_1 = \frac{1}{2} \frac{12V}{2\Omega + 2\Omega} = 1.5A, \quad V_1 = (4\Omega)(1.5A) = 6V.$$

$$(c) \quad R_{eq} = \left(\frac{1}{4\Omega} + \frac{1}{4\Omega} \right)^{-1} + 2\Omega = 4\Omega,$$

$$P = \frac{(12V)^2}{4\Omega} = 36W.$$

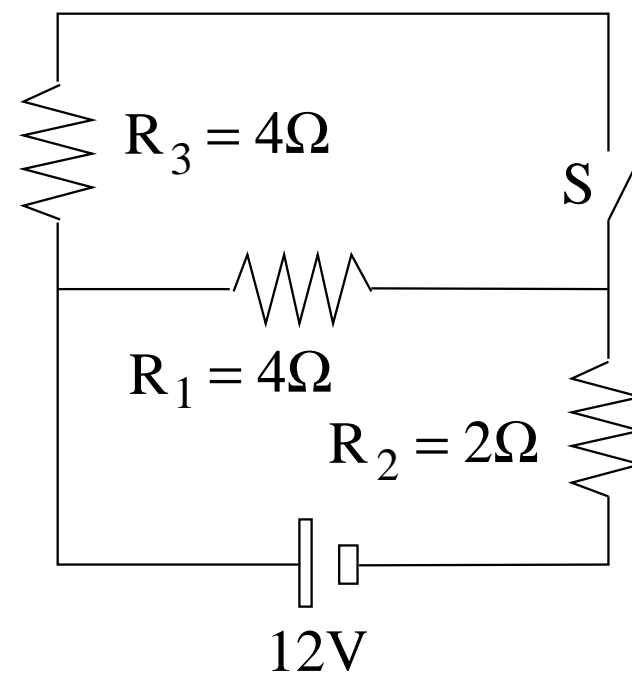


Unit Exam II: Problem #3 (Spring '08)



Consider the electric circuit shown. Find the currents I_1 , I_2 , and I_3

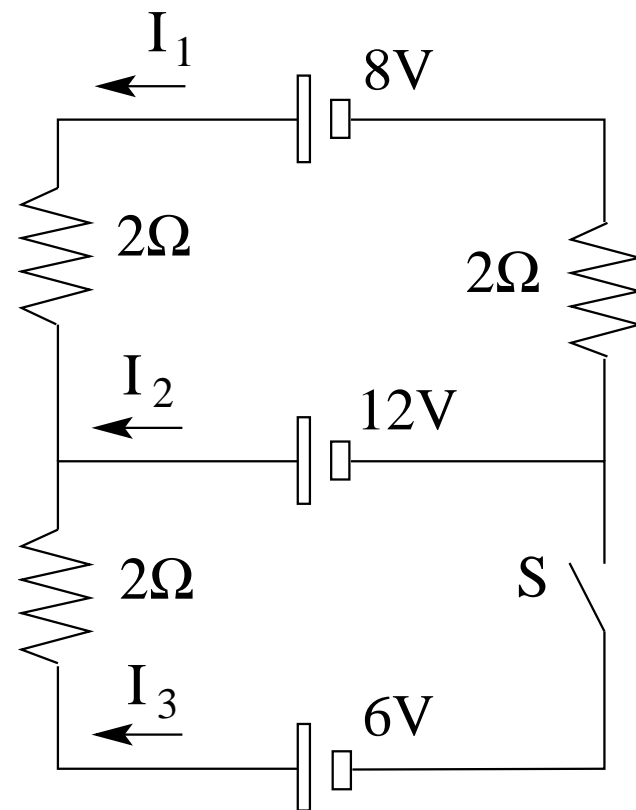- (a) with the switch S open,
- (b) with the switch S closed.



Unit Exam II: Problem #3 (Spring '08)



Consider the electric circuit shown. Find the currents I_1 , I_2 , and I_3

- (a) with the switch S open,
- (b) with the switch S closed.

Solution:

(a)
$$I_1 = \frac{8V - 12V}{4\Omega} = -1A,$$
$$I_2 = -I_1 = +1A.$$
$$I_3 = 0.$$

(b)
$$I_1 = \frac{8V - 12V}{4\Omega} = -1A,$$
$$I_3 = \frac{6V - 12V}{2\Omega} = -3A.$$
$$I_2 = -I_1 - I_3 = +4A.$$

