
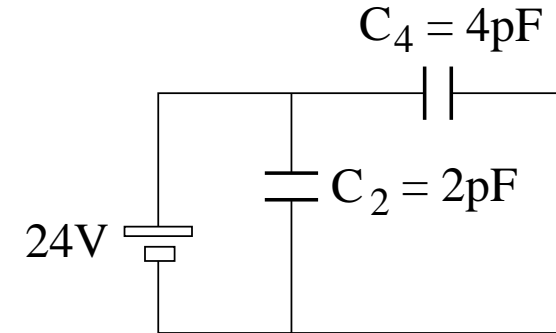


## Unit Exam II: Problem #1 (Spring '11)

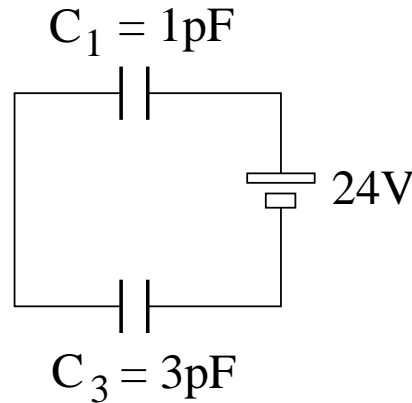

Both capacitor circuits are at equilibrium.

- (a) Find the charge  $Q_1$  on capacitor 1.
- (b) Find the voltage  $V_3$  across capacitor 3.
- (c) Find the charge  $Q_2$  on capacitor 2.
- (d) Find the energy  $U_4$  stored on capacitor 4.





# Unit Exam II: Problem #1 (Spring '11)



Both capacitor circuits are at equilibrium.

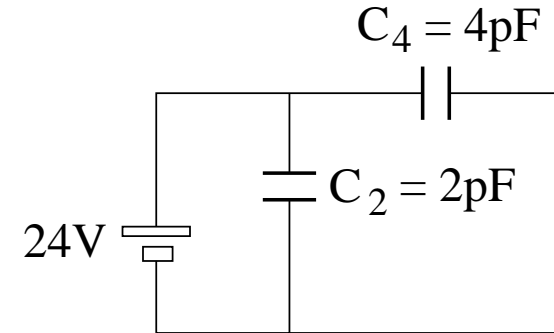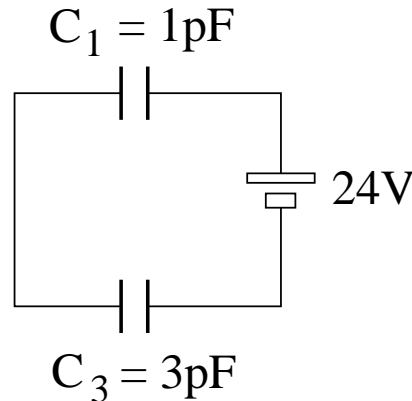- (a) Find the charge  $Q_1$  on capacitor 1.
- (b) Find the voltage  $V_3$  across capacitor 3.
- (c) Find the charge  $Q_2$  on capacitor 2.
- (d) Find the energy  $U_4$  stored on capacitor 4.



**Solution:**

$$(a) \quad C_{13} = \left( \frac{1}{C_1} + \frac{1}{C_3} \right)^{-1} = 0.75\text{pF}, \quad Q_1 = Q_3 = Q_{13} = (24\text{V})(0.75\text{pF}) = 18\text{pC}.$$

$$(b) \quad V_3 = \frac{Q_3}{C_3} = \frac{18\text{pC}}{3\text{pF}} = 6\text{V}.$$

$$(c) \quad Q_2 = (24\text{V})(2\text{pF}) = 48\text{pC}.$$


$$(d) \quad U_4 = \frac{1}{2}C_4V_4^2 = \frac{1}{2}(4\text{pF})(24\text{V})^2 = 1152\text{pJ}.$$

## Unit Exam II: Problem #2 (Spring '11)



Consider the resistor circuit shown.

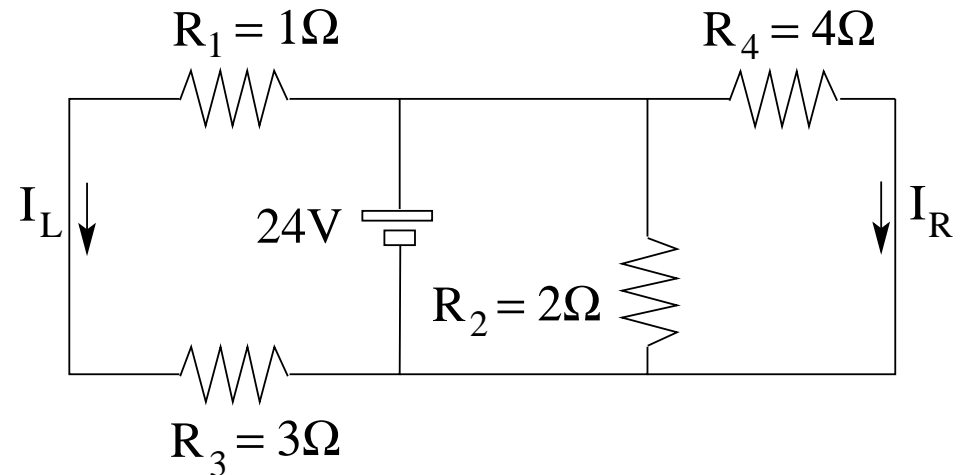- (a) Find the current  $I_L$  on the left.
- (b) Find the current  $I_R$  on the right.
- (c) Find the equivalent resistance  $R_{eq}$  of all four resistors.
- (d) Find the power  $P_2$  dissipated in resistor 2.



## Unit Exam II: Problem #2 (Spring '11)



Consider the resistor circuit shown.

- (a) Find the current  $I_L$  on the left.
- (b) Find the current  $I_R$  on the right.
- (c) Find the equivalent resistance  $R_{eq}$  of all four resistors.
- (d) Find the power  $P_2$  dissipated in resistor 2.


**Solution:**

$$(a) \quad I_L = \frac{24V}{1\Omega + 3\Omega} = 6A.$$

$$(b) \quad I_R = \frac{24V}{4\Omega} = 6A.$$

$$(c) \quad R_{eq} = \left( \frac{1}{1\Omega + 3\Omega} + \frac{1}{2\Omega} + \frac{1}{4\Omega} \right)^{-1} = 1\Omega.$$
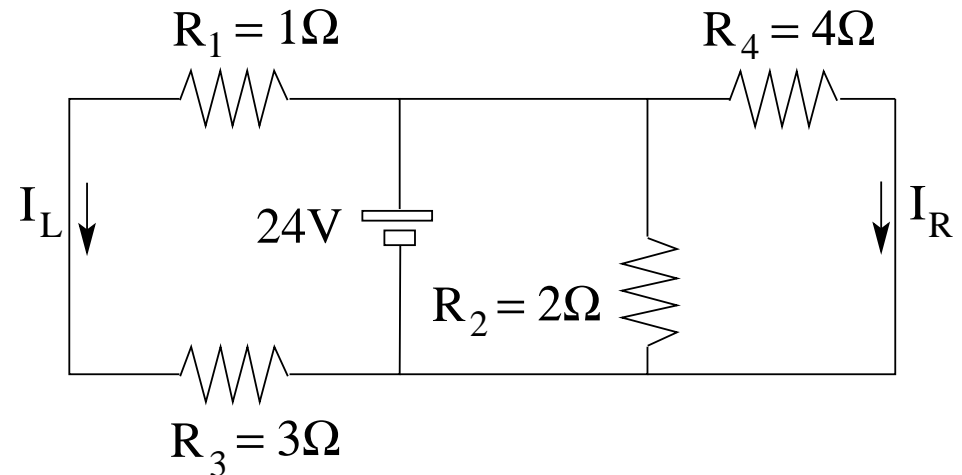
$$(d) \quad P_2 = \frac{(24V)^2}{2\Omega} = 288W.$$




## Unit Exam II: Problem #3 (Spring '11)



Consider the electric circuit shown.

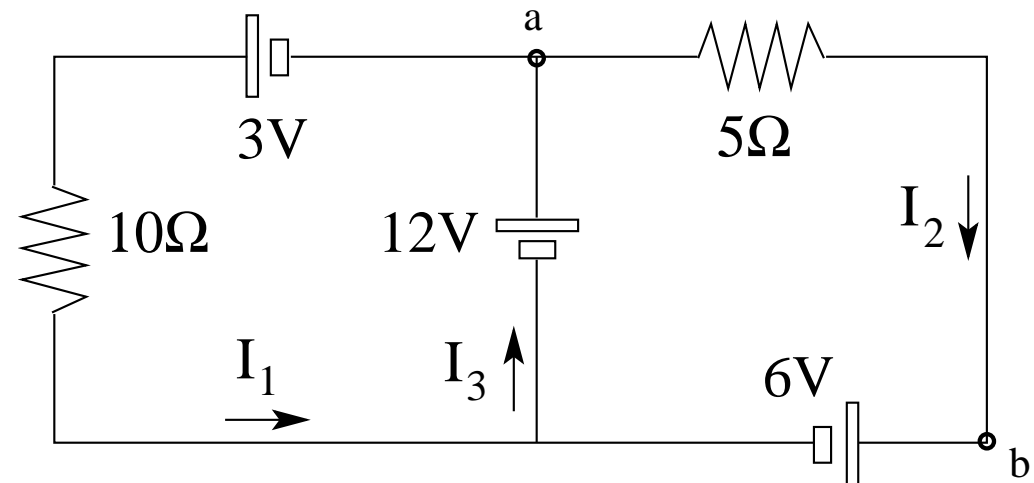- (a) Find the current  $I_1$ .
- (b) Find the current  $I_2$ .
- (c) Find the current  $I_3$ .
- (d) Find the potential difference  $V_a - V_b$ .




## Unit Exam II: Problem #3 (Spring '11)



Consider the electric circuit shown.

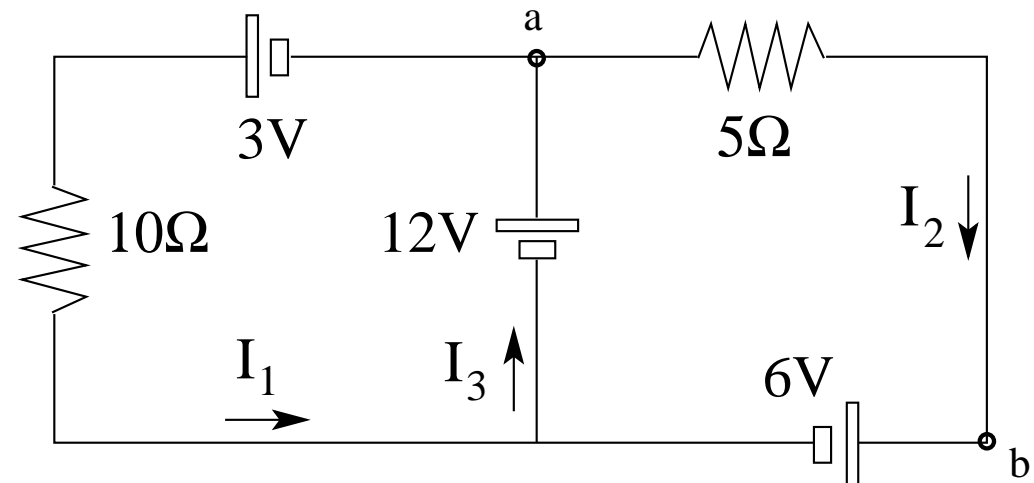- (a) Find the current  $I_1$ .
- (b) Find the current  $I_2$ .
- (c) Find the current  $I_3$ .
- (d) Find the potential difference  $V_a - V_b$ .



**Solution:**

$$(a) \quad 12V + 3V - I_1(10\Omega) = 0 \quad \Rightarrow \quad I_1 = \frac{15V}{10\Omega} = 1.5A.$$

$$(b) \quad -6V + 12V - I_2(5\Omega) = 0 \quad \Rightarrow \quad I_2 = \frac{6V}{5\Omega} = 1.2A.$$

$$(c) \quad I_3 = I_1 + I_2 = 2.7A.$$

$$(d) \quad V_a - V_b = -6V + 12V = 6V.$$