
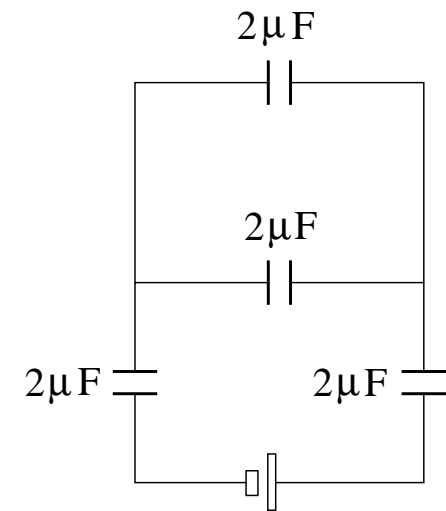


# Unit Exam II: Problem #1 (Spring '12)

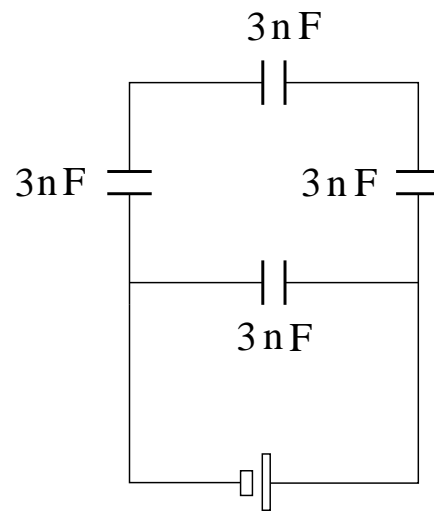



Find the equivalent capacitances  $C_{eq}$  of the two capacitor circuits.


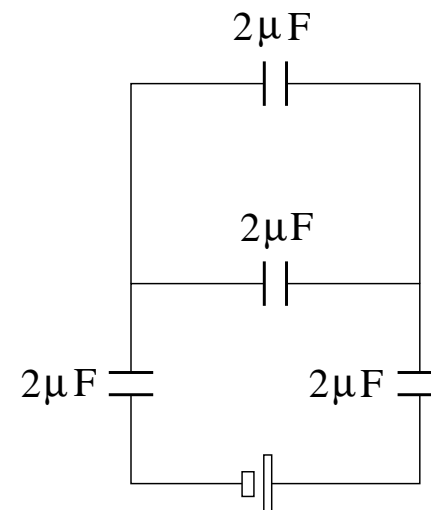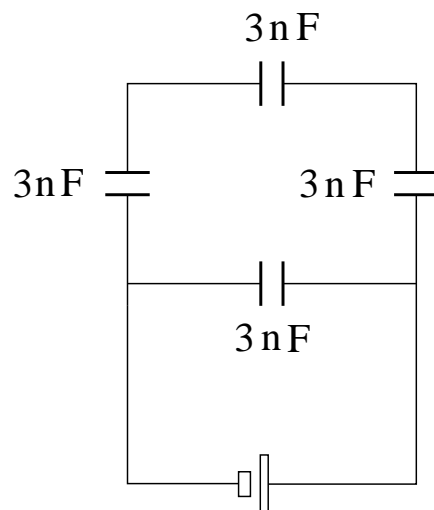
# Unit Exam II: Problem #1 (Spring '12)



Find the equivalent capacitances  $C_{eq}$  of the two capacitor circuits.



**Solution:**


- $C_{eq} = 3\text{nF} + \left( \frac{1}{3\text{nF}} + \frac{1}{3\text{nF}} + \frac{1}{3\text{nF}} \right)^{-1} = 4\text{nF}.$
- $C_{eq} = \left( \frac{1}{2\mu\text{F}} + \frac{1}{2\mu\text{F} + 2\mu\text{F}} + \frac{1}{2\mu\text{F}} \right)^{-1} = \frac{4}{5}\mu\text{F}.$

## Unit Exam II: Problem #2 (Spring '12)



Consider a parallel-plate capacitor of capacitance  $C = 6\text{pF}$  with plates separated a distance  $d = 1\text{mm}$  and a potential difference  $V = V_+ - V_- = 3\text{V}$  between them.

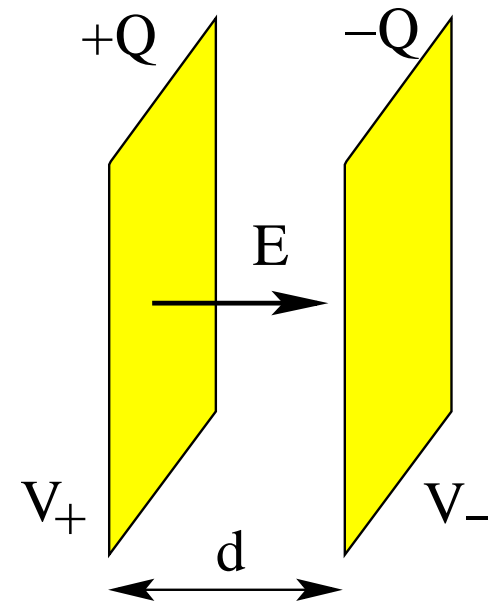- (a) Find the magnitude  $E$  of the electric field between the plates.
- (b) Find the amount  $Q$  of charge on each plate.
- (c) Find the energy  $U$  stored on the capacitor.
- (d) Find the area  $A$  of each plate.




## Unit Exam II: Problem #2 (Spring '12)



Consider a parallel-plate capacitor of capacitance  $C = 6\text{pF}$  with plates separated a distance  $d = 1\text{mm}$  and a potential difference  $V = V_+ - V_- = 3\text{V}$  between them.

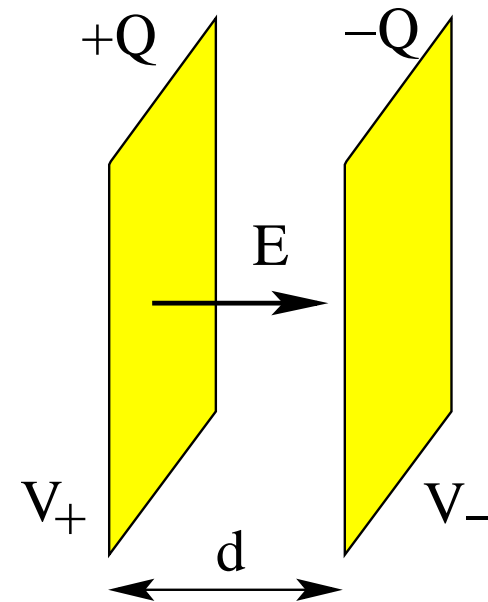- (a) Find the magnitude  $E$  of the electric field between the plates.
- (b) Find the amount  $Q$  of charge on each plate.
- (c) Find the energy  $U$  stored on the capacitor.
- (d) Find the area  $A$  of each plate.



**Solution:**

$$(a) \quad E = \frac{V}{d} = \frac{3\text{V}}{1\text{mm}} = 3000\text{V/m.}$$

$$(b) \quad Q = CV = (6\text{pF})(3\text{V}) = 18\text{pC.}$$


$$(c) \quad U = \frac{1}{2}QV = 0.5(18\text{pC})(3\text{V}) = 27\text{pJ.}$$

$$(d) \quad A = \frac{Cd}{\epsilon_0} = \frac{(6\text{pF})(1\text{mm})}{8.85 \times 10^{-12}\text{C}^2\text{N}^{-1}\text{m}^{-2}} = 6.78 \times 10^{-4}\text{m}^2.$$
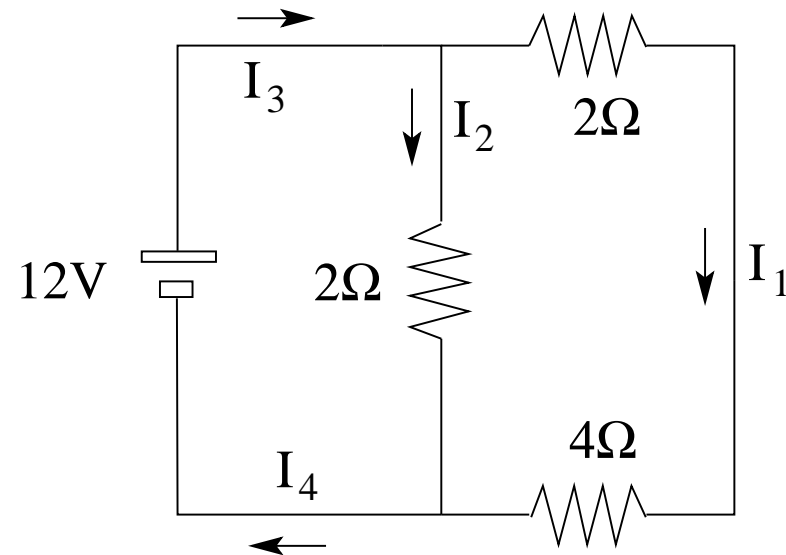
## Unit Exam II: Problem #3 (Spring '12)




Consider the electric circuit shown. Find the currents  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_4$


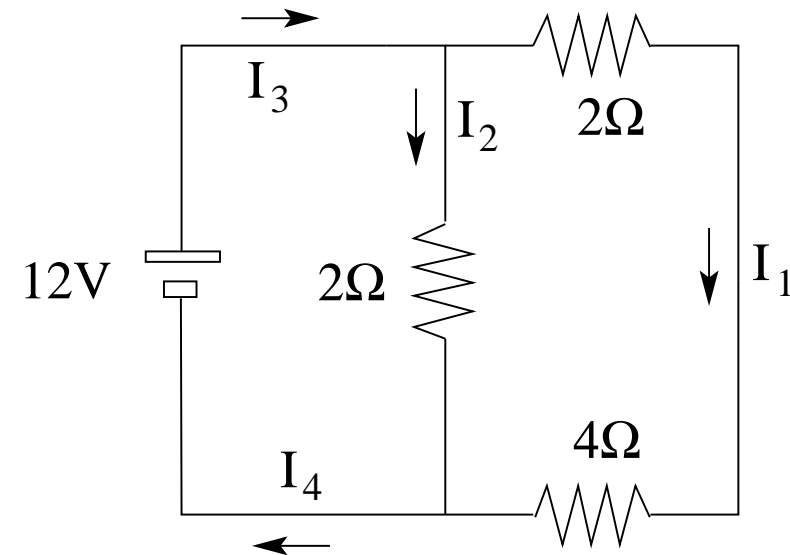
## Unit Exam II: Problem #3 (Spring '12)



Consider the electric circuit shown. Find the currents  $I_1$ ,  $I_2$ ,  $I_3$ , and  $I_4$




**Solution:**

- $I_1 = \frac{12\text{V}}{2\Omega + 4\Omega} = 2\text{A}.$
- $I_2 = \frac{12\text{V}}{2\Omega} = 6\text{A}.$
- $I_3 = I_4 = I_1 + I_2 = 8\text{A}.$
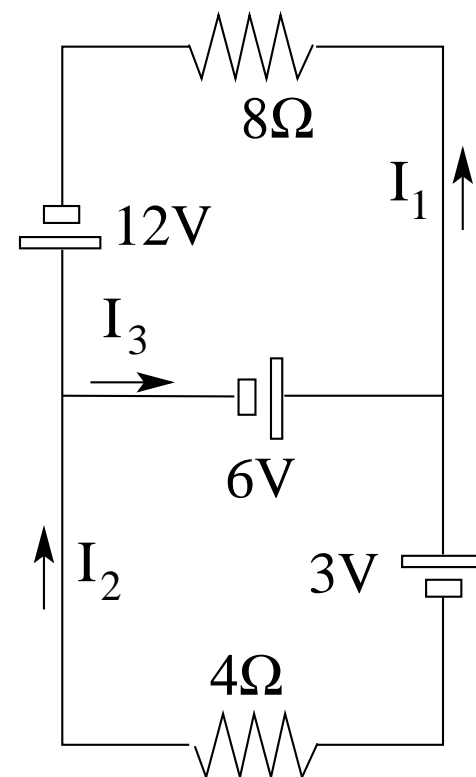
## Unit Exam II: Problem #4 (Spring '12)




Consider the electric circuit shown. Find the currents  $I_1$ ,  $I_2$ , and  $I_3$


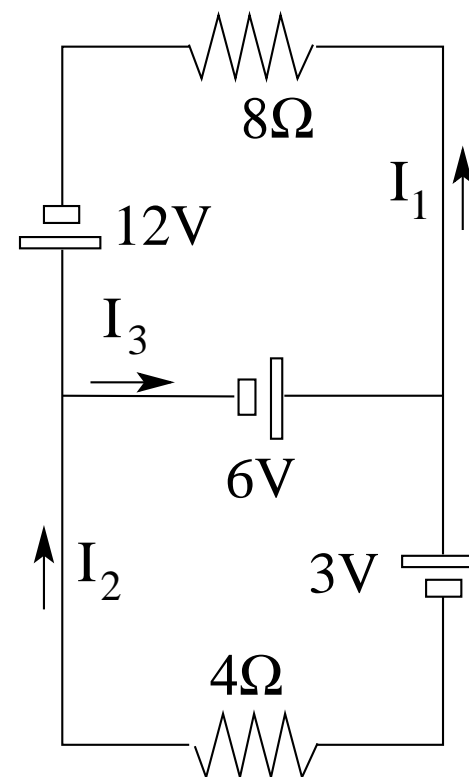
## Unit Exam II: Problem #4 (Spring '12)



Consider the electric circuit shown. Find the currents  $I_1$ ,  $I_2$ , and  $I_3$



**Solution:**

- $12V + 6V - (8\Omega)I_1 = 0 \Rightarrow I_1 = \frac{9}{4}A = 2.25A.$
- $6V - 3V - (4\Omega)I_2 = 0 \Rightarrow I_2 = \frac{3}{4}A = 0.75A.$
- $I_3 = I_1 + I_2 = 3.00A.$