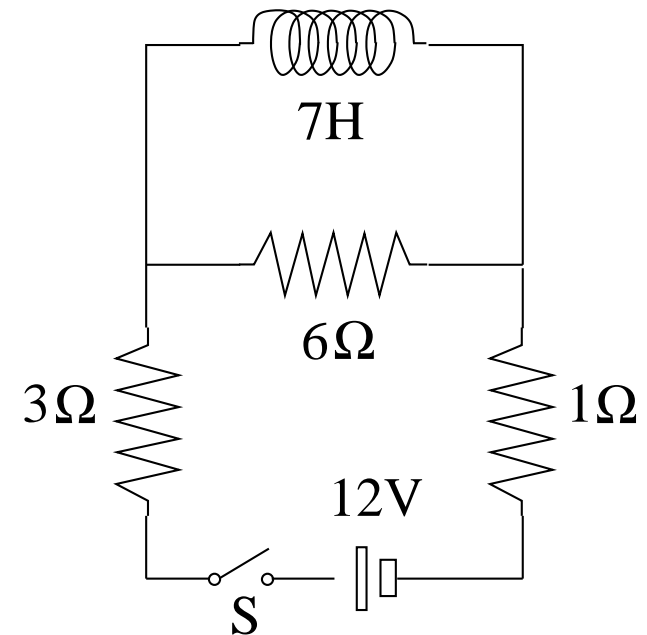


# Unit Exam IV: Problem #1 (Spring '12)



In the circuit shown we close the switch  $S$  at time  $t = 0$ . Find the current  $I_L$  through the inductor and the voltage  $V_6$  across the  $6\Omega$ -resistor

- (a) immediately after the switch has been closed,
- (b) a very long time later.



# Unit Exam IV: Problem #1 (Spring '12)




In the circuit shown we close the switch  $S$  at time  $t = 0$ . Find the current  $I_L$  through the inductor and the voltage  $V_6$  across the  $6\Omega$ -resistor

- (a) immediately after the switch has been closed,
- (b) a very long time later.

**Solution:**

(a)  $I_L = 0, \quad I_6 = \frac{12V}{10\Omega} = 1.2A, \quad V_6 = (6\Omega)(1.2A) = 7.2V.$

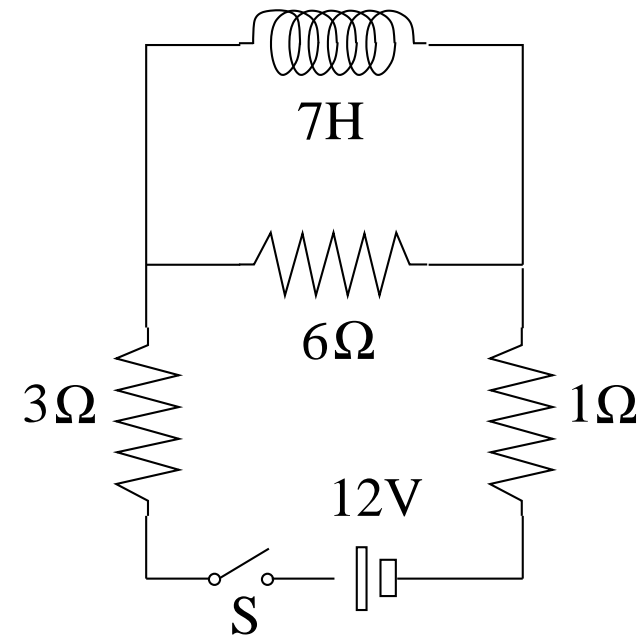(b)  $I_L = \frac{12V}{4\Omega} = 3A, \quad V_6 = 0.$




## Unit Exam IV: Problem #2 (Spring '12)



At time  $t = 0$  the capacitor is charged to  $Q_{max} = 4\mu\text{C}$  and the switch is being closed. The charge on the capacitor begins to decrease and the current through the inductor begins to increase.

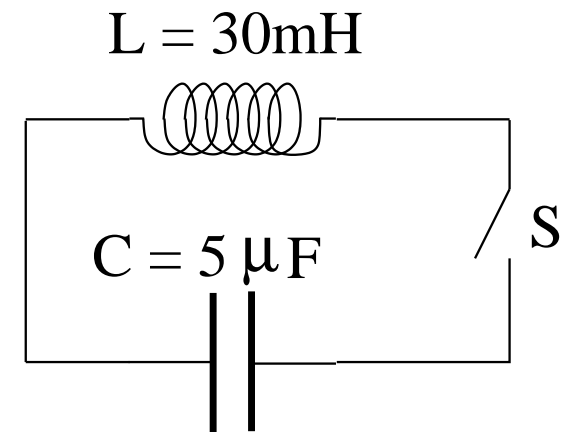- (a) At what time  $t_1$  is the capacitor discharged for the first time?
- (b) At what time  $t_2$  has the current through the inductor returned to zero for the first time?
- (c) What is the maximum energy stored in the capacitor at any time?
- (d) What is the maximum energy stored in the inductor at any time?



## Unit Exam IV: Problem #2 (Spring '12)



At time  $t = 0$  the capacitor is charged to  $Q_{max} = 4\mu\text{C}$  and the switch is being closed. The charge on the capacitor begins to decrease and the current through the inductor begins to increase.

- (a) At what time  $t_1$  is the capacitor discharged for the first time?
- (b) At what time  $t_2$  has the current through the inductor returned to zero for the first time?
- (c) What is the maximum energy stored in the capacitor at any time?
- (d) What is the maximum energy stored in the inductor at any time?


**Solution:**

$$(a) T = \frac{2\pi}{\omega} = 2\pi\sqrt{LC} = 2.43\text{ms}, \quad t_1 = \frac{T}{4} = 0.608\text{ms}.$$

$$(b) t_2 = \frac{T}{2} = 1.22\text{ms}.$$

$$(c) U_C^{max} = \frac{Q_{max}^2}{2C} = 1.6\mu\text{J}.$$
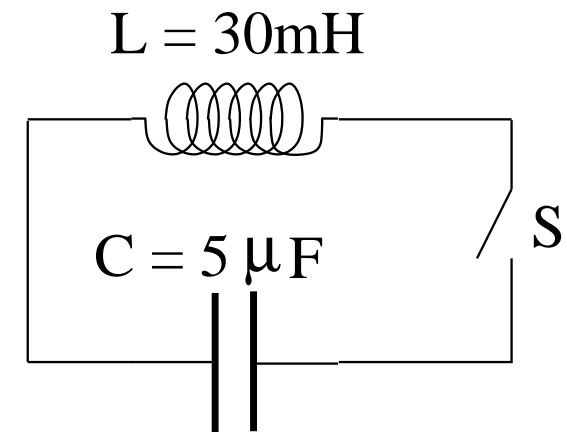
$$(d) U_L^{max} = U_C^{max} = 1.6\mu\text{J} \quad (\text{energy conservation.})$$




## Unit Exam IV: Problem #3 (Spring '12)



The *ac* voltage supplied in the circuit shown is  $\mathcal{E} = \mathcal{E}_{max} \cos(\omega t)$  with  $\mathcal{E}_{max} = 170\text{V}$  and  $\omega = 377\text{rad/s}$ .

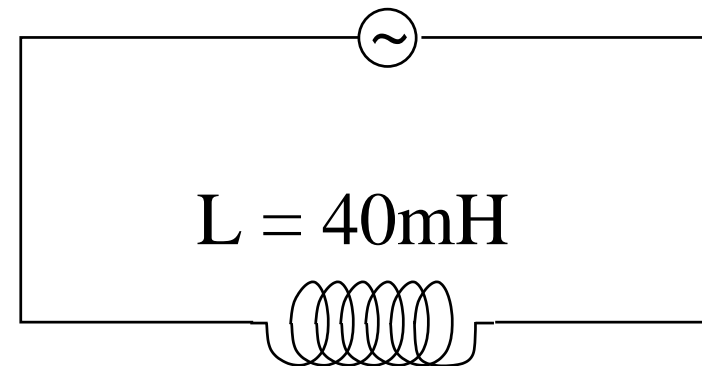- (a) What is the maximum value  $I_{max}$  of the current?
- (b) What is the emf  $\mathcal{E}(t)$  at  $t = 5\text{ms}$ ?
- (c) What is the current  $I(t)$  at  $t = 5\text{ms}$ ?
- (d) What is the power transfer  $P(t)$  between *ac* source and device at  $t = 5\text{ms}$ ?




## Unit Exam IV: Problem #3 (Spring '12)



The *ac* voltage supplied in the circuit shown is  $\mathcal{E} = \mathcal{E}_{max} \cos(\omega t)$  with  $\mathcal{E}_{max} = 170\text{V}$  and  $\omega = 377\text{rad/s}$ .

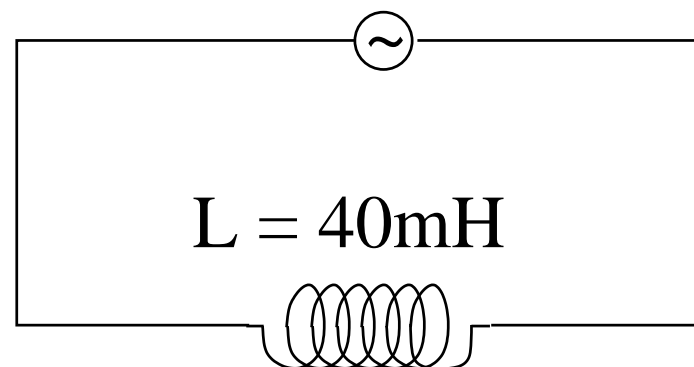- (a) What is the maximum value  $I_{max}$  of the current?
- (b) What is the emf  $\mathcal{E}(t)$  at  $t = 5\text{ms}$ ?
- (c) What is the current  $I(t)$  at  $t = 5\text{ms}$ ?
- (d) What is the power transfer  $P(t)$  between *ac* source and device at  $t = 5\text{ms}$ ?



**Solution:**

$$(a) I_{max} = \frac{\mathcal{E}_{max}}{\omega L} = \frac{170\text{V}}{(377\text{rad/s})(40\text{mH})} = 11.3\text{A}.$$

$$(b) \mathcal{E} = (170\text{V}) \cos(1.885\text{rad}) = (170\text{V})(-0.309) = -52.5\text{V}.$$

$$(c) I = (11.3\text{A}) \cos(1.885\text{rad} - \pi/2) = (11.3\text{A}) \cos(0.314) = (11.3\text{A})(0.951) = 10.7\text{A}.$$

$$(d) P = \mathcal{E}I = (-52.5\text{V})(10.7\text{A}) = -562\text{W}.$$