


Ohm's Law



$$V = RI \text{ with } R = \text{const}$$

satisfied

RESISTOR 

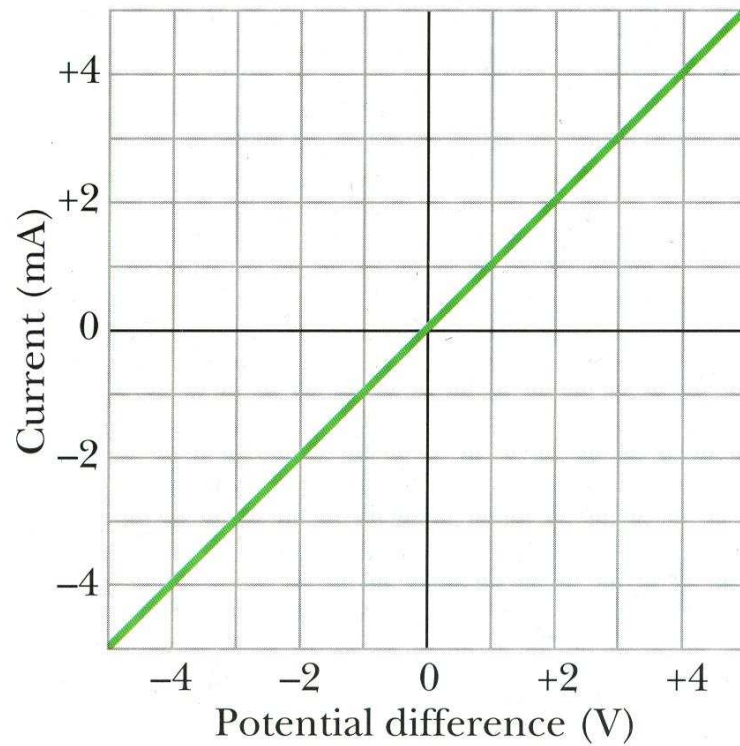

violated

DIODE 

