

Impedances: RLC in Series (1)





$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

resonance at $\omega_0 = \frac{1}{\sqrt{LC}}$

limit $R \rightarrow 0$

$$Z = \left| \omega L - \frac{1}{\omega C} \right|$$

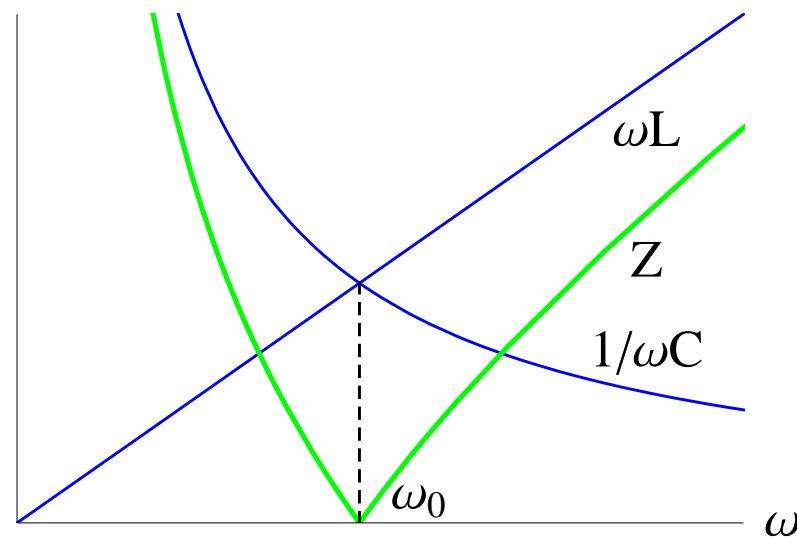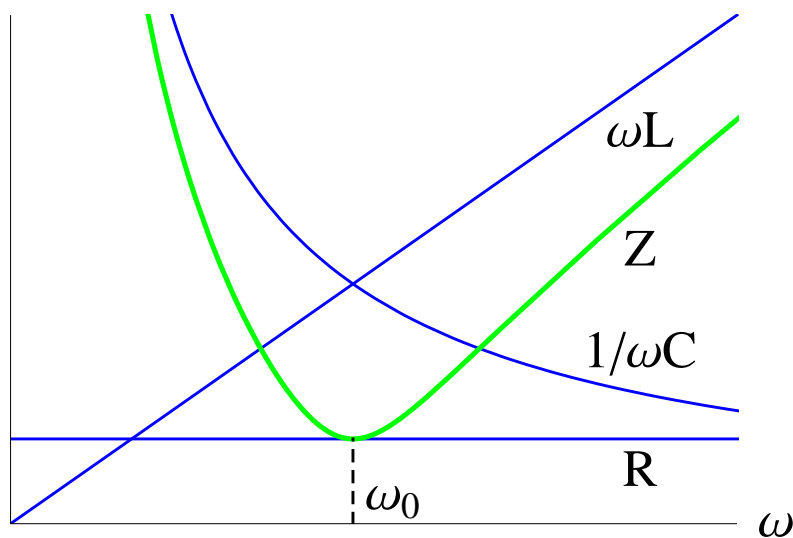


Impedances: RLC in Series (2)



limit $C \rightarrow \infty$

$$Z = \sqrt{R^2 + (\omega L)^2}$$

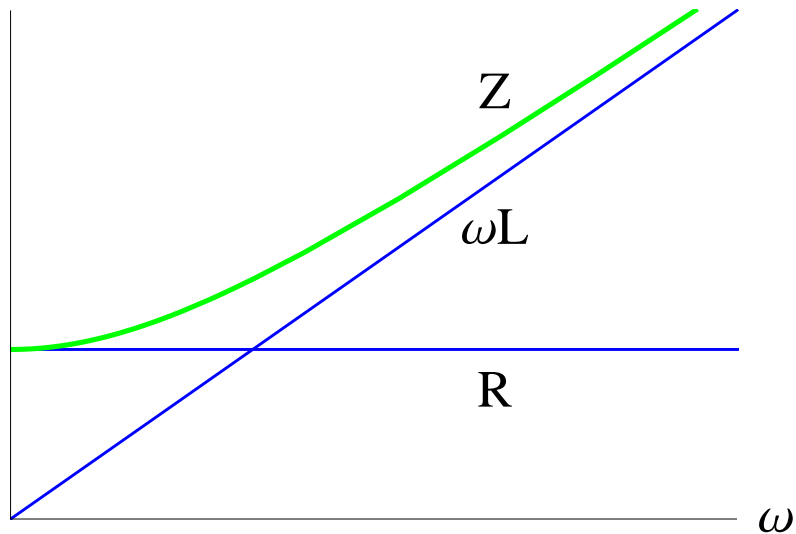

limit $L \rightarrow 0$

$$Z = \sqrt{R^2 + \frac{1}{(\omega C)^2}}$$

