
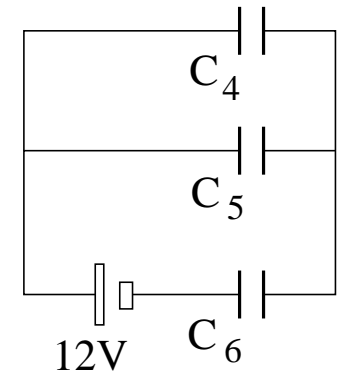


## Unit Exam II: Problem #1 (Fall '14)

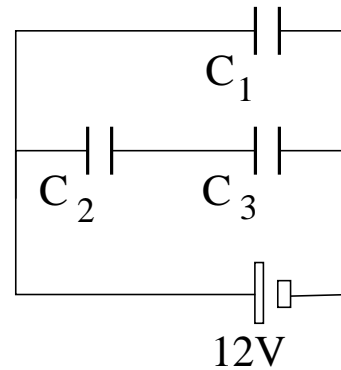

Both capacitor circuits, charged up by batteries as shown, are now at equilibrium. Each of the six capacitors has a  $2\text{pF}$  capacitance.

- (a) Find the equivalent capacitance of the circuit on the left.
- (b) Find the voltages  $V_1$ ,  $V_2$ ,  $V_3$  across capacitors  $C_1$ ,  $C_2$ ,  $C_3$ , respectively.
- (c) Find the equivalent capacitance of the circuit on the right.
- (d) Find the charges  $Q_4$ ,  $Q_5$ ,  $Q_6$  on capacitors  $C_4$ ,  $C_5$ ,  $C_6$ , respectively.




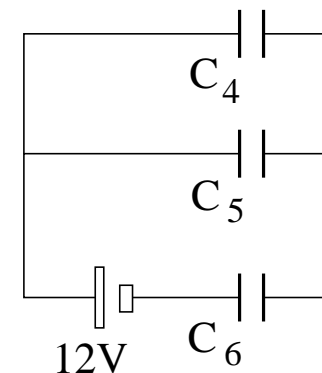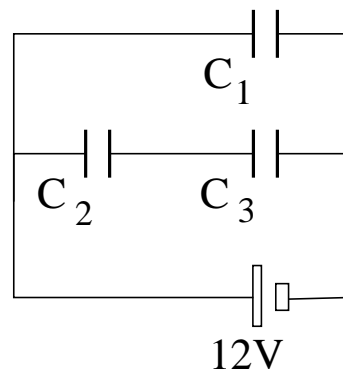
## Unit Exam II: Problem #1 (Fall '14)



Both capacitor circuits, charged up by batteries as shown, are now at equilibrium. Each of the six capacitors has a 2pF capacitance.

- Find the equivalent capacitance of the circuit on the left.
- Find the voltages  $V_1$ ,  $V_2$ ,  $V_3$  across capacitors  $C_1$ ,  $C_2$ ,  $C_3$ , respectively.
- Find the equivalent capacitance of the circuit on the right.
- Find the charges  $Q_4$ ,  $Q_5$ ,  $Q_6$  on capacitors  $C_4$ ,  $C_5$ ,  $C_6$ , respectively.



**Solution:**

$$(a) C_{eq} = 2\text{pF} + \left( \frac{1}{2\text{pF}} + \frac{1}{2\text{pF}} \right)^{-1} = 3\text{pF}.$$

$$(b) V_1 = 12\text{V}, \quad V_2 = V_3 = 6\text{V}$$

$$(c) C_{eq} = \left( \frac{1}{2\text{pF} + 2\text{pF}} + \frac{1}{2\text{pF}} \right)^{-1} = \frac{4}{3}\text{pF}.$$


$$(d) Q_{45} = Q_6 = C_{eq}(12\text{V}) = 16\text{pC} \quad \Rightarrow \quad Q_4 = Q_5 = 8\text{pC}.$$
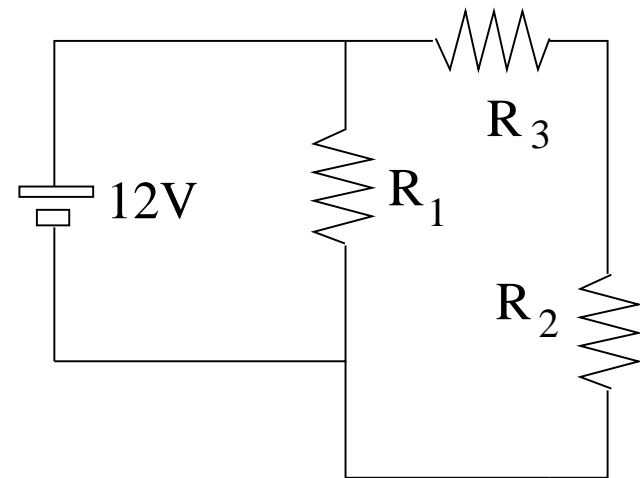
## Unit Exam II: Problem #2 (Fall '14)



Consider the resistor circuit shown with  $R_1 = 5\Omega$ ,  $R_2 = 1\Omega$ , and  $R_3 = 3\Omega$ .

- Find the equivalent resistance  $R_{eq}$ .
- Find the currents  $I_1$ ,  $I_2$ ,  $I_3$  through resistors  $R_1$ ,  $R_2$ ,  $R_3$ , respectively.
- Find the voltages  $V_1$ ,  $V_2$ ,  $V_3$  across resistors  $R_1$ ,  $R_2$ ,  $R_3$ , respectively.




## Unit Exam II: Problem #2 (Fall '14)



Consider the resistor circuit shown with  $R_1 = 5\Omega$ ,  $R_2 = 1\Omega$ , and  $R_3 = 3\Omega$ .

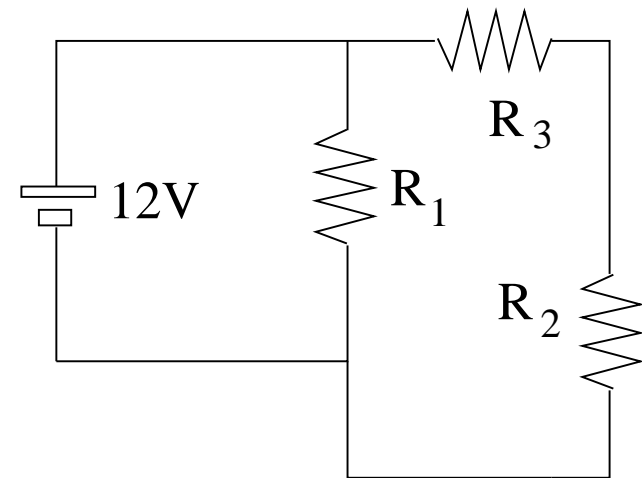- (a) Find the equivalent resistance  $R_{eq}$ .
- (b) Find the currents  $I_1$ ,  $I_2$ ,  $I_3$  through resistors  $R_1$ ,  $R_2$ ,  $R_3$ , respectively.
- (c) Find the voltages  $V_1$ ,  $V_2$ ,  $V_3$  across resistors  $R_1$ ,  $R_2$ ,  $R_3$ , respectively.



**Solution:**

$$(a) R_{eq} = \left( \frac{1}{1\Omega + 3\Omega} + \frac{1}{5\Omega} \right)^{-1} = \frac{20}{9} \Omega = 2.22\Omega.$$

$$(b) I_1 = \frac{12V}{5\Omega} = 2.4A, \quad I_2 = I_3 = \frac{12V}{1\Omega + 3\Omega} = 3A.$$


$$(c) V_1 = R_1 I_1 = 12V, \quad V_2 = R_2 I_2 = 3V, \quad V_3 = R_3 I_3 = 9V.$$

## Unit Exam II: Problem #3 (Fall '14)



Consider the two-loop circuit shown.

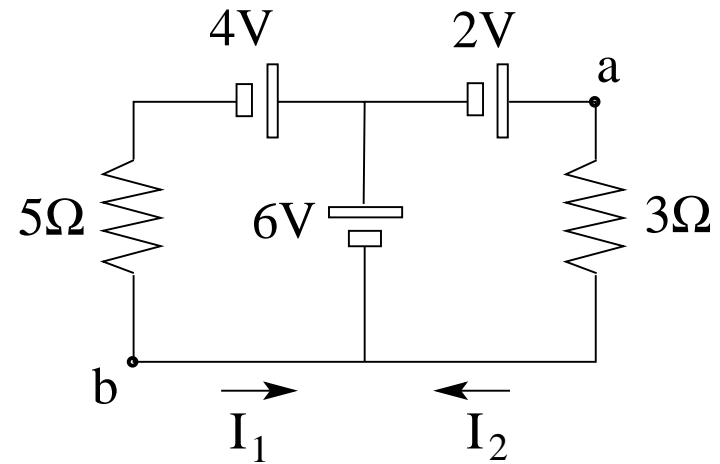- (a) Find the current  $I_1$ .
- (b) Find the current  $I_2$ .
- (c) Find the potential difference  $V_a - V_b$ .




## Unit Exam II: Problem #3 (Fall '14)



Consider the two-loop circuit shown.

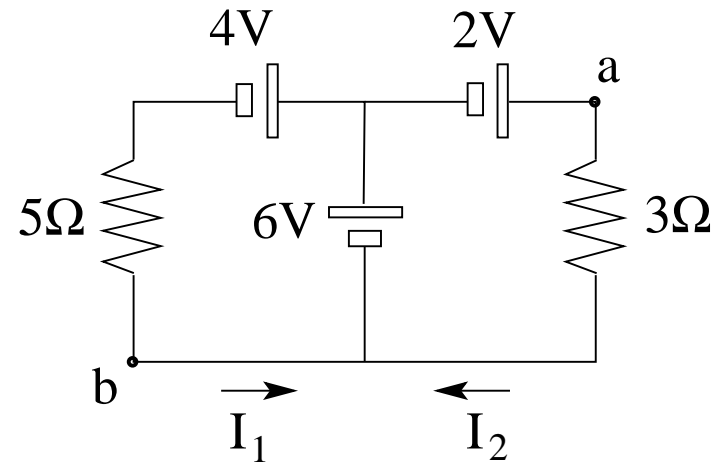- (a) Find the current  $I_1$ .
- (b) Find the current  $I_2$ .
- (c) Find the potential difference  $V_a - V_b$ .



**Solution:**

$$(a) \quad I_1 = \frac{6V - 4V}{5\Omega} = 0.4A.$$

$$(b) \quad I_2 = \frac{6V + 2V}{3\Omega} = 2.67A.$$

$$(c) \quad V_a - V_b = 6V + 2V = 8V.$$