
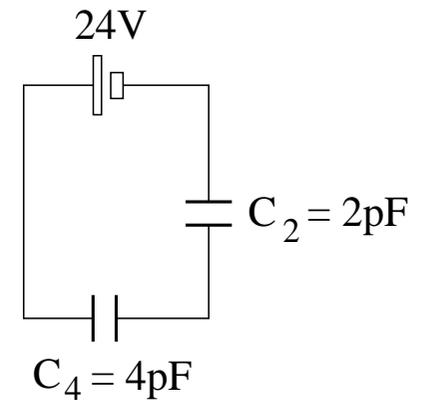


Unit Exam II: Problem #1 (Spring '15)

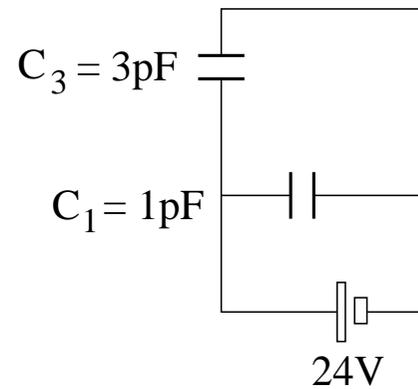

Both capacitor circuits are at equilibrium.

- (a) Find the charge Q_1 on capacitor 1.
- (b) Find the energy U_3 stored on capacitor 3.
- (c) Find the charge Q_2 on capacitor 2.
- (d) Find the voltage V_4 across capacitor 4.





Unit Exam II: Problem #1 (Spring '15)



Both capacitor circuits are at equilibrium.

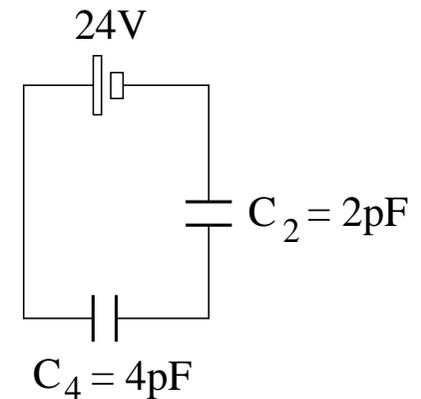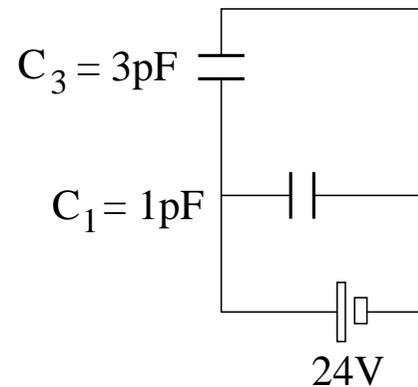- (a) Find the charge Q_1 on capacitor 1.
- (b) Find the energy U_3 stored on capacitor 3.
- (c) Find the charge Q_2 on capacitor 2.
- (d) Find the voltage V_4 across capacitor 4.



Solution:

(a) $Q_1 = C_1 V_1 = (1\text{pF})(24\text{V}) = 24\text{pC}.$

(b) $U_3 = \frac{1}{2} C_3 V_3^2 = \frac{1}{2} (3\text{pF})(24\text{V})^2 = 864\text{pJ}.$

(c) $C_{24} = \left(\frac{1}{C_2} + \frac{1}{C_4} \right)^{-1} = \frac{4}{3}\text{pF},$



$$Q_2 = Q_4 = Q_{24} = C_{24} V_{24} = \left(\frac{4}{3}\text{pF} \right) (24\text{V}) = 32\text{pC}.$$

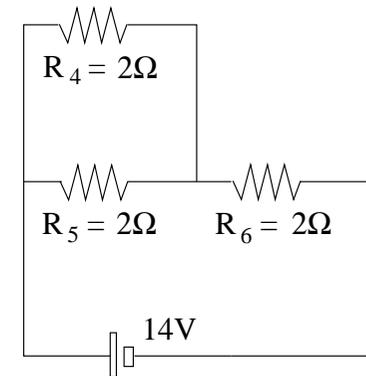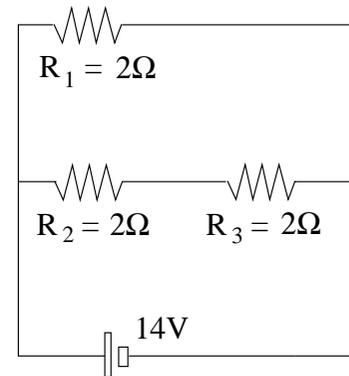(d) $V_4 = \frac{Q_4}{C_4} = \frac{32\text{pC}}{4\text{pF}} = 8\text{V}.$

Unit Exam II: Problem #2 (Spring '15)





In the two resistor circuits shown find the equivalent resistances R_{123} (left) and R_{456} (right). Then find the currents I_1, I_2, I_3 through the individual resistors on the left. and the currents I_4, I_5, I_6 through the individual resistors on the right.



Unit Exam II: Problem #2 (Spring '15)



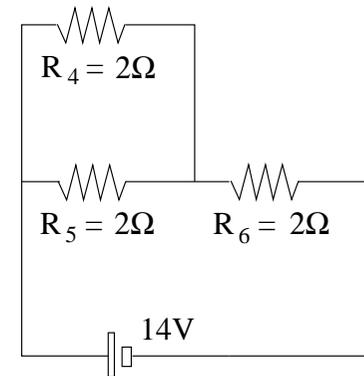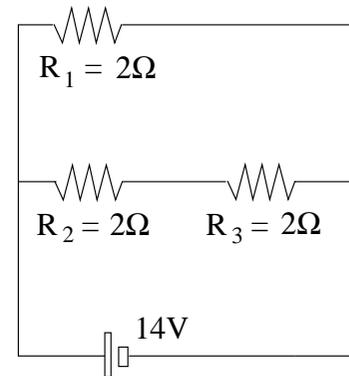In the two resistor circuits shown find the equivalent resistances R_{123} (left) and R_{456} (right). Then find the currents I_1, I_2, I_3 through the individual resistors on the left. and the currents I_4, I_5, I_6 through the individual resistors on the right.




Solution:

- $R_{23} = 2\Omega + 2\Omega = 4\Omega$, $R_{123} = \left(\frac{1}{2\Omega} + \frac{1}{4\Omega}\right)^{-1} = \frac{4}{3}\Omega$
- $R_{45} = \left(\frac{1}{2\Omega} + \frac{1}{2\Omega}\right)^{-1} = 1\Omega$, $R_{456} = R_{45} + R_6 = 3\Omega$
- $I_1 = \frac{14V}{2\Omega} = 7A$, $I_2 = I_3 = \frac{14V}{4\Omega} = 3.5A$
- $I_6 = I_{45} = \frac{14V}{3\Omega} = 4.67A$, $I_4 = I_5 = \frac{1}{2}I_6 = 2.33A$

Unit Exam II: Problem #3 (Spring '15)



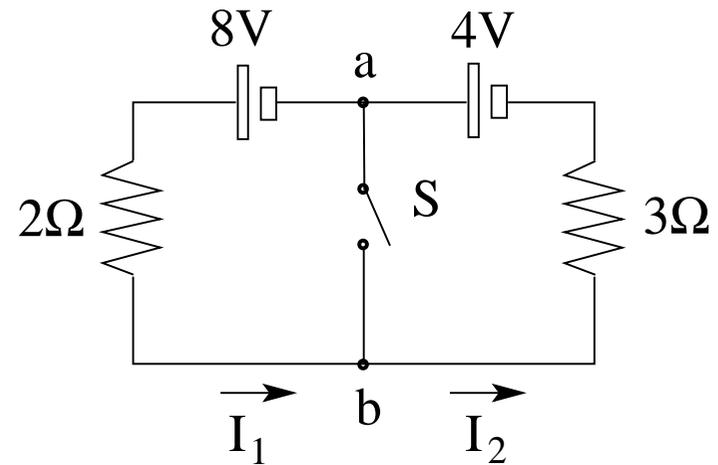In the circuit shown find the currents I_1 , I_2 , and the potential difference $V_b - V_a$
(a) if the switch S is open,
(b) if the switch S is closed.




Unit Exam II: Problem #3 (Spring '15)



In the circuit shown find the currents I_1 , I_2 , and the potential difference $V_b - V_a$

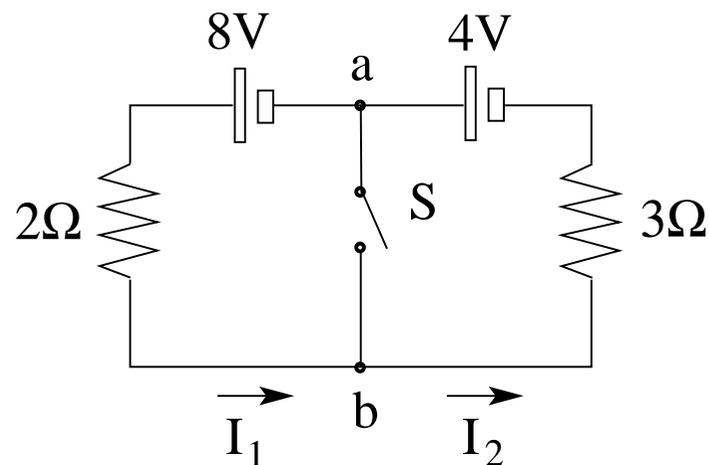- (a) if the switch S is open,
- (b) if the switch S is closed.



Solution:

$$(a) \quad I_1 = I_2 = \frac{12V}{5\Omega} = 2.4A$$

$$V_b - V_a = 8V - (2.4A)(2\Omega) = -4V + (2.4A)(3\Omega) = 3.2V.$$

$$(b) \quad I_1 = \frac{8V}{2\Omega} = 4A, \quad I_2 = \frac{4V}{3\Omega} = 1.33A, \quad V_b - V_a = 0.$$