

Capacitor Problem (2)



Consider two equal capacitors connected in series.

- (a) Find the voltages $V_A - V_B$, $V_B - V_C$, $V_A - V_D$.
- (b) Find the charge Q_A on plate A .
- (c) Find the electric field E between plates C and D .

