

# Capacitor Circuit (1)



Find the equivalent capacitances of the two capacitor networks.  
All capacitors have a capacitance of  $1\mu F$ .

