



Connect the three capacitors in such a way that the equivalent capacitance is  $C_{eq} = 4\mu\text{F}$ . Draw the circuit diagram.

