



Connect the three capacitors in such a way that the equivalent capacitance is $C_{eq} = 2\mu\text{F}$. Draw the circuit diagram.

