



Find the equivalent capacitances of the following circuits.

