



- (a) Name two capacitors from the circuit on the **left** that are connected in **series**.
- (b) Name two capacitors from the circuit on the **right** that are connected in **parallel**.

