

Capacitor Circuit (8)



In the circuit shown find the charges Q_1, Q_2, Q_3, Q_4 on each capacitor and the voltages V_1, V_2, V_3, V_4 across each capacitor

- (a) when the switch S is open,
- (b) when the switch S is closed.

