



A 1250W radiant heater is constructed to operate at 115V.

- (a) What will be the current in the heater?
- (b) What is the resistance of the heating coil?
- (c) How much thermal energy is generated in one hour by the heater?