

Resistor Circuit (1)



Consider the two resistor circuits shown.

- (a) Find the resistance R_1 .
- (b) Find the emf $\mathcal{E}_1$.
- (c) Find the resistance R_2 .
- (d) Find the emf $\mathcal{E}_2$.

