

Resistor Circuit (2)



Consider the two resistor circuits shown.

- (a) Find the resistance R_1 .
- (b) Find the current I_2 .
- (c) Find the current I_3 .
- (d) Find the resistance R_4 .

