

Resistor Circuit (3)



Consider the resistor and capacitor circuits shown.

- (a) Find the equivalent resistance R_{eq} .
- (b) Find the power P_2, P_3, P_4 dissipated in each resistor.
- (c) Find the equivalent capacitance C_{eq} .
- (d) Find the energy U_2, U_3, U_4 stored in each capacitor.

