

## Resistor Circuit (4)



Consider the resistor circuit shown.

- (a) Find the direction of the positive current (cw/ccw).
- (b) Find the magnitude of the current.
- (c) Find the voltage  $V_{ab} = V_b - V_a$ .
- (d) Find the voltage  $V_{cd} = V_d - V_c$ .

