

Resistor Circuit (6)



Consider the resistor circuit shown.

- (a) Choose a current direction and use the loop rule to determine the current.
- (b) Name the direction of positive current (cw/ccw).
- (c) Find $V_{ab} \equiv V_b - V_a$ along two different paths.

