



Consider two 24V batteries with internal resistances (a)  $r = 4\Omega$ , (b)  $r = 2\Omega$ .

- Which setting of the switch (L/R) produces the larger power dissipation in the resistor on the side?

