

## Resistor Circuit (8)



Consider the circuit of resistors shown.

- Find the equivalent resistance  $R_{eq}$ .
- Find the currents  $I_1, \dots, I_5$  through each resistor and the voltages  $V_1, \dots, V_5$  across each resistor.
- Find the total power  $P$  dissipated in the circuit.

