

## Applying the Junction Rule



In the circuit of steady currents, use the junction rule to find the unknown currents  $I_5, \dots, I_9$ .

