

## Resistor Circuit (12)



Consider the electric circuit shown.

- Find the equivalent resistance  $R_{eq}$  of the circuit.
- Find the total power  $P$  dissipated in the circuit.

