



At time $t = 0$ the capacitor in this circuit is discharged and the switch is being closed.

Find the current I_1

- (a) at $t = 0$,
- (b) at $t = \infty$.

Find the current I_2

- (c) at $t = 0$,
- (d) at $t = \infty$.

