

RC Circuit: Application (4)



In this 3-loop RC circuit, the switch S is closed at time $t = 0$.

- (a) Find the currents I_1, I_2, I_3 just after the switch has been closed.
- (b) Find the currents I_1, I_2, I_3 a very long time later.

