



In the RC circuit shown, the switch  $S$  has been open for a long time.

- (a) Find the currents  $I_1$  and  $I_2$  immediately after the switch has been closed.
- (b) Find the currents  $I_1$  and  $I_2$  a very long time later.

