

RL Circuit: Energy Transfer During Current Buildup



Loop rule: $IR + L\frac{dI}{dt} = \mathcal{E}$ ($I > 0$, $\frac{dI}{dt} > 0$)

- $I\mathcal{E}$: rate at which EMF source delivers energy
- $IV_R = I^2R$: rate at which energy is dissipated in resistor
- $IV_L = LI\frac{dI}{dt}$: rate at which energy is stored in inductor

Balance of energy transfer: $I^2R + LI\frac{dI}{dt} = I\mathcal{E}$

