

RL Circuit: Application (1)



Each branch in the circuit shown contains a 3A fuse. The switch is closed at time $t = 0$.

- (a) Which fuse is blown in the shortest time?
- (b) Which fuse lasts the longest time?

