



Each RL circuit contains a 2A fuse. The switches are closed at $t = 0$.

- In what sequence are the fuses blown?

