

RL Circuit: Application (8)



In the circuit shown the switch has been open for a long time.

Find the currents I_1 and I_2

- just after the switch has been closed,
- a long time later,
- as functions of time for $0 < t < \infty$.

