

Magnetic Induction: Application (14)



Consider an RC circuit with $R = 3\Omega$, $C = 2\mu\text{F}$ wired in the form of a square with sides of length $L = 0.9\text{m}$ and positioned in a region of uniform magnetic field \vec{B} pointing out of the plane. The magnitude of the field varies with time as shown in the graph. At time $t = 0$ the capacitor is discharged.

Find the charge on the capacitor as a function of time

- (a) for $0 < t < 6\mu\text{s}$
- (b) for $t > 6\mu\text{s}$.

